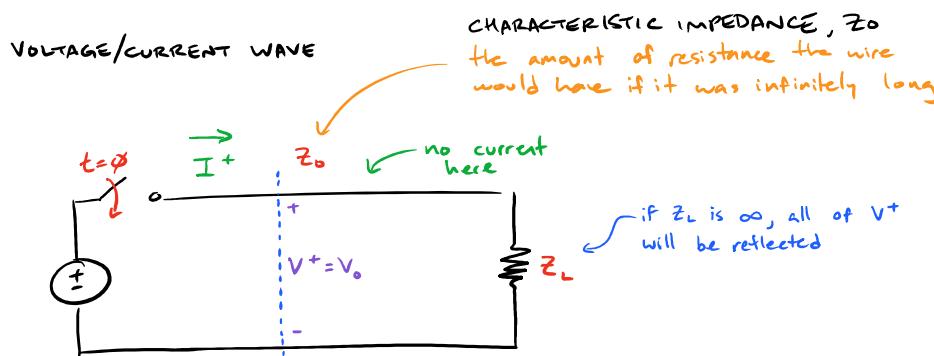


## Quiz 1 Review

Thursday, February 4, 2016 7:11 PM



let's say it takes 1 second for current to reach load

@ $t=0$  we close switch



current will start to flow based solely on the characteristic impedance,  $Z_0$ , of the transmission line.

@ $t < 1$  there is voltage at wave pulse  $V_0$ ,  
 some of the wire has current, some doesn't

@t=1 V<sub>o</sub> reaches the load

if  $Z_L = Z_0$ , current will flow through the same ← WE WANT TO MATCH IMPEDANCES TO PROVIDE MAXIMUM POWER TRANSFER AND MINIMIZE DISTORTION  
 if  $Z_L \neq Z_0$ , some voltage will be reflected

↳ then if internal impedance of the source is different from  $Z_0$ , it will again be reflected back.


@  $t = \infty$  circuit is stabilized so transmission resistance is basically gone

## SOURCE SEES



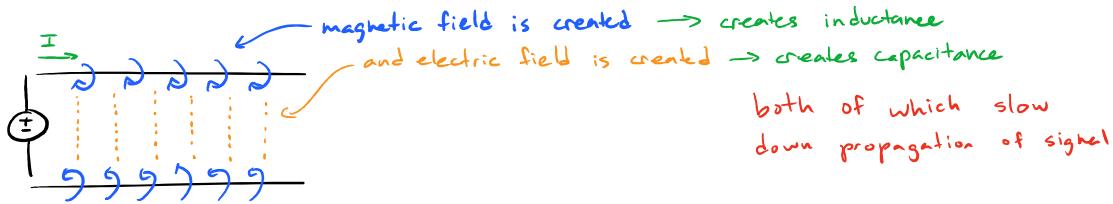
## REALISTIC MODEL OF A TRANSMISSION LINE

$\xrightarrow{I}$  magnetic field is created  $\rightarrow$  creates inductance  
 and electric field is created  $\rightarrow$  creates capacitance



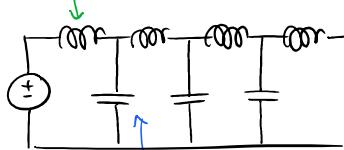inductor opposes current by generating voltage against it.  
then eventually becomes S.C. after current stabilizes



an accurate representation of what is fundamentally happening in transmission line to delay propagation

"PULSE FORMING NETWORK"  
then the capacitor gets charged and drains voltage while inductor stabilizes, then becomes an open-circuit which allows next inductor to get current, etc.

ASSUMING LOSSLESS TRANSMISSION

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

↳ resistive, although composed of the inductance & capacitance of the wire

speed of the wave is proportional to how fast the inductors reach full current and how fast the capacitors can be charged

$$v = \frac{1}{\sqrt{LC}} \quad \approx \frac{2}{3}c \text{ for coaxial cable}$$

↳ also  $v = \lambda f$

note all these  $Ls$  &  $Gs$  &  $Rs$  and such are per unit length

#### LOSSLESS PROPAGATION

- No power is dissipated in transmission line
- All power at the input reaches output

$$R = G = \emptyset$$

→ two sources of loss are

1. LEAKAGE THROUGH DIELECTRIC
2. RESISTANCE OF THE CONDUCTOR

MODELING THE TRANSMISSION LINE USING MATH THIS TIME  
(I'm going to skip the proofs & derivations though)

#### VOLTAGE EQUATION

$$\frac{\delta V}{\delta z} = - \left( Rz + L \frac{\delta I}{\delta t} \right)$$

#### CURRENT EQUATION

$$\frac{\delta I}{\delta z} = - \left( Gz + C \frac{\delta V}{\delta t} \right)$$

Differential Equations

## Differential Equations

$$\frac{\delta V}{\delta z} = - \left( Rz + L \frac{\delta I}{\delta t} \right)$$

$$\frac{\delta I}{\delta z} = - \left( Gz + C \frac{\delta V}{\delta t} \right)$$

where we took  $\Delta z$  to mean a short wire element of length  $\Delta z$

NOW SOLVING FOR A LITTLE MORE

### GENERAL VOLTAGE EQUATION

$$\frac{\delta^2 V}{\delta z^2} = LC \frac{\delta^2 V}{\delta t^2} + (LG + RC) \frac{\delta V}{\delta t} + RGV$$

### GENERAL CURRENT EQUATION

$$\frac{\delta^2 I}{\delta z^2} = LC \frac{\delta^2 I}{\delta t^2} + (LG + RC) \frac{\delta I}{\delta t} + RG I$$

↑ these are both in the form of the wave equation  $\frac{\delta^2 f(z,t)}{\delta z^2} = \frac{1}{v^2} \frac{\delta^2 f(z,t)}{\delta t^2}$

which has the solution  $f(z,t) = f_i(t - \frac{z}{v}) + f_e(t + \frac{z}{v})$

forward moving component  
backward moving component

OUR SOLUTION →

$$V = V^+ + V^-$$

positive current is defined by convention as  
moving in the clockwise direction (→)

## Wave Equations

↑ note that because  $v = \frac{1}{\sqrt{LC}}$ ,  $\frac{1}{v^2} = LC$   
which you can see in our equation!

love dat engineering

the negative sign is to counteract  
the negative direction of current, the  
voltage isn't necessarily negative

NOW LET'S TALK ABOUT THOSE PESKY REFLECTIONS

RECAP: if the load impedance doesn't match the characteristic impedance of the transmission line, there will be a reflection which reduces power transmission → bad

### VOLTAGE REFLECTION COEFFICIENT, $\Gamma$

↑ the fraction of the voltage of the incident wave that's reflected by the load resistance

$$V^- = \Gamma V^+$$

$$\frac{\text{net load voltage}}{\text{net load current}} = R_L = Z_0 \frac{1+\Gamma}{1-\Gamma}$$

$$\Gamma = \frac{R_L - Z_0}{R_L + Z_0}$$

← we can solve for the reflection coefficient as a function of the load and characteristic impedance

if  $R_L > Z_0 \rightarrow \Gamma > 0 \rightarrow$  voltage same sign, current sign swap

if  $R_L < Z_0 \rightarrow \Gamma < 0 \rightarrow$  voltage sign swap, current same sign

AND DON'T FORGET, THE SOURCE ALSO HAS REFLECTIONS

↳ source has internal resistance  $R_g$

→ we calculate amplitude of initial voltage wave as a voltage divider between  $R_g$  &  $Z_0$


$$V^+ = V_o \frac{Z_0}{Z_0 + R_g}$$

→ we calculate reflection coefficient same way as with load

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0}$$

VOLTAGE REFLECTION DIAGRAM (totally going to be on exam)

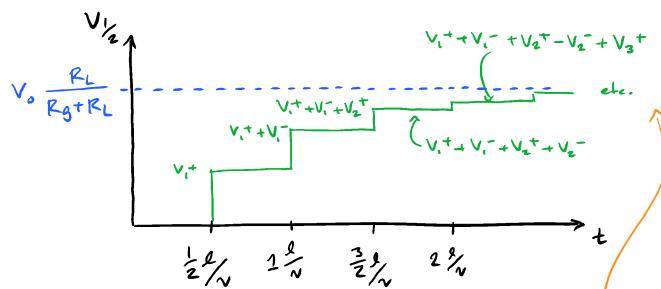let's say we want to observe the voltage  $\frac{1}{2}l$  of the way down the transmission line



asymptotically approaches voltage divider value  
↳ eventually will be treated as a wire

FIRST ROUND TRIP

$$V_i^+ = V_o \frac{Z_0}{Z_0 + R_g}$$

$$\text{Final voltage} = V_o \frac{R_L}{R_g + R_L}$$

$$V_i^- = \Gamma_L V_i^+$$

SECOND ROUND TRIP

$$V_2^+ = \Gamma_g V_1^- = \Gamma_g \Gamma_L V_i^+ \quad V_2^- = \Gamma_L V_2^+ = \Gamma_L^2 \Gamma_g V_i^+$$


THIRD ROUND TRIP

$$V_3^+ = \Gamma_g V_2^- = \Gamma_L^2 \Gamma_g^2 V_i^+ \quad V_3^- = \Gamma_L^3 \Gamma_g^2 V_i^+$$

etc.

CURRENT REFLECTION DIAGRAM

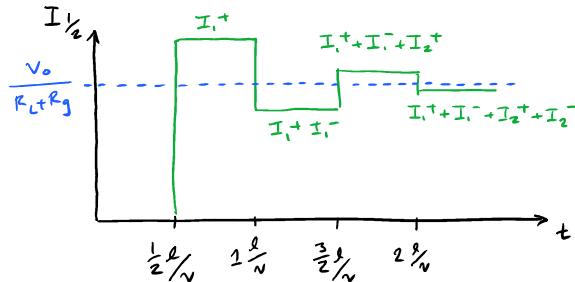use  $V^+ = Z_0 I^+$  and  $V^- = -Z_0 I^-$



$$\text{Final current} = \frac{V_o}{R_L + R_g}$$

FIRST ROUND TRIP

$$I_i^+ = \frac{V_i^+}{Z_0} \quad I_i^- = -\frac{V_i^-}{Z_0}$$

SECOND ROUND TRIP

$$I_2^+ = \frac{V_2^+}{Z_0} \quad I_2^- = -\frac{V_2^-}{Z_0}$$


etc.

$\frac{1}{2} \frac{l}{v}$     $\frac{1}{v}$     $\frac{3}{2} \frac{l}{v}$     $2 \frac{l}{v}$     $t$

$$\frac{l_2}{2} = \frac{l}{z_0}, \quad l_2 = \frac{l}{z_0}$$

etc.

Ex]

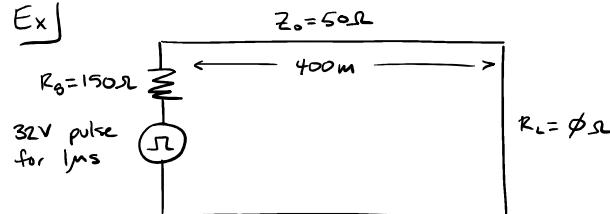

$$\text{velocity of wave} = 200 \frac{\text{m}}{\mu\text{s}}$$

PLOT REFLECTION DIAGRAMS AT SOURCE  
FOR AT LEAST 4 ROUND-TRIPS

=

DETERMINE REFLECTION COEFFICIENTS

$$\Gamma_L = \frac{R_L - z_0}{R_L + z_0} = -1 \quad \Gamma_g = \frac{R_g - z_0}{R_g + z_0} = \frac{1}{2}$$

DETERMINE INITIAL WAVE PULSE & RTT

$$V_1^+ = V_0 \frac{z_0}{R_g + z_0} = 32 \frac{1}{4} = 8V \quad T = 2 \frac{l}{v} = 2 \frac{400\text{m}}{200 \frac{\text{m}}{\mu\text{s}}} = 4 \mu\text{s}$$

DETERMINE REST OF PULSES

$$\begin{aligned} V_1^+ &= 8V \\ V_2^+ &= \Gamma_L V_1^- = -4V \\ V_3^+ &= 2V \\ V_4^+ &= -1V \end{aligned}$$

$$\begin{aligned} V_1^- &= \Gamma_g V_1^+ = -1 \cdot 8 = -8V \\ V_2^- &= 4V \\ V_3^- &= -2V \\ V_4^- &= 1V \end{aligned}$$



$$\begin{aligned} I_1^+ &= \frac{V_1^+}{z_0} = \frac{8V}{50\Omega} = 160 \text{mA} \\ I_2^+ &= -80 \text{mA} \\ I_3^+ &= 40 \text{mA} \\ I_4^+ &= -20 \text{mA} \end{aligned}$$



$$\begin{aligned} I_1^- &= \frac{-V_1^-}{z_0} = 160 \text{mA} \\ I_2^- &= -80 \text{mA} \\ I_3^- &= 40 \text{mA} \\ I_4^- &= -20 \text{mA} \end{aligned}$$

recall that we are measuring these values right at the source, this is where the interference between the incoming wave & the reflected wave is, so they will momentarily sum. for example:


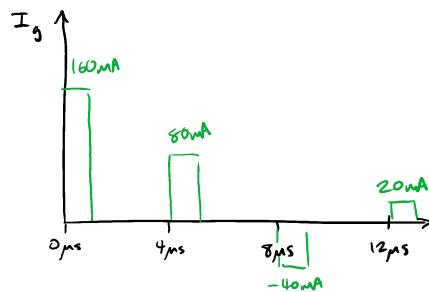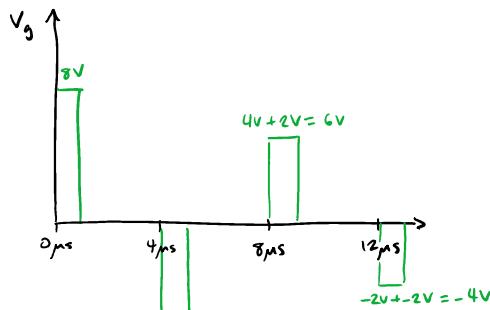
$$\therefore V_{\text{measured}} = V_1^- + V_2^+, V_2^- + V_3^+, \text{ etc.}$$



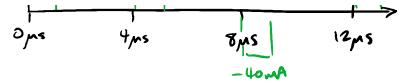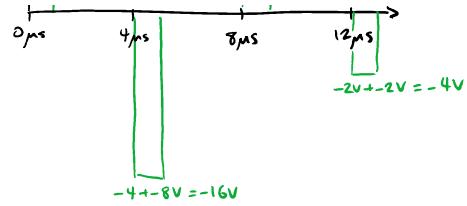

ALRIGHT, LET'S START TALKING ABOUT STEADY-STATE

PHASE CONSTANT,  $\beta \frac{\text{rad}}{\text{s}}$  → represents "spatial frequency", phase-shift per unit distance

$$\boxed{\beta = \frac{2\pi}{\lambda} = \frac{\omega}{v_p}}$$

$$\begin{aligned} V_s &= |V_0| \cos [\omega(t - \frac{z}{v}) + \phi] \\ &= V_0 \cos (\omega t - \beta z) \\ &= V_0 e^{j\omega t} e^{-j\beta z} \end{aligned}$$

this component doesn't really effect impedance  
so we'll just drop it.

VOLTAGE PHASOR

$$\boxed{V_s = V_0 e^{-j\beta z}}$$

In steady state realize there will be a forward wave and a ret backward wave

↳ sum of all incident and reflected waves

WAVE IMPEDANCE

$$Z_w(z) = \frac{V^+ e^{-j\beta z} + V^- e^{+j\beta z}}{I^+ e^{-j\beta z} + I^- e^{+j\beta z}}$$

using euler's identity  $\because R = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$\boxed{Z_w(z) = Z_0 \left[ \frac{Z_L \cos \beta z - j Z_0 \sin \beta z}{Z_0 \cos \beta z - j Z_L \sin \beta z} \right]}$$

when the line is equal to half the signal wavelength

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{m\lambda}{2} = m\pi \quad (m = 0, 1, 2, \dots)$$

$$\therefore Z_{in} = Z_w(l) = Z_0 \left[ \frac{Z_L \cos m\pi + j Z_0 \sin m\pi}{Z_0 \cos m\pi + j Z_L \sin m\pi} \right]$$

$$Z_{in} = Z_{in}$$

when the line is equal to an odd multiple of a  $\frac{1}{4}$  wavelength

$$\beta l = \frac{2\pi}{\lambda} (2m+1) \frac{\lambda}{4}$$

$$\therefore Z_{in} = \frac{Z_0^2}{Z_L}$$

$$\beta L = \frac{2\pi}{\lambda} (2m+1) \frac{\lambda}{4}$$

$$\therefore Z_{in} = \frac{Z_0^2}{Z_L}$$

## STANDING WAVES


happens when load not matched to transmission line

↳ the signal interferes constructively at some points & destructively at others

the load impedance can be calculated from the distance between the load and the minimum voltage and the voltage standing wave ratio

↳  $Z_{min}$
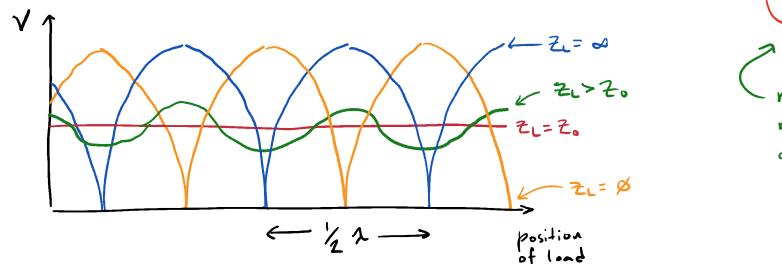
### STANDING WAVES ON A TRANSMISSION LINE



$$V_{max} = V_0 (1 + |\Gamma|)$$

$$V_{min} = V_0 (1 - |\Gamma|)$$

$$z_{max} = \frac{-1}{2\beta} (\phi + 2n\pi)$$

$$z_{min} = \frac{-1}{2\beta} (\phi + (2n+1)\pi)$$

positions of max/min voltages along transmission line

$n = 0, 1, 2, \dots$

$$S = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

read from rotating  $\Gamma$  to the right on the horizontal line on Smith Chart

$$\lambda = \frac{c}{f} = \frac{3/2}{100 \cdot 10^6}$$

$$\frac{3}{2}$$

## SMITH CHART


allows us to solve problems by relating

- input impedance
- reflection coefficient
- output impedance
- line length

built inside the unit-circle, each point representing rectangular coordinates of the reflection coefficient,  $\Gamma$

$\Gamma_{imaginary} \uparrow$

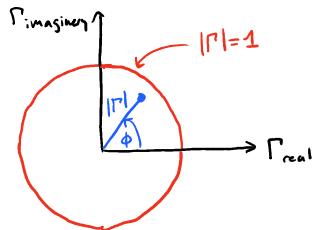coordinates of the reflection coefficient,  $\Gamma$



to use you must normalize your input impedance because the chart is calibrated in terms of per unit values of impedance & admittance


i.e. divide your impedances by the characteristic impedance

$$z = \frac{Z}{Z_0}$$

$$\Gamma = \frac{z - 1}{z + 1}$$


$$z = \frac{1 + \Gamma}{1 - \Gamma}$$

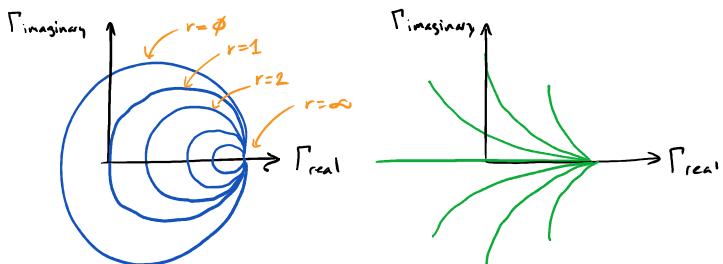smith chart is a graphical representation of these equations




circles represent real part of impedance

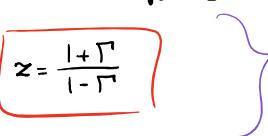curved lines represent imaginary part of impedance



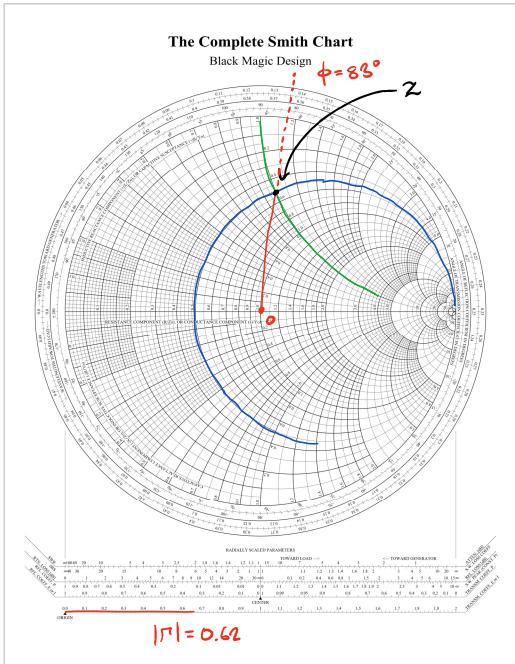Ex) Find reflection coefficient where load impedance is  $25 + j50 \Omega$



$$Z_L = 25 + j50\Omega, \text{ assume } Z_0 = 50\Omega$$

$$z = \frac{Z_L}{Z_0} = 0.5 + j1\Omega$$

plot the normalized impedance  
on the smith chart

real part  
imaginary part

measure distance from origin to z.  
project that distance onto transmission coefficient scale

$$|\Gamma| = 0.62$$

measure angle from "angle of reflection coefficient" scale

$$\phi = 83^\circ$$

Ex) Find the input impedance & VSWR from the load impedance

$Z_g$  will be on the circle with the radius of  $|\Gamma|$ , 0.62 in the previous example,  
rotated  $\times$  wavelengths toward the generator as indicated on the chart


and vice-versa if we have the input impedance  
and we want the load impedance


$Z_L \rightarrow Z_g$  rotate toward generator

$Z_g \rightarrow Z_L$  rotate toward load

To find VSWR, rotate point along radius  
to the right until purely resistive (flat)

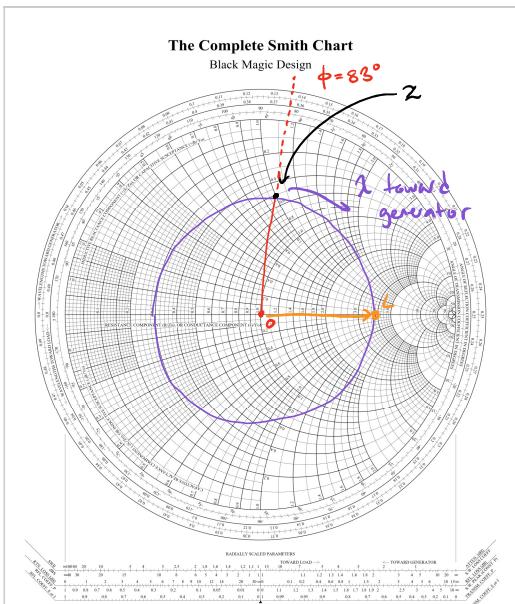↳ there are two flat points with  
the radius, take the larger (rightmost on the graph)



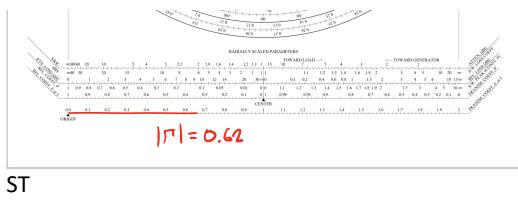

ST

WE'LL COME BACK TO SMITH CHARTS MOMENTARILY


But first let's talk about matching transmission lines → RECAP: it minimizes losses & distortion

we can create a matched system by doing two things  
that seem insane in DC called **SINGLE STUB MATCHING**

1. short-circuit the load  
lower EM radiation leakage




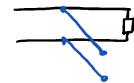2. open-circuit the load  
more practical for  
microstrip circuits



let's talk about the first one

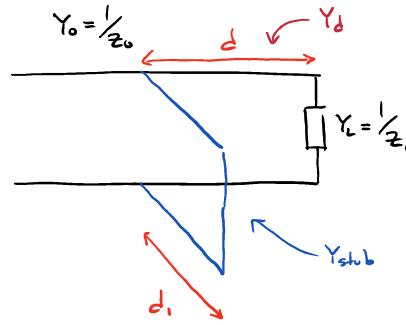Two design parameters      distance of the stub from the load,  $d$   
                                     length of the stub,  $d_1$



since it is in parallel, it'll be easier  
to work with admittance than impedance

IN ORDER TO MATCH,  $Y_{\text{stub}} + Y_d = Y_0$


let's do an example for how to solve  
this using the Smith Chart

$$d_1 = \frac{\theta_1}{4\pi} \lambda$$

$$Y_d = Y_0 \pm jB_{\text{stub}}$$

$$Y_{\text{stub}} = \mp jB_{\text{stub}}$$

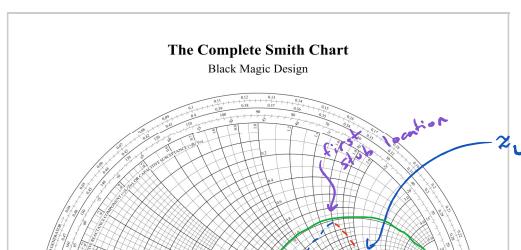Ex) Design a circuit stub to match load  $100 + j100 \Omega$  to a  $50 \Omega$  transmission line



$$Z_L = 100 + j100 \Omega \rightarrow Z = \frac{Z_L}{Z_0} = 2 + j2$$


plot  $Z_L$  point

draw  $\Gamma$  line from origin to point

draw unit circle along  $r=1$  (unitary conductance circle)

project circle of radius  $\Gamma$  from origin to intersections with unit circle

draw lines from origin to intersection

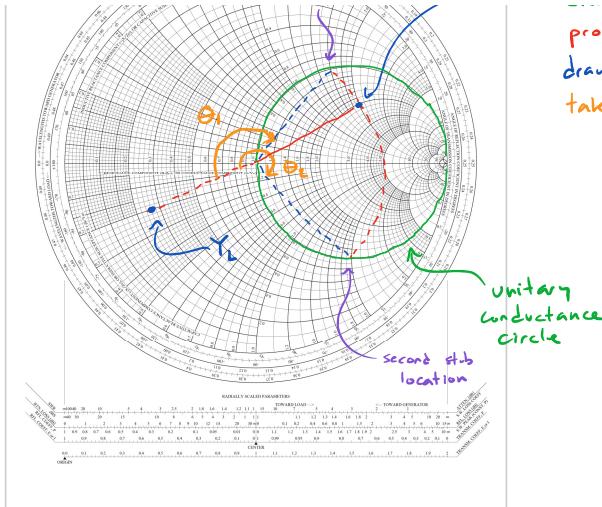

project circle of radius  $\Gamma$  from origin to intersections with unit circle  
 draw lines from origin to intersection  
 take angles between load admittance line & intersections

↳ you can put a stub at either of the corresponding locations.

There will always be two solutions:

first has a positive susceptance, must be cancelled with capacitive stub  
 second has a negative susceptance, must be cancelled with inductive stub

$$\theta = \frac{4\pi}{\lambda} d_1 \rightarrow d_1 = 160^\circ \frac{1/4}{180} \lambda = 0.2222\lambda$$

### LOSS IN TRANSMISSION LINES

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

loss leads to distortion

$$\alpha + j\beta = \sqrt{ZY}$$

"attenuation coefficient"

$$\text{signal decay, } \frac{M_p}{m}$$

$$\text{phase constant, } \frac{v_{rad}}{m}$$


incident term

reflected term

$$V(z,t) = V^+ e^{-\alpha z} \cos(\omega t + \beta z) + V^- e^{\alpha z} \cos(\omega t - \beta z)$$

exponential dec forward

exponential decay backward

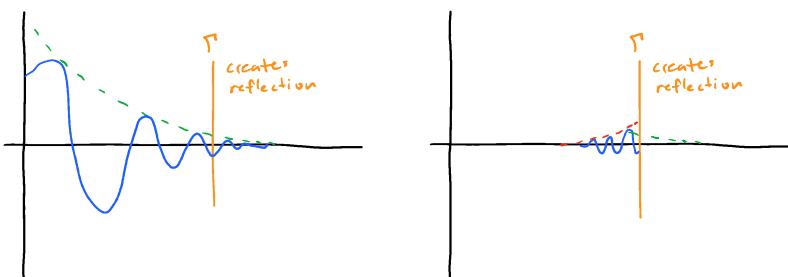

### LOW-LOSS PROPAGATION

$R \ll WL$ ,  $G \ll WC$  ↗ often true in practice

$$\alpha \approx \frac{1}{2} \left( R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right)$$

$$\beta \approx \omega \sqrt{LC} \left[ 1 + \frac{1}{8} \left( \frac{G}{WC} - \frac{R}{WL} \right)^2 \right]$$

↗ with this value, can determine phase velocity that depends on frequency

In lossy system:

$$Z_0 \neq \sqrt{\frac{L}{C}}$$

$$n_p = \frac{\omega}{\beta}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R+jWL}{G+jWC}} = |Z_0| e^{j\theta}$$

$$|Z_0| \neq 0$$

HEAVISIDE CONDITION

↗ means the signal is not distorted if condition is met

$$\frac{R}{L} = \frac{G}{C}$$

to achieve this, you can modify any term but really only want to modify L as increasing R or G increases distortion

$$R \neq 0 \text{ } \& \text{ } G \neq 0$$

loss increases w/ frequency b/c R increases w/ frequency

POWER TRANSMISSION

power decays 2x as fast as V or I

$$\langle P \rangle = \frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha z} \cos \theta$$

time-average power

$$= 20 \log \frac{|V_0(0)|}{|V_0(z)|}$$

POWER ATTENUATION

$$L_{dB} = 10 \log \left( \frac{\langle P(0) \rangle}{\langle P(z) \rangle} \right) = 10 \log e^{2\alpha z} = 20\alpha z \text{ log } e = 8.69 \alpha z$$

→ power at any point along transmission line

→ converted to decibels so that losses of connected lines can be added

power at point z

Ex) A 20m length of transmission line has a loss of 2dB from end-to-end. a) what fraction of power reaches the output? b) what fraction of power reaches the midpoint? c) what attenuation coefficient does this represent?

$$\alpha$$

$$\text{fraction of input power @ 20m} = \frac{\langle P(20) \rangle}{\langle P(0) \rangle}$$

$$L_{dB} = 10 \log \frac{\langle P(z) \rangle}{\langle P(0) \rangle} \rightarrow 2 dB = 10 \log \frac{\langle P(0) \rangle}{\langle P(20) \rangle}$$

$$\frac{\langle P(0) \rangle}{\langle P(20) \rangle} = 10^{-2/10} = 0.63$$

$$\rightarrow \frac{\langle P(20) \rangle}{\langle P(0) \rangle} = 10^{-2/10} = \boxed{0.63} \quad \leftarrow 63\% \text{ of power reaches output}$$

$$\text{loss per distance} = \frac{2 dB}{20m} = 0.1 \frac{dB}{m}$$

$$@ 10m, 10m(0.1 \frac{dB}{m}) = 1 dB$$

$$1 dB = 10 \log \frac{\langle P(0) \rangle}{\langle P(10) \rangle}$$

$$\rightarrow \frac{\langle P(10) \rangle}{\langle P(0) \rangle} = 10^{-1/10} = \boxed{0.79} \quad \leftarrow 79\% \text{ of power reaches midpoint}$$

$$10 \log \left( \frac{\langle P(0) \rangle}{\langle P(2) \rangle} \right) = 8.69 \text{ dB} \rightarrow \alpha = \frac{2 dB}{8.69 \cdot 20m} = \boxed{0.0115 \frac{Np}{m}}$$

2 dB

### REFLECTED POWER

$$\boxed{\frac{\langle P_r \rangle}{\langle P_i \rangle} = |\Gamma|^2} \quad \leftarrow \text{ratio of reflected power to incident power}$$

### TRANSMITTED POWER

$$\boxed{\frac{\langle P_t \rangle}{\langle P_i \rangle} = 1 - |\Gamma|^2}$$

Ex) Two lossy lines are joined end-to-end. First line is 10m long w/ loss of 0.2 dB/m. Second line is 15m long w/ loss of 0.1 dB/m. Reflection coefficient between lines is 0.3 & power at input is 100mW. Determine total loss & determine transmitted power.

$$\frac{\langle P_t \rangle}{\langle P_i \rangle} = 1 - |\Gamma|^2 \quad \rightarrow \text{loss at junction} \quad \boxed{L_{jdB} = 10 \log \frac{\langle P_i \rangle}{\langle P_t \rangle (1 - |\Gamma|^2)} = 10 \log \frac{1}{1 - |\Gamma|^2}}$$

$$L_{dB} = 10 \log \frac{\langle P(0) \rangle}{\langle P(25) \rangle} \quad \rightarrow 10 \log \frac{1}{1 - 0.3^2} = 0.4096 dB$$

$$\text{loss in line 1 } L_1 = 10m \left( 0.2 \frac{dB}{m} \right) = 2 dB$$

$$\text{loss in line 2 } L_2 = 15m \left( 0.1 \frac{dB}{m} \right) = 1.5 dB$$

$$\text{TOTAL LOSS } L_T = 2 dB + 1.5 dB + 0.41 dB = 3.91 dB$$

TRANSMITTED POWER

$$L_{dB} = 10 \log \frac{P(t)}{P(r)} \rightarrow 3.91 dB = 10 \log \frac{100 mW}{P_t}$$

$$P_t = 41.6 mW$$

@ two connected lines w/ different characteristic impedances

→ reflections occur at junction

$$\Gamma = \frac{Z_{0e} - Z_{0l}}{Z_{0e} + Z_{0l}}$$

$$\text{power that propagates into second line: } |1 - |\Gamma|^2|$$

SPECIAL CASES:

QUATER-WAVE MATCHING

↳ limited to where

$$l \approx (2m+1) \frac{\lambda}{4} \quad (\text{odd multiple})$$

line length is  $\frac{1}{4}\lambda$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_{0e} = \sqrt{Z_0 Z_0 l}$$

line length is  $\frac{1}{2}\lambda$

$$Z_{in} = Z_L$$