

# Super Phasors

Monday, February 22, 2016 3:31 PM

WHAT IS THE VOLTAGE ACROSS RESISTOR

$$v(t) = L \frac{di}{dt} = 0.01 \frac{d}{dt} 5 \cos(2000t)$$

$$= 0.01 (-10000 \sin(2000t))$$

$$= -100 \sin(2000t)$$

$$= 100 \sin(2000t + \frac{180}{180}\pi)$$

$$= 100 \cos(2000t + \frac{180\pi}{180} - \frac{90}{180}\pi)$$

$$= 100 \cos(2000t + \frac{90}{180}\pi)$$

$$i(t) = 5 \cos 2000t \quad 0.01H$$


to write voltage with positive amplitude:  $-\sin(\alpha) = \sin(\alpha + \frac{180\pi}{180})$

to write voltage w.r.t cosine as given:  $\sin(\alpha) = \cos(\alpha - \frac{90\pi}{180})$

SAME EXERCISE, NOW USING PHASORS

$$Z_L = j\omega L \rightarrow Z_L = j(2000 \frac{rad}{s}) 0.01H = j20\Omega$$

$$\bar{I} = (\frac{5}{\sqrt{2}} \angle 0^\circ)$$

$$\bar{V} = \bar{I} Z_L = (\frac{100}{\sqrt{2}} \angle 90^\circ)$$

$$\hookrightarrow v(t) = 100 \cos(2000t + \frac{90\pi}{180})$$

Ex) TWO PURE ELEMENTS ARE CONNECTED IN SERIES WITH THE FOLLOWING  $V$  &  $I$ , WHAT ARE THEY?

$$v(t) = 255 \sin(300t + \frac{45}{180}\pi)$$

$$\downarrow$$

$$\bar{V} = \frac{255}{\sqrt{2}} \angle 45^\circ$$

$$i(t) = 8.5 \sin(300t + \frac{15}{180}\pi)$$

$$\downarrow$$

$$\bar{I} = \frac{8.5}{\sqrt{2}} \angle 15^\circ$$


$$\bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{\frac{255}{\sqrt{2}} \angle 45^\circ}{\frac{8.5}{\sqrt{2}} \angle 15^\circ} = 30 \angle 30^\circ \Omega = 25.98 + j15$$

$$\begin{aligned} R &= 25.98\Omega & \omega L &= 15 \\ L &= \frac{15}{30} = 50mH \end{aligned}$$

## ANGLES

$$\bar{Z} = R + jX = Z \angle \theta$$

$$\theta = \arctan \frac{X}{R}$$

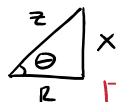


the angle between the voltage & current is the same as the angle b/w the resistance and the reactance


$$\begin{aligned} \bar{V} &= V \angle \alpha & \bar{I} &= I \angle \beta \\ Z \angle \theta &= \frac{\bar{V}}{\bar{I}} = \frac{V}{I} \angle (\alpha - \beta) \\ \theta &= \alpha - \beta \end{aligned}$$



## RL BRANCH

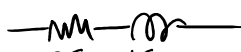
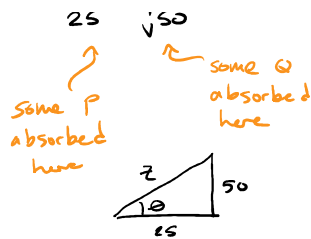
$$\theta = \arctan \frac{50}{25} = 63.435^\circ$$




$$\rightarrow \theta = \angle V - \angle I$$


$$\rightarrow \angle V = \angle I + 63.435^\circ$$

the current lags by  $63.435^\circ$

### RC BRANCH

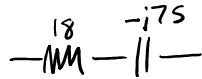
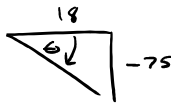
$$\theta = \tan^{-1} \frac{-75}{18} = -76.504^\circ$$




$$\rightarrow \theta = \angle V - \angle I = -76.504^\circ$$

$$\rightarrow \angle I = \angle V + 76.504^\circ$$

current leads by  $76.5^\circ$

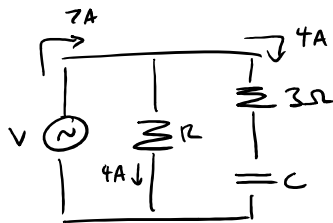
Ex) IN THE CIRCUIT BELOW, THE CURRENT HAVE BEEN MEASURED WITH AN AC AMMETER?



DETERMINE  $R$ ,  $C$ , &  $V_{\text{source}}$


$$f = 60 \text{ Hz}$$

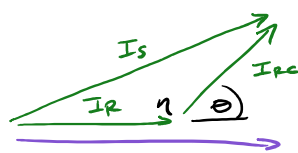1. Choose any voltage or current as base reference,
2. we'll choose  $V$  to be  $0^\circ$
3. the current through the  $R$  branch,  $I_R$ , will be in-phase with voltage
4. the current through  $RC$  must be slightly leading



cosine law

$$c^2 = a^2 + b^2 - 2ab \cos(\eta)$$

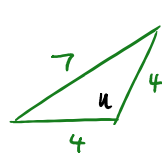

$$\eta = 122.0955^\circ$$

$$\rightarrow \theta = 180 - \eta = 57.9045^\circ$$

$$\theta = \tan^{-1} \frac{X}{R}$$

$$\rightarrow X_C = R \tan \theta = 3 \tan 57.904 = 4.784 \Omega$$

angle actually (-)ive b/c capacitive

$$X = \frac{1}{\omega C} \rightarrow C = \frac{1}{2\pi 60 (4.784)} = 554 \mu\text{F}$$


$$V = IZ \rightarrow V_{\text{rms}} = I_{\text{rms}} Z_{\text{rc}} = 4A (\sqrt{3^2 + 4.784^2}) = 22.59 \text{ V}$$

$$Z = \sqrt{R^2 + X^2}$$


$$R = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{22.59 \text{ V}}{4 \text{ A}} = 5.647 \Omega$$

POWER

## POWER

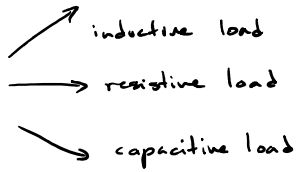


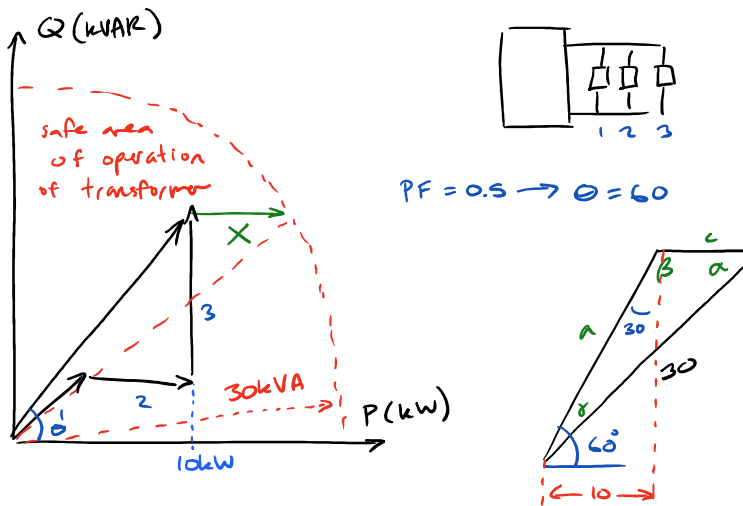Ex) transformer rated for 30kVA, it feeds a load of 10kW @ PF=0.5 lagging, how much resistive load can you add to bring to full rated power?



$$a = \frac{10}{\cos(60^\circ)} = 20 \quad \beta = (180 - 90 - \theta) + 90 = 120$$

from cosine law

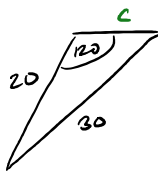

$$c = 14.5 \text{ kW}$$