

# DC Motors

Tuesday, February 16, 2016 12:06 PM

NAMEPLATE:

maximum mechanical output power @ full load


external source feeding motor

$P_{rated} = 15 \text{ hp}$   
 $V_t = 240 \text{ V}$   
 $n_{rated} = 1200 \text{ rpm}$   
 $R_a = 0.40 \text{ ohm}$   
 $R_s = 0.04 \text{ ohm}$

$I_{L,rated} = 55 \text{ A}$   
 $N_p = 2700 \text{ turns per pole}$   
 $N_s = 27 \text{ turns per pole}$   
 $R_f = 100 \text{ ohm}$   
 $R_{adj} = 100 \text{ to } 400 \text{ ohm}$

Rotational losses = 1800W at full load.  
Magnetization curve on next slide.


To start,  $R_{adj}$  is set at 175 ohm

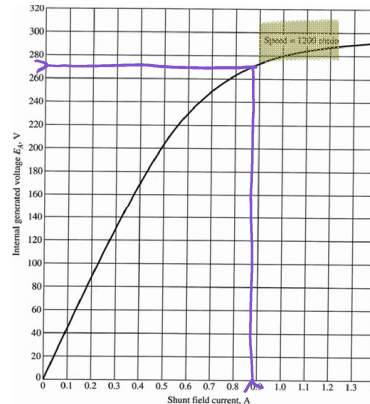

Ex) GIVEN ABOVE NAMEPLATE AND MAGNETIZATION CHARACTERISTIC, FIND IDLING VELOCITY OF MOTOR

=

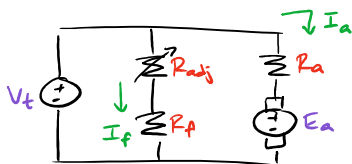"idling" → no mechanical load  
→ output mech. power,  $P_{out} = \emptyset$



$$I_f = \frac{V_t}{R_{adj} + R_f} = \frac{240 \text{ V}}{175 + 100 \Omega} = 0.87 \text{ A}$$

converted power → output power =  $\emptyset$   
 $P_{conv} = E_a I_a = P_{rot} + P_{out}$   
 rotational losses, friction etc.

KVL

$$V_t = I_a R_a + E_a$$

$$240 = I_a (0.4) + E_a$$

$$E_a I_a = P_{rot} = 1800 \text{ W}$$

$$I_a = 592 \text{ or } 7.59 \text{ A}$$

idling so very unlikely @ 592A

$$E_a = 237 \text{ V}$$

@ 1200 RPM  $\& I_f = 0.87 \text{ A} \rightarrow E_a^{1200} = 270 \text{ V}$   
 (from mag. characterization curve)

don't know velocity

$$\frac{E_a}{E_a^{1200}} = \frac{n}{1200} \rightarrow n = \frac{237}{270} \cdot 1200 = 1054 \text{ RPM}$$

↑ idling velocity

induced voltage  
 $\&$  RPM same ratio

Ex) SAME MOTOR AS ABOVE AT FULL LOAD, 15 HP  
 FIND VELOCITY  $\&$  SR%

=

$$I_f = 0.87 \text{ A}, E_a^{1200} = 270 \text{ V}$$

$$P_{conv} = E_a I_a = P_{rot} + P_{out} \rightarrow E_a I_a = 12990 \text{ W}$$

$$1800 \text{ W} + 15 \text{ hp} \times \frac{746 \text{ W}}{\text{hp}}$$

$$I_a = 540 \text{ A or } 60 \text{ A}$$

$$E_a = 24 \text{ V or } 216 \text{ V}$$

$$\text{KVL} \rightarrow V_t = I_a R_a + E_a \rightarrow 240 = 0.4 I_a + E_a$$

↑ last answer in the

ball-park

$$\frac{E_a^n}{E_a^{1200}} = \frac{n}{1200} \rightarrow n = \frac{216}{270} 1200 = 960 \text{ RPM}$$

↑ velocity @ full load

### SPEED REGULATION PARAMETER

how much load affects the speed

$$SR\% = \frac{\omega(\text{idling}) - \omega(\text{full-load})}{\omega(\text{full-load})}$$

$$SR\% = \frac{1054 - 960}{960} \times 100\% = 9.79\%$$

Ex) WHAT IS THE TORQUE AT FULL LOAD?


=

$$P_o = \tau_{\text{load}} \omega_{\text{mech}} \rightarrow \tau_{\text{load}} = \frac{P_o}{\omega_{\text{mech}}} = \frac{15 \text{ hp} \cdot 746 \frac{\text{W}}{\text{hp}}}{960 \text{ RPM} \cdot \frac{2\pi \text{ rad/s}}{60 \frac{\text{RPM}}{\text{rev}}}} = 111.3 \text{ Nm}$$

↑ at full load
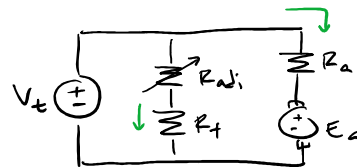
### Closer look @ $R_{adj}$

$$R_{adj} \uparrow \quad I_f \downarrow \quad I_a \uparrow \quad \text{RPM} \uparrow$$



Ex) WHAT HAPPENS IF WE INCREASE  $R_{adj}$  TO  $250\Omega$  FROM  $175\Omega$ ?

=

$$I_f = \frac{V_t}{R_{adj} + R_f} = \frac{240}{250 + 100} = 0.67 \text{ A}$$

$$\text{from curve} \rightarrow E_a = 247 \text{ V}$$

$$P_{\text{conv}} = E_a I_a = P_{\text{rot}} + P_{\text{out}}$$

$$\rightarrow E_a I_a = 1800 \text{ W} + 15 \text{ hp} (746) = 12990 \text{ W}$$

$$\text{KVL} \rightarrow 240 = 0.4 I_a + E_a$$

$$\rightarrow E_a = 24.1 \text{ V} \quad \text{or} \quad 216 \text{ V}$$

$$\rightarrow n = \frac{216}{247} 1200 = 1049 \text{ RPM}$$

↑ similar velocity as when idling w/  $175\Omega R_{adj}$

### ARMATURE REACTIONS

"this machine has compensation windings"

↳ i.e. windings cancel out armature reaction so neglect them

if not, consider the following:

$$\text{MMF}_f = N_f I_f + N_s I_s - K_{ar} I_a$$

↳ manufacturer usually divides everything by  $I_f$

take this  
value to  
curve

$$I_f^* = I_f + \frac{N_s}{N_f} I_s - \frac{K_{ar}}{N_f} I_a$$


manufacturer might say something like:

"the armature reaction MMF is given as  
 $K_{ar} I_a = 1200 \text{ A} @ I_a = 55 \text{ A}$ "

$$\rightarrow \text{ie. } K_{ar} = 21.8 \frac{\text{A}}{\text{A}}$$

↑ for every amp in armature  
there are 21.8 amps of  
magnetomotive force subtracted  
from MMF of field

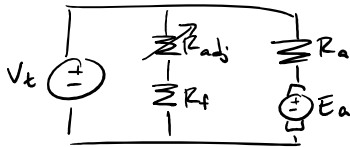Ex)  $K_{ar} = 21.8 \text{ A/A}$ ,  $N_f = 2700$ ,  $N_s = 20$ ,  $R_{ad} = 175 \Omega$   
everything same as above except ARMATURE REACTION  
=



$$P_{\text{conv}} = E_a I_a = P_{\text{rot}} + P_{\text{out}}$$

$$E_a I_a = 12990 \text{ W}$$

$$240 = 0.4 I_a + E_a$$

not even close

$$E_a = 24.1 \text{ V or } 216 \text{ V}$$

$$I_a = 60.1 \text{ A}$$

$$I_f = \frac{240}{175 + 100} = 0.87 \text{ A}$$

$$I_f^* = I_f + \frac{N_s}{N_f} I_s - \frac{K_{ar}}{N_f} I_a \rightarrow I_f^* = I_f - \frac{21.8}{2700} I_a = 0.39 \text{ A}$$

no series  
coil  
connected

from curve

$$E_a^{1200} = 167 \text{ V}$$

$$n = \frac{E_a^n}{E_a^{1200}} 1200 = \frac{216}{167} 1200 = 1552 \text{ RPM}$$

↑ faster than idle

this machine accelerates w/ load  
and reaches S.S. of 1552 RPM

(negative SR%)

## LONG CUMULATIVE COIL

↳ series coil & shunt coil help  
each other create stronger mag. field

$$I_f^* = I_f + \frac{N_s}{N_f} I_s + \frac{K_{ar}}{N_f} I_a$$

↑ addition, not subtraction

as before

Ex)

A 100 hp 250 V cumulative compounded DC motor has an internal resistance, including the series winding, of 0.04 ohm. There are 1000 turns per pole on the shunt field and 3 turns per pole on the series winding. "Idling," the adjustable resistor has been adjusted to make the motor run at 1200 rpm. Neglect core, mech, and stray losses. No armature reaction!

$I_f$ (A)	1	2	3	4	5	6	7	8	9	10
$E_a$ (V)	65	130	180	220	250	265	275	283	287	289

- What is the idling shunt field current?
- Cumulative compounded, find rpm if  $I_a = 200A$
- Differentially compounded, rpm,  $I_a = 200A$

$$V_t = 250V$$

Because compounded

$$N_f = 1000$$


$$N_s = 3$$

$$P_{rot} = \phi \text{ loss}$$

$$P_{out} = \phi \text{ idling}$$

$$n = 1200 \text{ RPM}$$

$$R_a + R_s = 0.04 \Omega$$

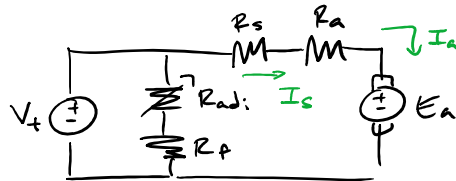

$$P_{conv} = P_{rot} + P_{out} = E_a I_a$$

$$\rightarrow E_a I_a = \phi$$

same because compounded

$$a) E_a = k \phi \omega \leftarrow \omega \neq \phi \nmid \phi \neq \phi \therefore E_a \neq \phi \therefore \underline{I_a = \phi} \nmid \underline{I_s = \phi}$$

$$\rightarrow \therefore E_a = V_t \text{ because if } I_a = \phi, \text{ no drop across } R_s + R_a \text{ branch}$$

$$\underline{E_a = 250V}$$

Determine  $I_f^*$  from  $E_a$  & table (use interpolation if necessary)


$$@ 1200 \text{ RPM } \underline{I_f^* = 5A}$$

$$I_f^* = I_f + \frac{N_s}{N_f} I_s - \frac{K_{ar}}{N_f} I_a$$

$$I_s = I_a = \phi$$

$$\rightarrow I_f = I_f^* = \underline{5A}$$

b)

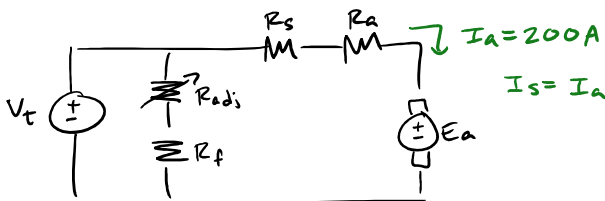

$$KVL \rightarrow V_t = I_a(R_s + R_a) + E_a$$

$$\rightarrow E_a = 250 - 200(0.04) = 242V$$

$$I_f^* = I_f + \frac{N_s}{N_f} I_s - \frac{K_{ar}}{N_f} I_a \quad \text{b/c problem says no armature reaction}$$

$$\rightarrow I_f^* = 5A + \frac{3}{1000} 200 = \underline{5.6A}$$

same as before

Determine  $I_f$  from table  $I_f^* = 5.6 \pm$  interpolation

Determine  $E_a$  from table using  $I_f^* = 5.6$  & interpolation

@ 1200 RPM  $E_a^{1200} = 262V$

$$\frac{E_a^n}{E_a^{1200}} = \frac{n}{1200} \rightarrow n = 1200 \frac{242}{262} = \boxed{1108 \text{ RPM}}$$

can calculate everything else,  $P_{out}$ ,  $\tau_{load}$  etc. from this.

# DC MOTOR WITH COMPOUND EXCITATION

