

Assignment 3 - DC Motors


Wednesday, February 17, 2016

3:43 PM

(10 pts)


A shunt DC motor is fed from a 225 V DC source. The field coil has a resistance of 222Ω . The total armature resistance (including the contact resistance of the brushes against the segments of the commutator) is 0.13Ω . The field adjustable resistor is set at 412Ω . The motor is rated for 25 hp. The motor has compensation windings.

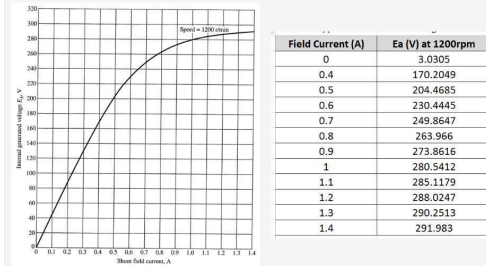Magnetization characteristic $E_a = f(I_f)$:



(a) What is the start up armature current? (A) A

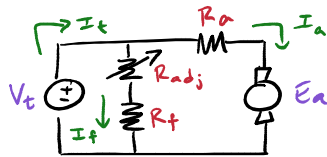(b) What is the start up torque, in $N \cdot m$? $N \cdot m$



$$\begin{aligned} R_a &= 0.13 \Omega \\ R_f &= 222 \Omega \\ R_{adj} &= 412 \Omega \\ V_t &= 225 \text{ V} \end{aligned}$$

@ start up $E_a = 0 \therefore$

$$I_a^{\text{start}} = \frac{V_t}{R_a} \rightarrow I_a^{\text{start}} = 1731 \text{ A}$$

$$I_f = \frac{V_t}{R_{adj} + R_f} \rightarrow I_f = 354.9 \text{ mA}$$

compensation windings $\therefore I_f^* = I_f \rightarrow E_a^{1200} = 145 \text{ V}$


$$E_a = k \phi \omega \rightarrow k \phi = \frac{E_a^{1200}}{1200 \frac{2\pi}{60}}$$

$$\tau = k \phi I_a \rightarrow \tau = \frac{145}{1200 \frac{2\pi}{60}} 1731 = 1997 \text{ Nm}$$

(10 pts)

A shunt DC motor is fed from a 190 V DC source, and let run idling (no mechanical load). The field coil has a resistance of 180Ω . The total armature resistance (including the contact resistance of the brushes against the segments of the commutator) is 0.19Ω . The field adjustable resistor is set at 468Ω . The total rotational losses have been measured at full load as 1800 W. The motor has compensation windings.

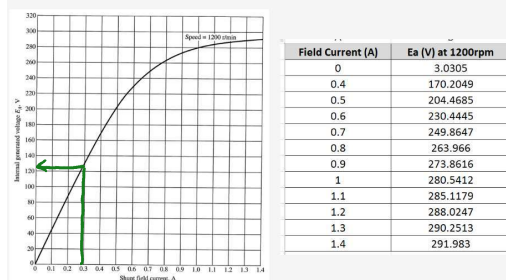Magnetization characteristic $E_a = f(I_f)$:



(c) What is the idling speed? RPM

(d) What is the terminal idling current, in amps? A

$$P_{\text{conv}} = I_a E_a \rightarrow 1800 = I_a E_a^*$$

$$E_a = V_t - I_a R_a \rightarrow E_a^h = 190 - I_a 0.19$$

$$\rightarrow E_a^h = 188.2, I_a = 9.565$$

$$I_f = \frac{V_t}{R_f + R_{adj}} \rightarrow I_f = 293 \text{ mA}$$

$$\rightarrow E_a^{1200} = 125 \text{ V}$$

$$\frac{E_a^h}{n} = \frac{E_a^{1200}}{1200}$$


$$\rightarrow n = \frac{1200 \cdot 188.2}{125} = \boxed{1807 \text{ RPM}}$$

$$I_t = I_a + I_f \rightarrow \boxed{I_t = 9.858 \text{ A}}$$

(10 pts)

A shunt DC motor is fed from a 173 V DC source. The field coil has a resistance of 204 Ω . The total armature resistance (including the contact resistance of the brushes against the segments of the commutator) is 0.19 Ω . The field adjusting resistor is set at 418 Ω . The motor is rated for 29 hp. The total rotational losses have been measured at full load as 900 W. The motor has compensation windings. You load this motor to its full capacity.

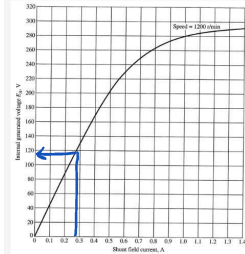Magnetization characteristic $E_a = f(I_f)$:



Field Current (A)	Ea (V) at 1200rpm
0	3.0305
0.4	170.2049
0.5	204.4685
0.6	230.4445
0.7	249.8647
0.8	263.966
0.9	273.8616
1	280.5412
1.1	285.1179
1.2	288.0247
1.3	290.2513
1.4	291.983

(e) What is the full load speed, in rpm? RPM

(f) What is the full load terminal current, in amps? A

(g) What is the speed regulation between idling and full load in percent? %

(p) What is the torque at the mechanical load, in N.m? N.m

$$P_{out} = 29 \text{ hp}, P_{rot} = 900 \text{ W}$$

$$P_{conv} = P_{out} + P_{rot} = E_a^h I_a$$

$$E_a^h = V_t - I_a R_a \quad \left. \begin{array}{l} E_a^h = 143.1 \text{ V} \\ I_a = 157.5 \text{ A} \end{array} \right\}$$

$$I_f = \frac{V_t}{R_{adj} + R_f} \rightarrow I_f = 278.1 \text{ mA}$$

$$\rightarrow E_a^{1200} = 119 \text{ V}$$

$$n_{full} = \frac{1200 \cdot 143.1}{119} = \boxed{1443 \text{ RPM}}$$

$$I_t = I_f + I_a \rightarrow \boxed{I_t = 147.8 \text{ A}}$$

$$\tau = \frac{E_a^h I_a}{n \frac{2\pi}{60}} \rightarrow \boxed{149.2 \text{ Nm}}$$

@ idling $P_{out} = 0 \therefore P_{conv} = 900$

$$\left. \begin{array}{l} E_a^{idling} I_a = 900 \\ E_a^{idling} = 173 - I_a 0.19 \end{array} \right\} \quad \left. \begin{array}{l} I_a = 5.232 \text{ A} \\ E_a^{idling} = 172 \text{ V} \end{array} \right\}$$


$$n_{idling} = \frac{1200(172)}{119} = 1734 \text{ RPM}$$

$$\%SR = \frac{n_{idling} - n_{load}}{n_{load}} 100 = \boxed{20\%}$$

(10 pts)

A shunt DC motor is fed from a 289 V DC source, and let run idling (no mechanical load). The field coil has a resistance of 242Ω . The total armature resistance (including the contact resistance of the brushes against the segments of the commutator) is 0.2Ω . The field adjusting resistor is set at 326Ω . The motor is rated for 12 hp. The total rotational losses have been measured at full load as 1300 W . The motor has compensation winding. 281.722 0.508803 207.485 1629.36 289 242 326 568

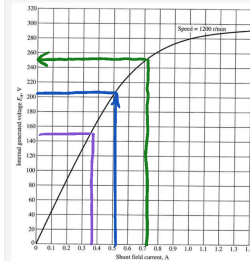Magnetization characteristic $E_a = f(I_f)$:



Field Current (A)	Ea (V) at 1200rpm
0	5.0305
0.4	170.2049
0.5	204.4685
0.6	230.4445
0.7	249.8647
0.8	263.966
0.9	273.8616
1	280.5412
1.1	285.1179
1.2	288.0247
1.3	290.2513
1.4	291.983

(h) What is the full load speed, in rpm? RPM

If the field adjustable resistor can be set at any value between 80Ω and 480Ω ,

(i) What is the maximum speed, in rpm, of the motor at full load. RPM

(j) What is the minimum speed, in rpm, of the motor at full load. RPM

(k) What is the maximum speed, in rpm, idling. RPM

(l) What is the minimum speed, in rpm, idling. RPM

$$1300 + 12(746) = I_a E_a^* \\ E_a^* = 289 - I_a(0.2)$$

$$E_a^* = 281.7 \text{ V}$$

$$I_a = 36.39 \text{ A}$$

$$I_f = \frac{289}{326 + 242} = 508.8 \text{ mA} \\ \rightarrow E_a^{1200} = 205 \text{ V}$$

$$n = \frac{1200 \cdot E_a^*}{E_a^{1200}} \rightarrow n = \boxed{1649 \text{ RPM}}$$

$$\text{full load } \therefore P_{conv} = 1300 + 12(746)$$

$$\rightarrow E_a^* = 281.7 \text{ V}$$

$$R_{adj} \uparrow n \uparrow \therefore n_{max} @ R_f = 480 \Omega$$

$$\rightarrow I_f = \frac{289}{242 + 480} = 400 \text{ mA} \rightarrow E_a^{1200} = 170 \text{ V}$$

$$n_{max} = \frac{1200 \cdot 281.7}{170} = \boxed{1988 \text{ RPM}}$$

$$n_{min} @ R_f = 80 \Omega$$

$$I_f = \frac{289}{242 + 80} = 898 \text{ mA} \rightarrow E_a^{1200} = 275 \text{ V}$$

$$n_{min} = \frac{1200(281.7)}{275} = \boxed{1229 \text{ RPM}}$$

$$\text{idling } \therefore P_{out} = 0 \therefore P_{conv} = 1300$$

$$\left. \begin{aligned} 1300 &= I_a E_a^* \\ E_a^* &= 289 - I_a(0.2) \end{aligned} \right\} \begin{aligned} E_a^* &= 288.1 \text{ V} \\ I_a &= 4.512 \text{ A} \end{aligned}$$

$$\therefore 1200 \cdot 288.1$$

$$E_a^n = 289 - I_a(0.2) \quad \left\{ \begin{array}{l} E_a = 288.1 \text{ V} \\ I_a = 4.512 \text{ A} \end{array} \right.$$


$$n_{\max} = \frac{1200 \cdot 288.1}{170} = \boxed{2034 \text{ RPM}}$$

$$n_{\min} = \frac{1200 \cdot 288.1}{275} = \boxed{1257 \text{ RPM}}$$

(10 pts)

A shunt DC motor is fed from a 212 V DC source. The field coil has a resistance of 234 Ω . The total armature resistance (including the contact resistance of the brushes against the segments of the commutator) is 0.23 Ω . The field adjustable resistor is set at 105 Ω . The motor is rated for 14 hp. The total rotational losses have been measured at full load as 1050 W. The motor has compensation windings that can be deactivated (academic). When the compensation windings are deactivated, the armature reaction is 550 A when the armature current is 102 A. The field coil has $N_f = 2950$ turns per pole. Compute both with and without compensation winding, the full load speed in rpm.

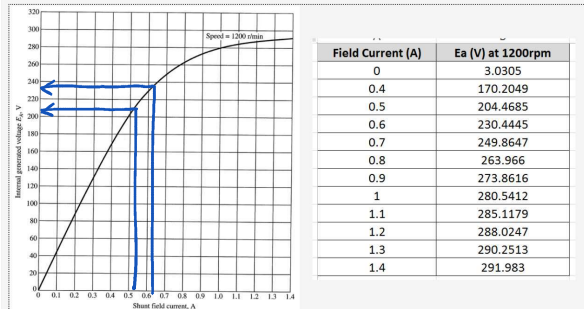Magnetization characteristic $E_a = f(I_f)$:



(h) With compensation winding, what is the full load speed, in rpm? RPM

(x) Without compensation winding, what is the full load speed, in rpm? RPM

$$\begin{aligned} 14(746) + 1050 &= E_a^n I_a \\ E_a^n &= 212 - I_a(0.23) \end{aligned} \quad \left\{ \begin{array}{l} E_a^n = 198.7 \\ I_a = 57.85 \end{array} \right.$$

$$I_f = \frac{212}{105 + 234} = 625 \text{ mA}$$

$$\rightarrow E_a^{1200} = 235 \text{ V}$$

$$n = \frac{1200 \cdot 198.7}{235} = \boxed{1015 \text{ RPM}}$$

with compensation windings

$$I_f^* = I_f - \frac{\text{MMF}}{N_f} I_a$$

$$\rightarrow I_f^* = 625 \text{ mA} - \frac{350}{2950} 57.85 = 520 \text{ mA}$$


$$\rightarrow E_a^{1200} = 205 \text{ V}$$

$$n = \frac{1200 \cdot 198.7}{205} = \boxed{1163 \text{ RPM}}$$

(20 pts)


A long compound DC motor is fed from a 287 V DC source and its draining 19 A off the external DC source. The field coil has a resistance of 144Ω . The total armature resistance (including the contact resistance of the brushes against the segments of the commutator) is 0.27Ω . The field adjustable resistor is set at 139Ω . The motor is rated for 21 hp. The total rotational losses have been measured at full load as 1000 W. The motor has compensation windings. The field coil has $N_f = 3000$ turns per pole, and the series coil has $N_s = 23$ turns per pole and $R_s = 0.03 \Omega$.

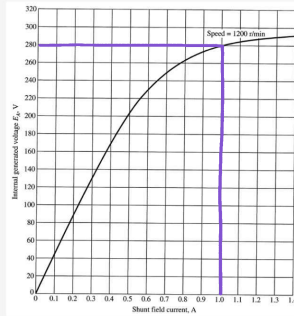Magnetization characteristic $E_a = f(I_f)$:



Field Current (A)	Ea (V) at 1200rpm
0	3.0305
0.4	170.2049
0.5	204.4685
0.6	230.4445
0.7	249.8647
0.8	263.966
0.9	273.8616
1	280.5412
1.1	285.1179
1.2	288.0247
1.3	290.2513
1.4	291.983

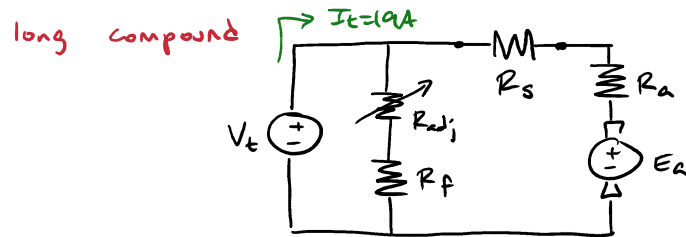- (a) What is the speed, in rpm? RPM
- (b) What is the output torque, in N.m? N.m
- (c) What is the current of the external source when the motor is fully loaded, in amps? A
- (d) At full load, what is the speed, in rpm? RPM



$$I_f = \frac{V_t}{R_{adj} + R_f} \rightarrow I_f = 1.014 \text{ A}$$

$$I_a = I_t - I_f \rightarrow I_a = 17.99 \text{ A} \quad \text{when } I_t \text{ measured}$$

$$E_a^n = V_t - I_a(R_a + R_s) \rightarrow E_a^n = 281.6 \text{ V} \quad @ 19 \text{ A}$$

$$I_f^* = I_f + I_s \frac{N_s}{N_f} \rightarrow I_f^* = 1.152$$

$$\hookrightarrow E_a^{1200} = 286.6 \text{ V}$$

$$n = \frac{1200 E_a^n}{E_a^{1200}} \rightarrow n = \frac{1200 \cdot 281.6}{286.6} = \boxed{1179 \text{ RPM}}$$

$$\tau = \frac{E_a^n I_a - P_{rot}}{n \frac{2\pi}{60}} \rightarrow \tau = \frac{281.6 (17.99) - 1000}{1179 \frac{2\pi}{60}} = \boxed{34 \text{ Nm}}$$

when @ full load, $P_{conv} = 21(746) + 1000$

$$21(746) + 1000 = I_a E_a^n \quad \left. \begin{array}{l} E_a^n = 269.6 \\ I_a = 58.12 \end{array} \right\}$$

$$E_a^n = 287 - I_a(0.27 + 0.03)$$

$$I_t = I_a + I_f \rightarrow I_t = 58.12 + \frac{287}{144 + 139} = \boxed{63.12 \text{ A}}$$

$$\hookrightarrow I_f = 1.014 \text{ A} \rightarrow E_a^{1200} = 280 \text{ V}$$




$$\hookrightarrow I_f = 1.014 \text{ A} \rightarrow E_a^{1200} = 280 \text{ V}$$




(10 pts)

An independently excited DC motor whose armature is energized by an external DC source V_t , has its field excitation circuit independently energized by another DC voltage source $V_f = 273 \text{ V}$. The field adjustable resistor R_{adj} is set at 182Ω . The field coil has a resistance $R_f = 202 \Omega$. The armature resistance is $R_a = 0.03 \Omega$.

DC motor with independent excitation:

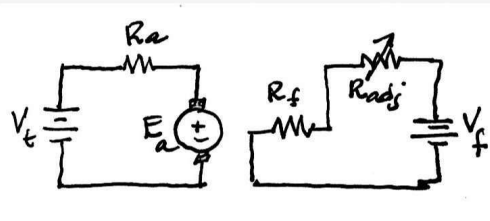

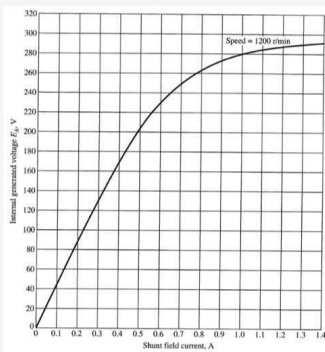Magnetization characteristic $E_a = f(I_f)$:



Field Current (A)	E_a (V) at 1200rpm
0	3.0305
0.4	170.2049
0.5	204.4685
0.6	230.4445
0.7	249.8647
0.8	263.966
0.9	273.8616
1	280.5412
1.1	285.1179
1.2	288.0247
1.3	290.2513
1.4	291.983

What is the idling speed, in rpm, of the motor when ...

(a) For $V_t = 231 \text{ V}$ $n_{idle} = ? \text{ RPM}$

(b) For $V_t = 288 \text{ V}$ $n_{idle} = \text{ } \text{RPM}$

(c) For $V_t = 287 \text{ V}$ $n_{idle} = \text{ } \text{RPM}$

$$I_f = \frac{V_f}{R_f + R_{adj}}$$

$$\hookrightarrow I_f = 1.014 \text{ A} \rightarrow E_a^{1200} = 280 \text{ V}$$

$$\text{assuming } I_a = \phi \rightarrow E_a^n = V_t$$

$$V_t = 231 \quad n = \frac{1200}{280} \cdot 231 = 1109 \text{ RPM}$$

$$V_t = 288 \quad n = \frac{1200}{280} \cdot 288 = 1382 \text{ RPM}$$

$$V_t = 287 \quad n = 1378 \text{ RPM}$$

(10 pts)

A series DC motor is connected to a DC source of 236 V and its rated current is 61 A. It has a series coil with 37 turns per pole and $R_s = 0.02 \Omega$. Its armature resistance is 0.03Ω . The magnetization curve, measured at 900 rpm, and expressed in terms of E_a versus magnetomotive force in amps, is given by the following table (to use this "curve", please use linear interpolation). Armature reaction is negligible in this machine. Neglect rotational losses.

Figure:

$E_a (V)$	95	150	188	212	229	243
$MMF (A)$	500	1,000	1,500	2,000	2,500	3,000

With the motor loaded so that its current is half the rated armature current, compute its torque and speed


(a) $T_{50\%} = \text{ } N.m$

(b) $n_{50\%} = \text{ } rpm$

Now repeat the problem but with the motor draining full rated current

(c) $T_{100\%} = \text{ } N.m$

(d) $n_{100\%} = \text{ } rpm$

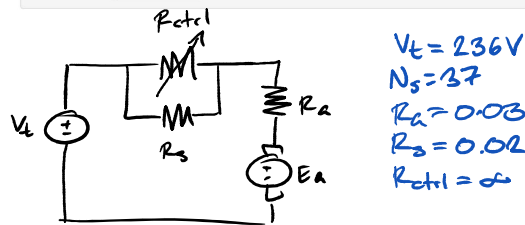

$$I_t = I_a \quad E_a = V_t - (R_s + R_a) I_a$$

$$@ I_t = \frac{1}{2} 61 \rightarrow E_a^h = 234.5V$$

$$MMF = N_s I_s \rightarrow MMF = 37 \left(\frac{1}{2} 61 \right) = 1129A$$

↳ from graph interpolation $E_a^{900} = 159.8V$

$$n = \frac{900 \cdot E_a^h}{E_a^{900}} \rightarrow \boxed{n = 1321 RPM}$$

$$\tau = \frac{E_a^h I_a}{n \frac{2\pi}{60}} \rightarrow \boxed{\tau = 51.7 Nm}$$

$$@ I_t = 61 \rightarrow E_a^h = 233V$$

$$MMF = 2267 \rightarrow E_a^{900} = 220.7V$$

$$n = \frac{900(233)}{220.7} = \boxed{950.2 RPM}$$

$$\tau = \frac{233(61)}{950.2 \frac{2\pi}{60}} = \boxed{142.8 Nm}$$


(10 pts)

For the DC motor in the figure below, draw (these drawings may be asked in an exam, but are not for you to submit as part of this assignment; however, keep reading) an external DC power supply of 275 Vdc feeding this motor that has been connected (a) as a simple shunt motor with a field "adjustable" resistor of 100 ohms, no compensation winding; (b) as a series motor with a "controlling" resistor of 0.12 ohms (the one in parallel with the series coil), no compensation windings; (c) as a cumulative compounded long connection DC motor without compensation winding and a shunt field coil adjustable resistor of 100 ohms; (d) as a differential compounded short connection DC motor with compensation windings and a shunt field coil adjustable resistor of 100 ohms.


For every part above, produce three diagrams: a circuit diagram like the ones we used to solve numerical problems; a global view connection diagram (which in nothing but Figure 1 with the wires, adjustable resistor and external power supply); and a true wiring diagram (with the connection box on the right representing the actual motor, with the wires, adjustable resistor and external power supply).

If we know that $N_f = 2100$ turns per pole, $N_s = 23$ turns per pole, $R_f = 178$ ohms, $R_s = 0.03$ ohms, $R_a = 0.26$ ohms, $R_{comp} = 0.027$ ohms (compensation winding resistance), $MMF_{Ar} = 1360$ A when $I_a = 78$ A. The magnetization characteristic of this motor, measured at 1200 rpm, as $E_a(V)$ as a function of $I_f^*(A)$ is shown below. The current taken by the motor from the external source is 37 A. For each part above, what are the RPM and output torque. If the rotational losses are negligible. Note: In a short compound, the field coil circuit (R_{adj} plus R_f) are connected directly to the armature terminals.

The DC machine and its connection box:

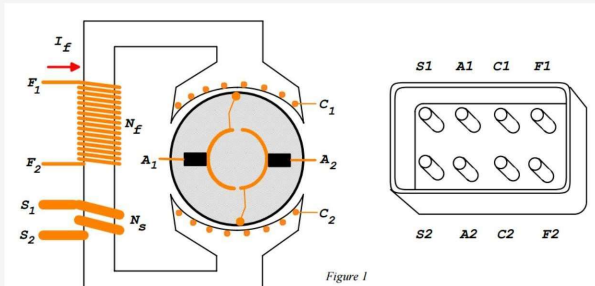

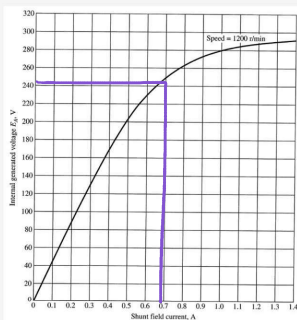Magnetization characteristic $E_a = f(I_f^*)$:



Field Current (A)	E_a (V) at 1200rpm
0	3.0305
0.4	170.2049
0.5	204.4685
0.6	230.4445
0.7	249.8647
0.8	263.966
0.9	273.8616
1	280.5412
1.1	285.1179
1.2	288.0247
1.3	290.2513
1.4	291.983

(a) For the shunt motor:

$n =$ RPM and Torque = N.m

(b) For the series motor:

$n =$ RPM and Torque = N.m

(c) For the cumulative compounded motor:

$n =$ RPM and Torque = N.m

(d) For the differential compounded motor:

$n =$ RPM and Torque = N.m


$MMF = 1360A$ $I_{Ar} = 78A$
 $V_t = 275V$ $I_t = 37A$ $P_{rot} = \phi$
 $R_f = 178$ $R_s = 0.03$ $R_a = 0.26$ $R_{comp} = 0.027$
 $N_f = 2100$ $N_s = 23$

SHUNT $R_{adj} = 100$ no compen windings

$$I_f = \frac{275}{100 + 178} = 989 \mu A$$

$$I_f^* = I_f - \frac{1360}{2100} I_a = 690 \mu A$$

$$\rightarrow E_a^{1200} = 247.9V$$

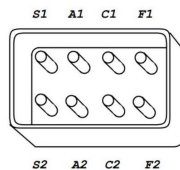

$$I_a = 37 - I_f = 36.01 \text{ A}$$

$$E_a^n = 275 - I_a(R_a) = 263.6 \text{ V}$$

$$n = \frac{1200(263.6)}{2\pi \cdot 7.9} = \boxed{1286 \text{ RPM}}$$

$$\tau = \frac{263.6(36.01)}{\frac{2\pi}{60}} = \boxed{71 \text{ Nm}}$$

SERIES $R_{ctrl} = 0.12$ no compen. windings

$$I_a = I_t = 37 \text{ A}$$

$$R_{eq} = (R_{ctrl} // R_s) + R_a = 0.284 \Omega$$

$$E_a^n = 275 - 37 R_{eq} = 264.5 \text{ V}$$

$$I_s = \frac{I_a R_{ctrl}}{R_s + R_{ctrl}} = 29.6 \text{ A}$$

$$I_f^* = I_f + \frac{N_s}{N_f} I_s - \frac{\text{MMF}}{N_f} I_a = 324.2 \text{ mA}$$

$$\rightarrow E_a^{1200} = 138.5 \text{ V}$$

$$n = \frac{1200 \cdot 264.5}{138.5} = \boxed{2292 \text{ RPM}}$$

$$\tau = \frac{264.5(37)}{2292 \frac{2\pi}{60}} = \boxed{40.78 \text{ Nm}}$$

LONG COMPUND $R_{adj} = 100$ $R_{ctrl} = 0.12$

$$I_f = \frac{275}{100 + 128} = 187.2 \text{ mA}$$

$$I_a = 36.01 \quad I_s = I_a \frac{R_{ctrl}}{R_s + R_{ctrl}} = 28.81$$

$$R_{eq} = 0.317 \Omega \rightarrow E_a^n = 263.6 \text{ V}$$

$$I_f^* = 1.006 \rightarrow E_a^{1200} = 280 \text{ V}$$

$$n = \frac{1200 \cdot 263.6}{280} = \boxed{1131 \text{ RPM}}$$

$$\boxed{\tau = 80.24 \text{ Nm}}$$

DIFFERENTIAL SHORT CMP

$R_{adj} = 100$, $R_{ctrl} = 0.12$ are comp. windings

$$\begin{aligned} V_i &= V_t - I_t(R_{ctrl} // R_s) \\ E_a &= V_i - I_a(R_a + R_{comp}) \\ I_f &= \frac{V_i}{R_{adj} + R_f} \quad I_a = I_t - I_f \end{aligned}$$

$$\begin{aligned} V_f &= 286.5 \\ I_f &= 1.013 \text{ A} \\ I_a &= 33.99 \\ E_a^n &= 276.8 \text{ V} \end{aligned}$$

$$I_s = I_t \frac{R_{ctr1}}{R_a + R_{ctr1}} = 17.53 \text{ A}$$

$$\omega \quad I_f^* = 937.7 \text{ mA} \rightarrow E_a^{1200} = 276.4$$

$$\omega \quad I_f^* = 669 \text{ mA} \rightarrow E_a^{1200} = 243.8$$

$$n = 1202$$

$$n = \frac{1200 E_a^n}{E_a^{1200}} = 1362 \text{ RPM}$$

(-) $\nabla \phi$


$$I_f^* = 878.2 \text{ mA} \rightarrow E_a^{1200} = 271.7$$

$$\rightarrow n = 1223$$

(10 pts)

An independently excited DC motor whose armature is energized by an external DC source V_t that can range between 130 V and 210 V. Its field excitation circuit is independently energized by another DC voltage source $V_f = 275 \text{ V}$. The field adjustable resistor R_{adj} can range between 76Ω and 499Ω . The resistance of the field coil is $R_f = 116 \Omega$.

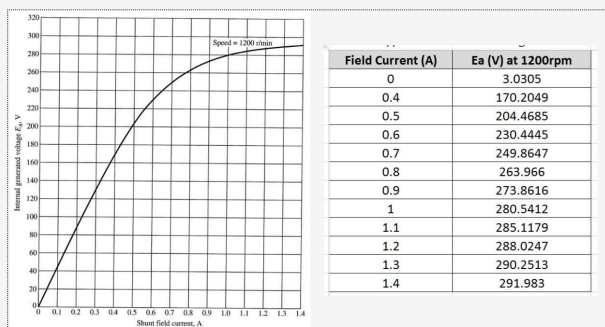
Magnetization characteristic $E_a = f(I_f)$:



What is the maximum and minimum idling speed that this motor can attain by varying V_t and R_{adj} ...

(a) $n_{max} =$ RPM

(b) $n_{min} =$ RPM

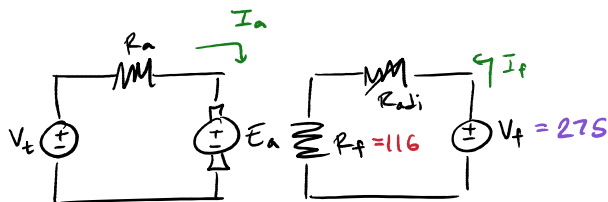

$$R_{adj} = 76 \rightarrow 499 \Omega \quad I_f = \frac{V_f}{R_f + R_{adj}}$$

$$@ R_{adj} = 76 \Omega \quad I_f = 1.4323 \text{ A} \quad E_a^{1200} = 291.983 \text{ V}$$

$$@ R_{adj} = 499 \Omega \quad I_f = 447.15 \text{ mA} \quad E_a^{1200} = 187.15 \text{ V}$$

assuming $I_a = \phi$, $V_t = E_a^n$

$$V_t = 130 \rightarrow 210 \text{ V}$$

$$\frac{E_a^n}{1200} \rightarrow n = 1200 \frac{E_a^n}{E_a^{1200}}$$

$$\frac{E_a^n}{E_a^{1200}} \rightarrow n = 1200 \frac{E_a^n}{E_a^{1200}}$$

$$76\Omega \quad 130V \quad n = 1200 \frac{130}{291.983} = 534.277$$

$$76\Omega \quad 210V \quad n = 1200 \frac{210}{291.983} = 863.0659$$

$$499\Omega \quad 130V \quad n = 1200 \frac{130}{187.15} = 833.5559$$

$$499\Omega \quad 210V \quad n = 1200 \frac{210}{187.15} = 1346.5135$$