

Address Decoding Techniques

What is Address Decoding ?

- **Address decoding** is a simple process that attempts to 'map' a memory device to a **particular range of CPU addresses**, that is, the memory device will respond to the CPU if the CPU issues an address within the designated range for the device.
- Address decoding allows us to **partition** the memory space of the CPU into smaller block that can then be designated as areas for **Sram**, **Dram**, **Flash** etc. and even memory mapped **IO** devices that respond like memory.
- The same techniques allow us to break up a section of say Sram into smaller sections allocated to individual Sram chips.
- For example, in a 68000 system, which has an address space of **8M Words** (**16M bytes**), address decoding might be used to create a **256k word** Partition of Sram allocated to the address range [**04 0000 – 07 FFFF**].

This in turn could be further broken down into 4 smaller blocks/banks of **64k words** [**04 0000 – 04 FFFF**], [**07 0000 – 07 FFFF**] and then constructed from **4 x 64kword** memory chips to occupy the full 256k word address range.

- **Designing an Address decoder** is a straightforward **combinatorial design problem**, where the circuit produces **Chip Select** signals to enable individual memory devices whenever the CPU issues an address corresponding to that chosen for the device.


Address Decoding Techniques

- Decoding memory addresses is analogous to decoding telephone numbers
 - The **telephone exchange** is analogous to our **address decoder**.
 - Each telephone number must be **unique** (within its **domain**)
 - We use the telephone number to uniquely **address individual phones**.
- For example dialling the number **001 604 123 4567** will cause the telephone exchange to map the digits **001** to **Canada**, the digits **604** to say the city of **Vancouver** the digits **123** to a **suburb of Vancouver** and the digits **4567** to a **unique phone** within the suburb. In other words
 - The **first 3 digits** of the phone number partition the global phone space into a **country**.
 - The **next 3 digits** partition the country phone space into a **city** or **region**.
 - The **next 3 digits** partition the city/region phone space into a **suburb**.
 - Finally the remaining **4 digits** partition the suburb space into unique phones with the numbers in the range **0000 - 9999**.
- There are lots of **design issues**, **trade offs** and **technologies** that we can use to solve this problem.

Address Decoding Techniques

- In a computer system the same principles of **separating/partitioning** into domains occurs.
- In particular, we decode/partition the CPU's **total address space** such that
 - **Part of the address** issued by the CPU (*usually signified by the **higher order address lines***) is used to partition the total memory space of the CPU into areas of say **Sram, Dram, Flash** or **Memory Mapped Peripherals**.
 - Within each partition, an additional **sub-set** of the **remaining address lines** may be further decoded to select individual **Banks** of memory chips within that **partition**, e.g. to partition the Sram area into **4 blocks** of **64k Words** each.
 - Finally whatever address bits are then **left** are **decoded** internally by the memory chip itself to **select memory locations or registers within the chip**.

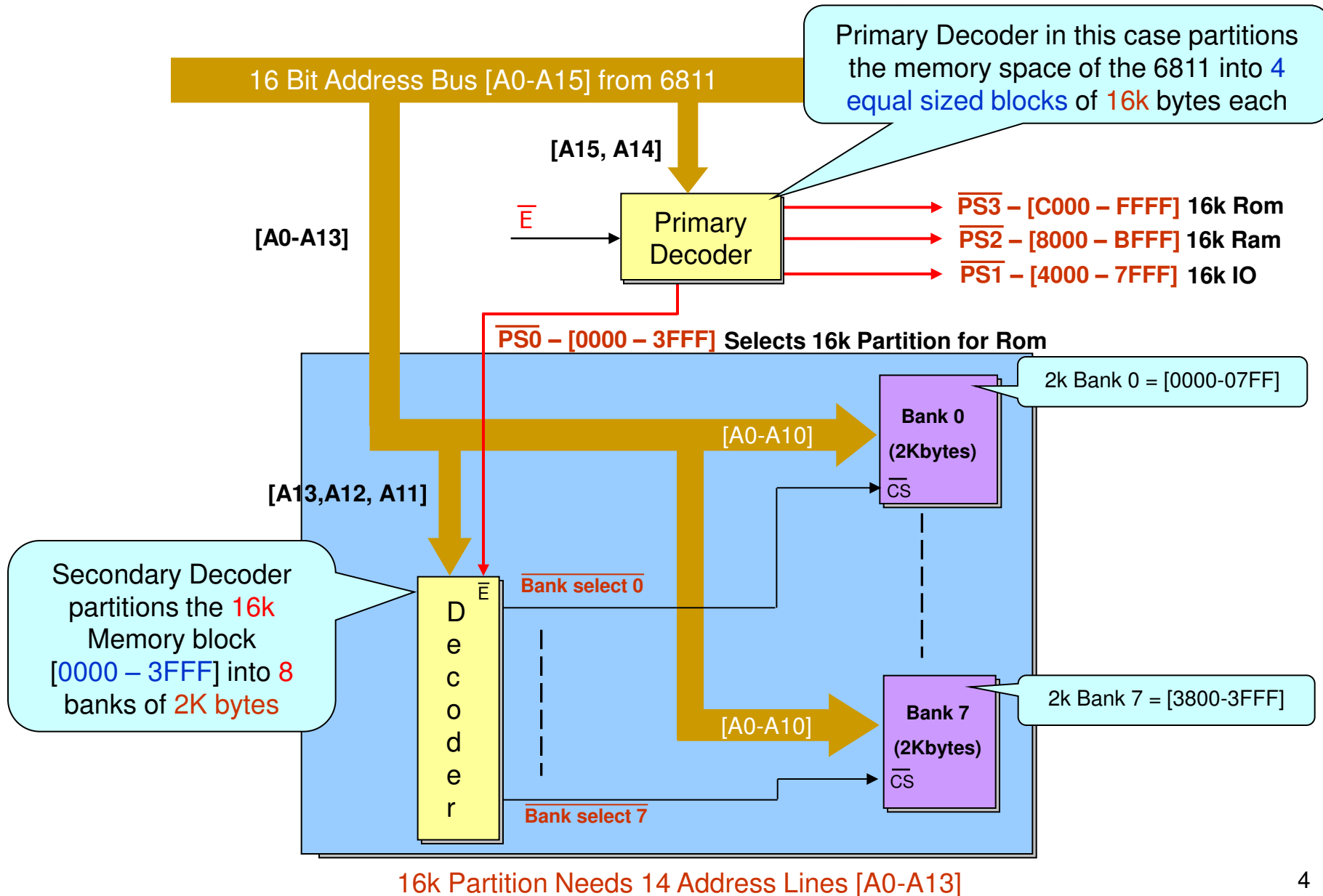
Example Partitioning of 6811's 64k Memory Space



Address Decoding Techniques

Designing a Memory Map

- Memory systems are usually **partitioned** into blocks of **Rom**, **Ram** and **Peripherals**. (see *opposite*)
- The only constraint that most CPUs impose on the designer is that there should be some **Rom** at say location **0** upwards to hold the **reset exception vector** table and **Boot code**
- Everything else is '**user definable**'. No single memory map is necessarily **any better** than any other, they are just different.
- Some maps are **designed to have holes in them to allow for expansion**, some are designed with **economy in mind**, i.e. to use the **minimum amount of logic** etc. and some are just random !!

 


68000 Memory Map
Partitioned into 3 Blocks
or Rom, Ram, and
Peripherals

Address Decoding Techniques

- Design an address decoder for a 68000 system with memory devices arranged as follows:

- 2K Word Block of Rom: M1
 - 2K Word Block of Ram: M2
- Each block will need 11 address lines connected to the lowest address lines issued by the CPU: A1-A11.
- Our task is to design the decoder that will generate the chip selects (CS1* and CS2*) for each block so that only one block responds to each address.
- We get to choose where to position the block in the memory map. That is, what range of CPU addresses the block responds to.

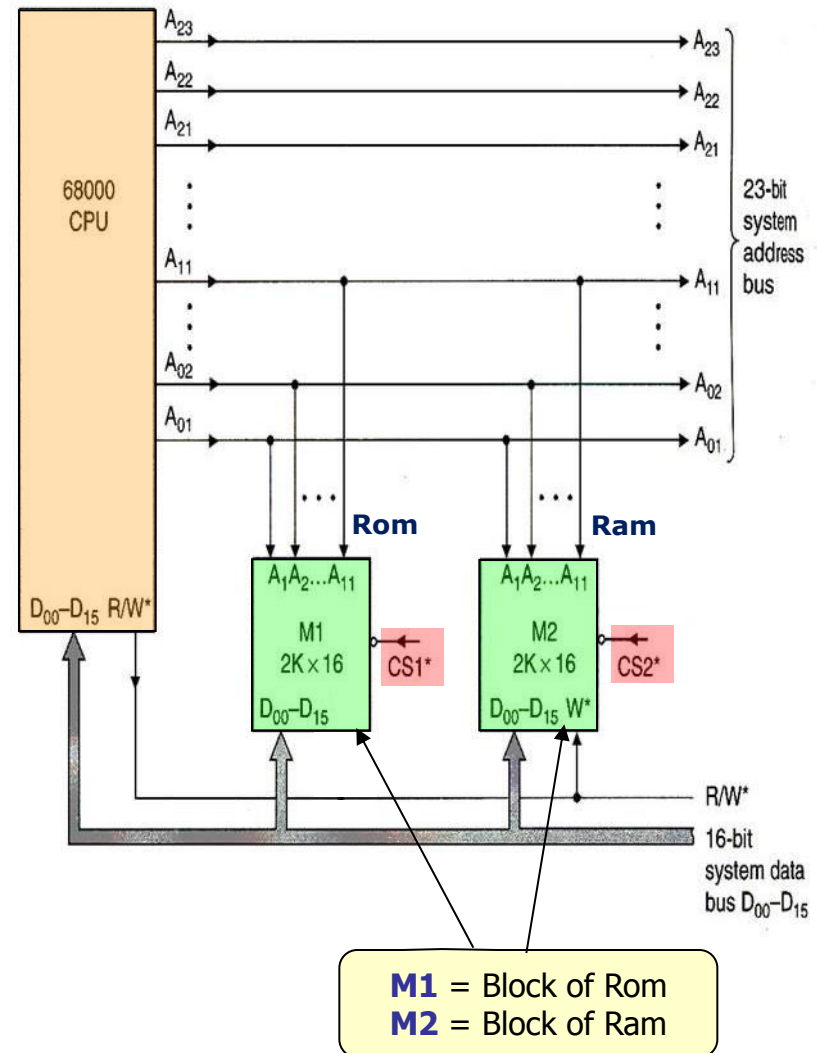

Full Address Decoding


Address Decoding Techniques

- A system employs Full address decoding, when the decoder circuit utilises all the **unused address lines** that are not directly connected to the memory chips.
- In our previous example, a full address decoder would decode **A12-A23** (*for original 68000, A12-A31 for soft core 68000 used in 465*).
- Let's design a decoder to place :-

- Rom (M1) at address [00 0000 – 00 0FFF]
- Ram (M2) at address [00 1000 – 00 1FFF]

- This arrangement will give us a total of **4KWords** of contiguous memory with no **gaps** and no **overlaps** and thus the memory map will look like that shown opposite.

Memory Map

 

Address Decoding Techniques

How do we design the circuit to realise this map?

- **Step1:** Create an **address table** with all CPU address lines listed as **columns**. In the case of the (*original*) 68000 this will be **A23-A1**.
- **Step 2:** Create a **Row entry** for each memory block that you are designing a **chip-select** signal for: **M1** and **M2**.
- **Step 3:** Decide how many of the CPU address lines will connect directly to the memory blocks and place an '**X**' meaning "**don't care**" under those address lines in the table because these address lines will be decoded by the memory chips/blocks themselves.


Because we are using **2K word** addresses, each Rom/Ram block will utilise **11** addresses lines ($2^{11} = 2048$), this leaves **A12-A23** to be decoded.

Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	
M1													x	x	x	x	x	x	x	x	x	x	x	Rom [000000-000FFF]
M2													x	x	x	x	x	x	x	x	x	x	x	Ram [001000-001FFF]

Note no A0

Address Decoding Techniques

- **Step 4:** Use the **remaining** address bits in the table to chose the combination of **0's** and **1's** on the address lines that will **select** the device at the locations required, taking care to make sure **no two devices** ever respond to the same address.
- Our full address decoder design thus decodes [**A12-A23**]
- Notice how a difference in **A12** is what effectively differentiates an address intended for **M1**, from **M2**. Thus
M1 is addressed when [**A23 - A13**] = **0** and [**A12**] = **0**
M2 is addressed when [**A23 - A13**] = **0** and [**A12**] = **1**
- These combinations of **address lines** are **mutually exclusive conditions** thus only one device can be selected at a time.



Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1		
M1	0	0	0	0	0	0	0	0	0	0	0	0	x	x	x	x	x	x	x	x	x	x	x	x	Rom[000000-000FFF]
M2	0	0	0	0	0	0	0	0	0	0	0	1	x	x	x	x	x	x	x	x	x	x	x	x	Ram[001000-001FFF]

Note no A0


$$M1 = A_{23} + A_{22} + A_{21} + \dots + A_{12}$$

$$M2 = A_{23} + A_{22} + A_{21} + \dots + (!A_{12})$$

Active low 'memory select' signals

Address Decoding Techniques

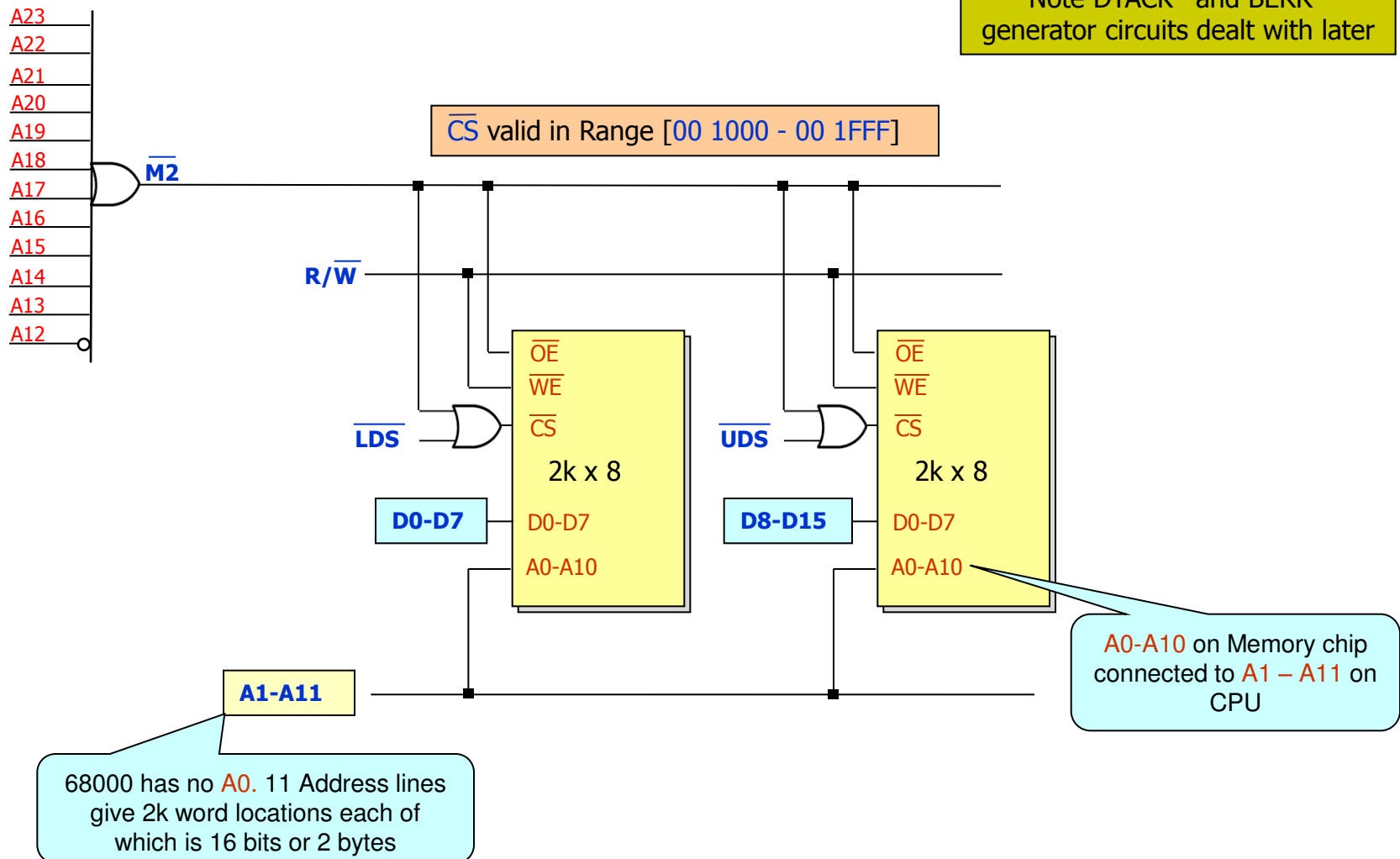Note DTACK* and BERR* generator circuits dealt with later



Two 2k byte devices working in parallel to give 2k words (or 4K bytes)

Address Decoding Techniques

A More Practical Example

- A 68000 system requires the following arrangement of Rom, Ram and Peripheral chips:
 - 10K word block of Rom arranged as
 - 2K words (Rom1)
 - 8K words (Rom2)
 - 2K word block of Ram (Ram1)
 - 2 Individual words for Peripheral 1 (Peri1)
 - 2 Individual words for Peripheral 2 (Peri2)
- You are free to assign the blocks any addresses you like with the exception of Rom1 which must reside at a base addresses of 0.
- Design a full address decoder to realise this memory map.

Address Decoding Techniques

- **Step 1:** Map each chip to an **address space** in the memory map of the system. The only constraint here is that **Rom1** should reside at **base address 0**. The allocation of other block addresses is fairly arbitrary so the memory map below has been chosen.

➤ Rom1 = [00 0000 - 00 0FFF]	2 K Words	(4 Kbyte range)
➤ Ram1 = [00 1000 - 00 1FFF]	2 K Words	(4 Kbyte range)
➤ Rom2 = [00 4000 - 00 7FFF]	8 K Words	(16 Kbyte range)
➤ Peri1 = [00 8000 - 00 8003]	2 Words	(4 byte range)
➤ Peri2 = [00 8004 - 00 8007]	2 Words	(4 byte range)

- These addresses were carefully chosen so that there is no **overlap** or **sharing** of addresses between the blocks. Many other memory maps could have been chosen.
- For example, **Rom2** could have been chosen to be **contiguous** with Rom 1 i.e. from address [00 1000 - 00 8FFF] but it wasn't because the decoder for an 8k block is easier to design if we assign the block a start address corresponding to that of a natural **8k boundary** in the memory (*we would need 4 separate 2k decoders OR'd together if we made Rom2 sit in a 2k boundary*). This is why **Rom2** was chosen to start at address [00 4000].

- **Step 2:** Decide how many Address lines each block will require governed by its size

Rom1 is a 2K word block requiring 11 address lines (i.e. $2^{11} = 2048$).

Ram1 is also a 2K word block also requiring 11 address lines.

Rom2 is an 8K word block requiring 13 address lines (i.e. $2^{13} = 8192$).

Peri1 is a 2 word peripheral requiring 1 address line.

Peri2 is a 2 word peripheral requiring 1 address line.

Address Decoding Techniques

- **Step 3:** Create an **address table** for your memory map. Place an 'x' in the row entry for each chip beneath the address lines that connect directly to the chip.

Note no A0, LDS* and UDS* select individual bytes within a word

Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	
000000-000FFF	0	0	0	0	0	0	0	0	0	0	0	0	x	x	x	x	x	x	x	x	x	x	x	Rom1
001000-001FFF	0	0	0	0	0	0	0	0	0	0	0	1	x	x	x	x	x	x	x	x	x	x	x	Ram1
004000-007FFF	0	0	0	0	0	0	0	0	0	1	x	x	x	x	x	x	x	x	x	x	x	x	x	Rom2
008000-008003	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	x	Peri1
008004-008007	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	x	Peri2

- From this address table we determine which combination of 0's and 1's on the **unused** address lines for each chip are used by the decoder to provide a chip select signal.
- We can thus see that the Boolean expression for the active **low** block select signals is given as

Write VHDL for these decoders

$$\text{Rom1} = A_{23} + A_{22} + A_{21} + \dots + A_{12}$$

$$\text{Ram1} = A_{23} + A_{22} + A_{21} + \dots + (!A_{12})$$

$$\text{Rom2} = A_{23} + A_{22} + A_{21} + \dots + A_{15} + (!A_{14})$$

$$\text{Peri1} = A_{23} + A_{22} + A_{21} + \dots + A_{16} + (!A_{15}) + A_{14} + A_{13} + \dots + A_3 + A_2$$

$$\text{Peri2} = A_{23} + A_{22} + A_{21} + \dots + A_{16} + (!A_{15}) + A_{14} + A_{13} + \dots + A_3 + (!A_2)$$