
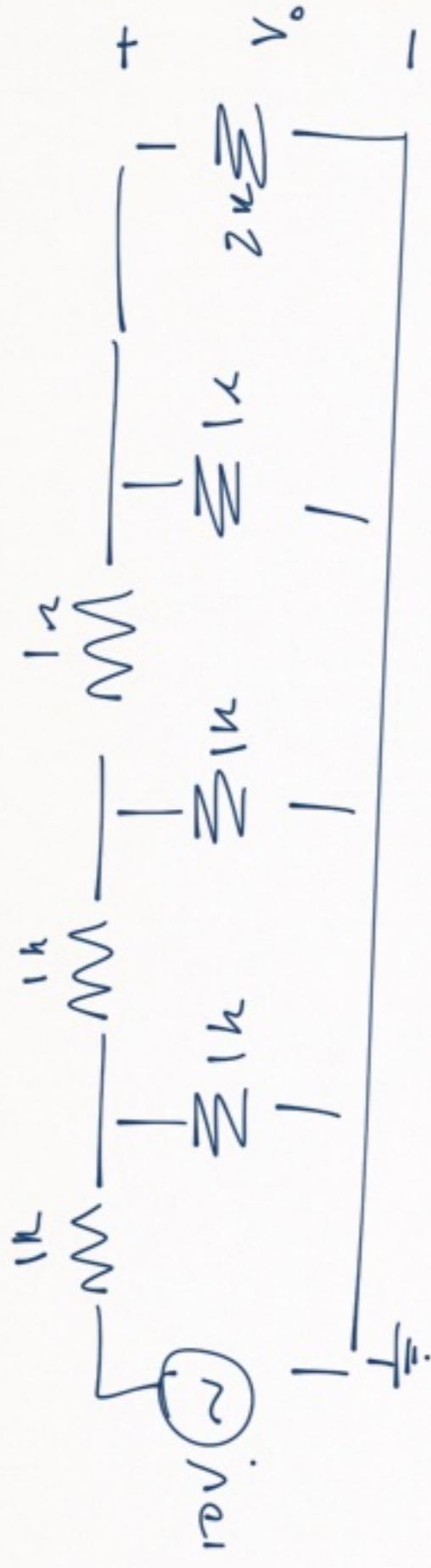


P1.1

Theor. eqv.

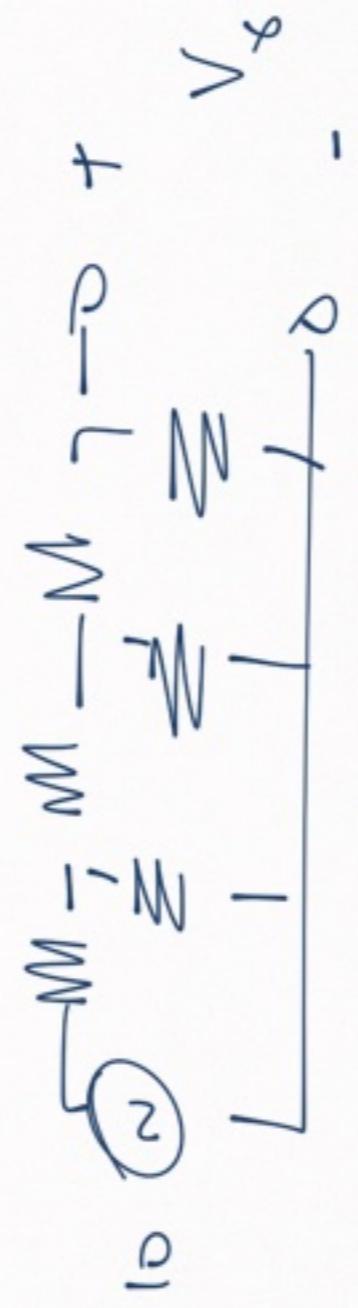


For 2 V_{Tn}



$$\|((Z_L // R) + j\omega) // j\omega) \rightarrow u = 1.62 \leq u = Z_{Tn}$$

Q1

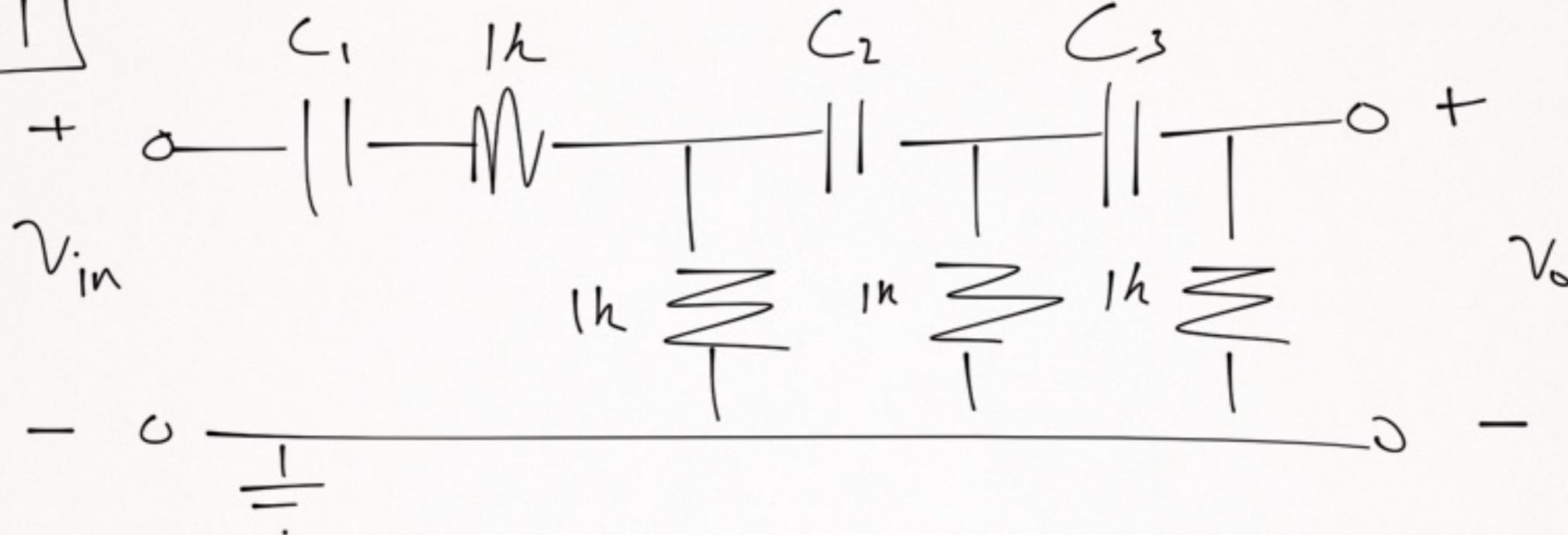

$$\text{Assume} \omega_a = \frac{1}{\sqrt{C_1}}$$

$$\tilde{L}_{C_1} = C_1 \cdot 2k$$




$$\tilde{L}_{C_2} = C_2 (1k + 1k//1k) = C_2 \cdot 1.5k$$


$$\tilde{L}_{C_3} = C_3 (1k + 1k//1k//1k) = C_3 \cdot \frac{4}{3}k$$

$$\omega_a \approx \frac{1}{\tilde{L}_{C_1}} = \frac{1}{C_1 \cdot 2k} = 10 \rightarrow \boxed{C_1 = 50 \mu F}$$

$$\omega_b \approx \frac{1}{\tilde{L}_{C_2}} = \frac{1}{C_2 \cdot 1.5k} = 100 \rightarrow \boxed{C_2 = 6.66 \mu F}$$
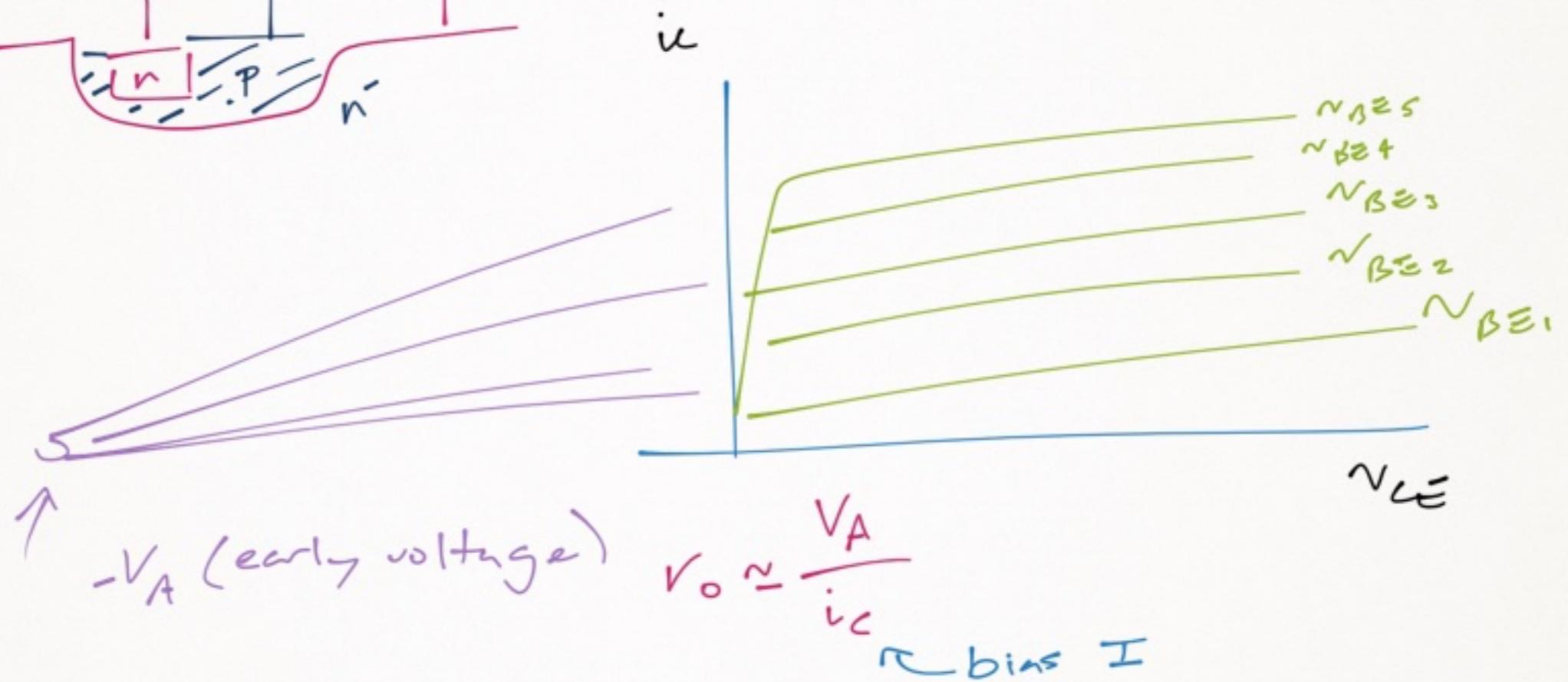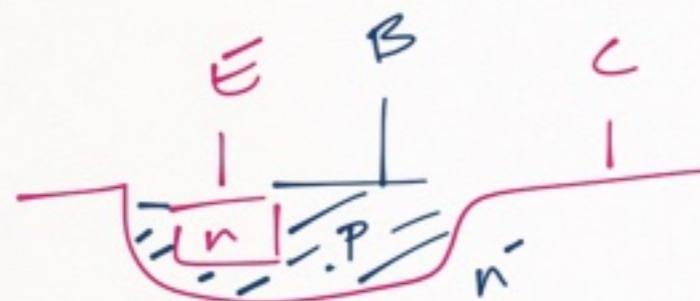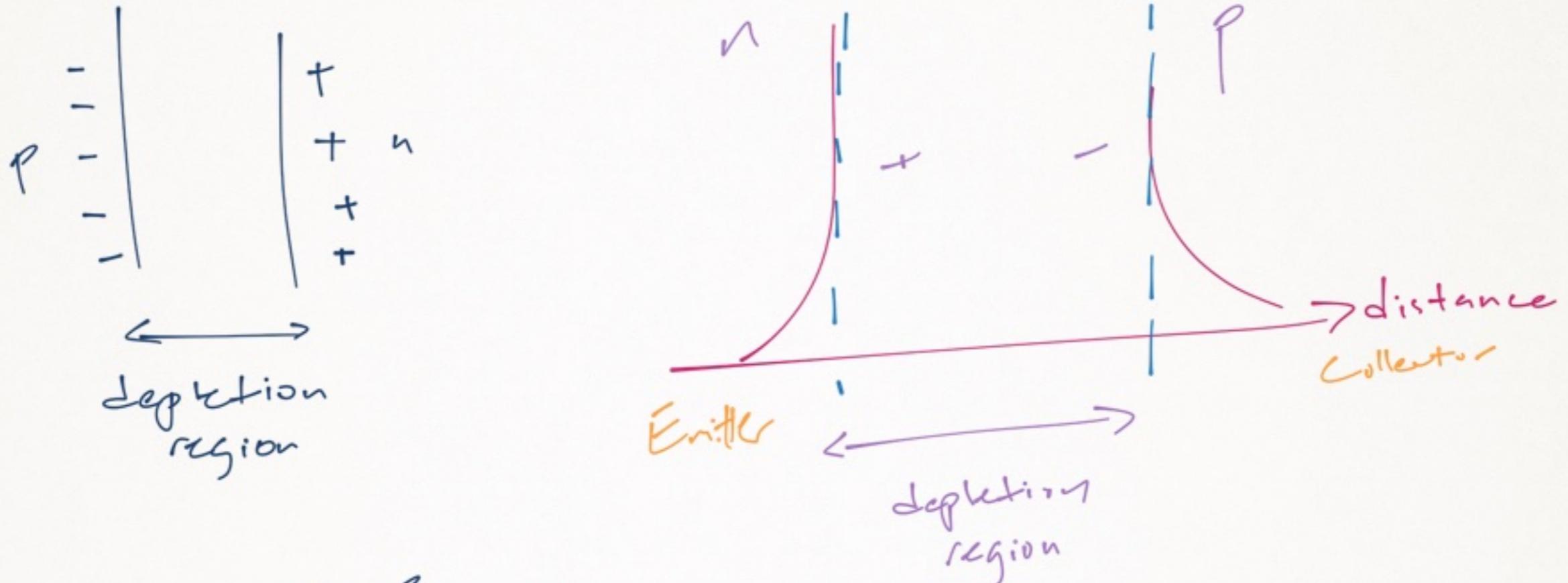
$$\omega_c \approx \frac{1}{\tilde{L}_{C_3}} = \frac{1}{C_3 \cdot \frac{4}{3}k} = 100 \rightarrow \boxed{C_3 = 0.75 \mu F}$$




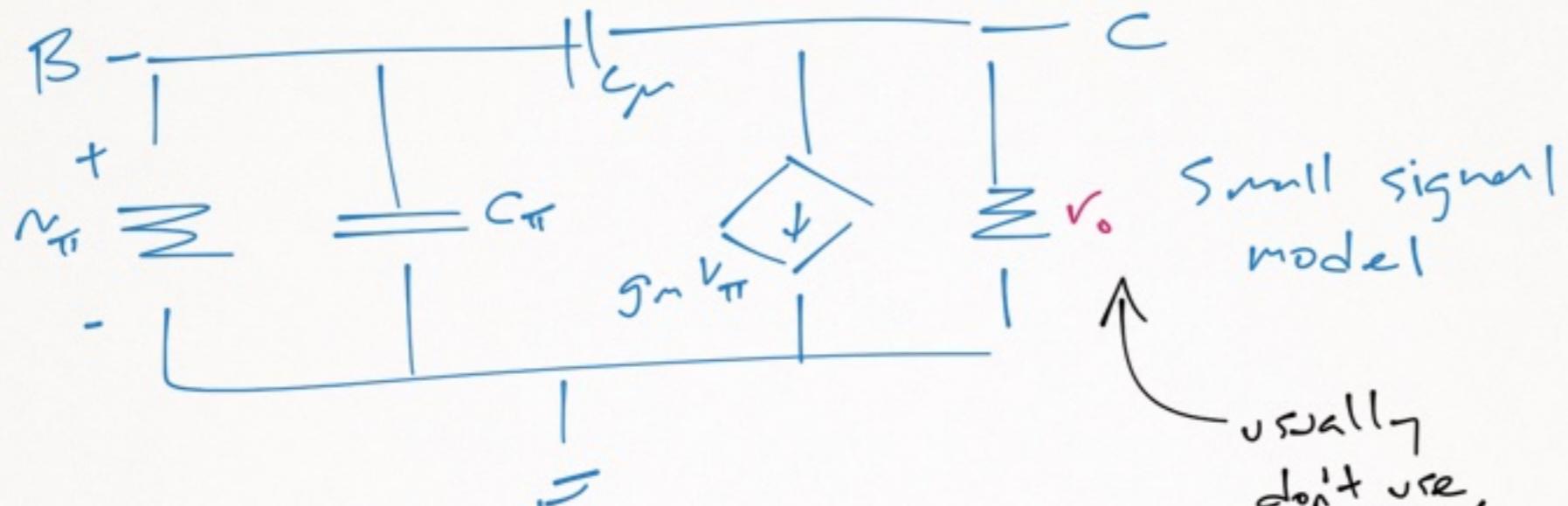


$$r_o = \left(\frac{2}{\beta} \left| \frac{1}{2v_{CE}} \right| v_{BE} = \text{constant} \right)^{-1} \approx \frac{V_A}{i_c}$$

usually
don't use,
approx as
50k

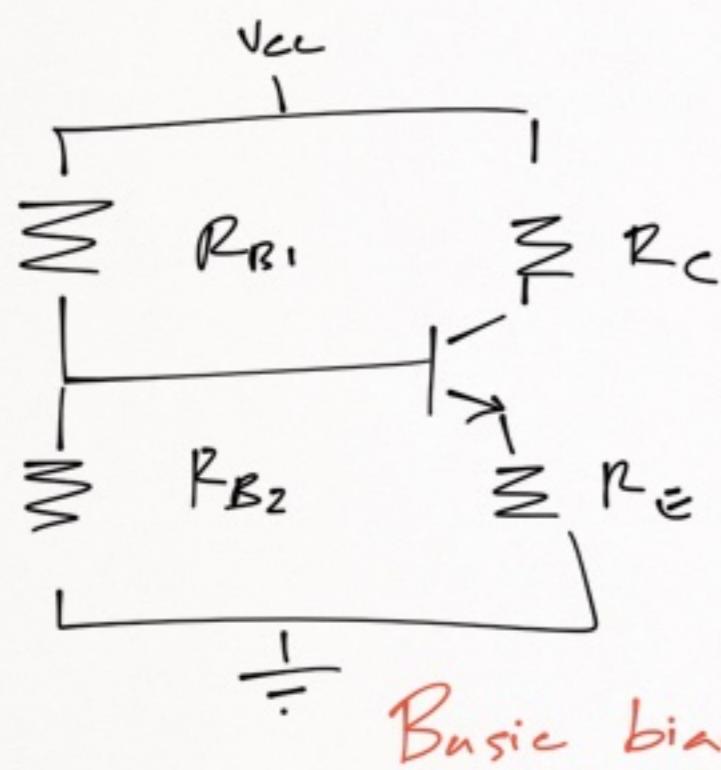- ① how to bias using curve tracer
- ② 1/3 rule (2 versions)




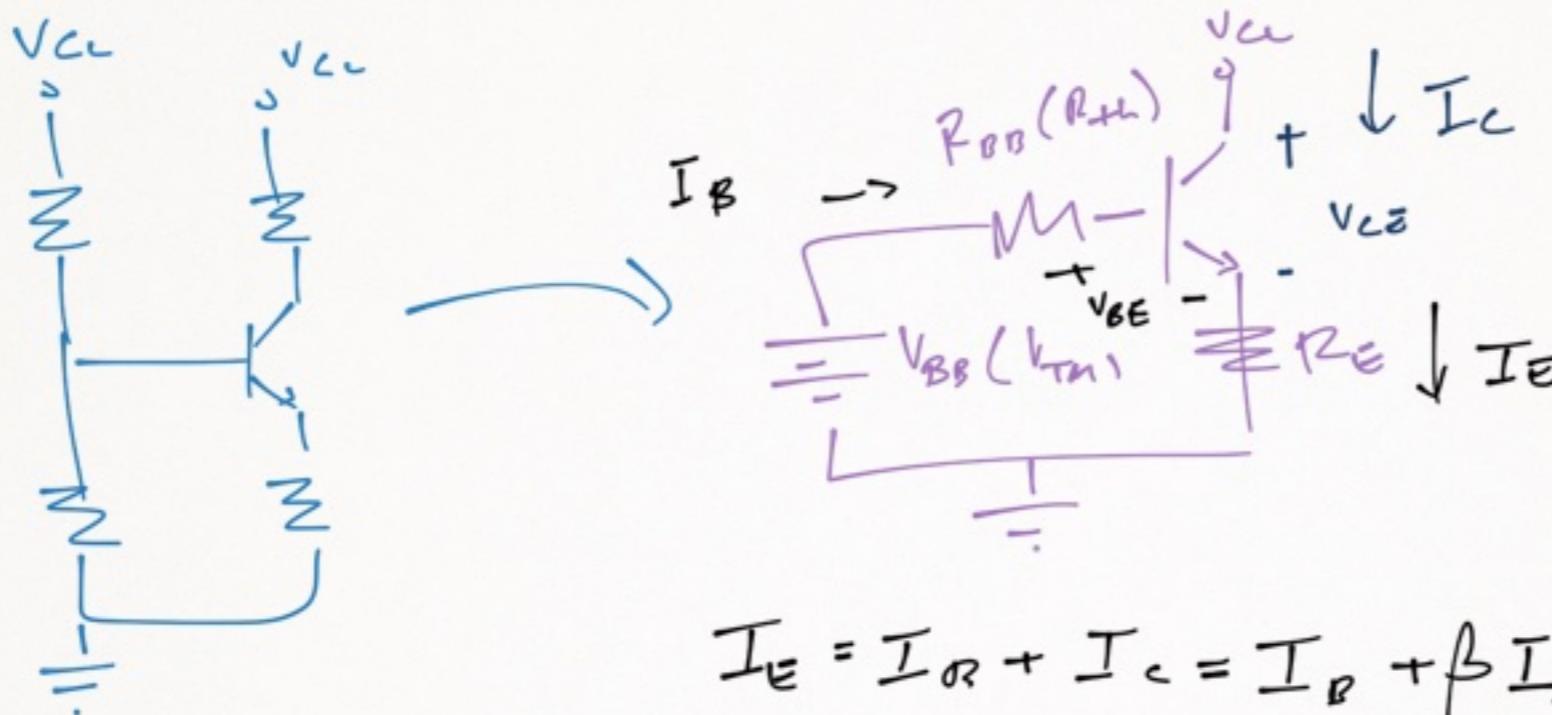


$$I_E = I_{\text{OZ}} + I_c = I_B + \beta I_B$$

$$I_n = -\frac{V_{RE}}{(1+\beta)R_E + R_{BB}} + \frac{V_{BB}}{(1+\beta)R_E + R_{BB}}$$
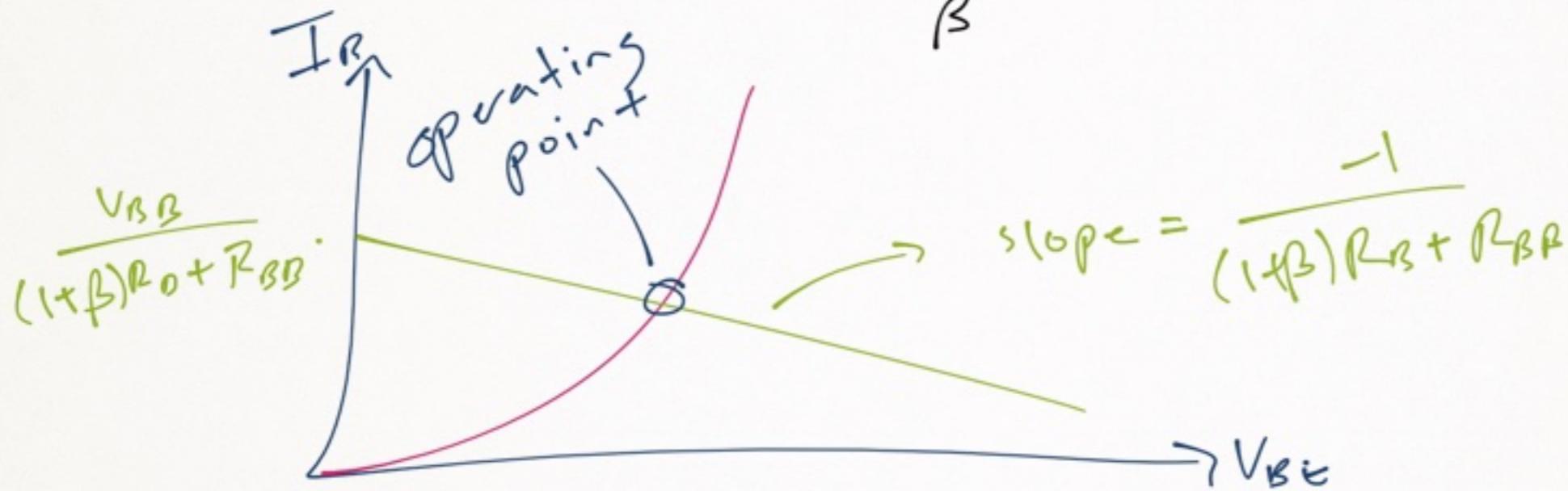
$$I_B = \frac{I_c}{\beta} = I_S e \quad \angle I_E = I_c$$




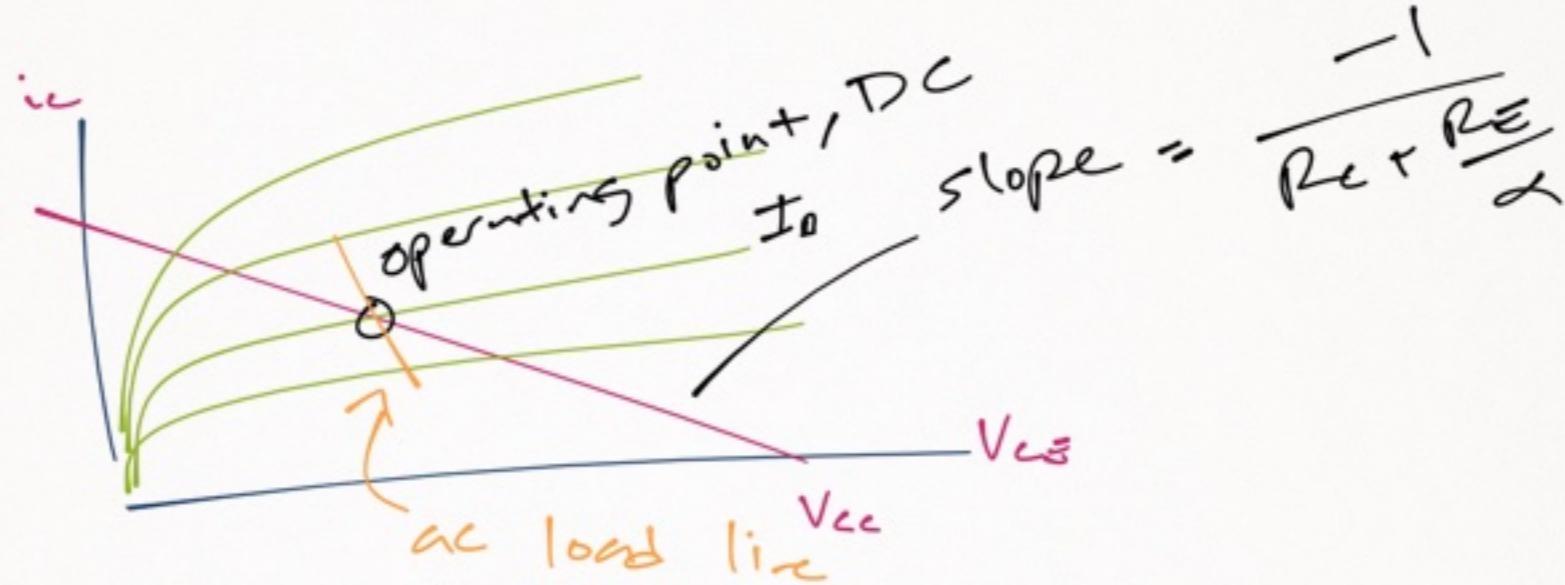
$$\frac{V_{CE}}{R_C + \frac{R_E}{\alpha}}$$



at DC coupling capacitors open circuit

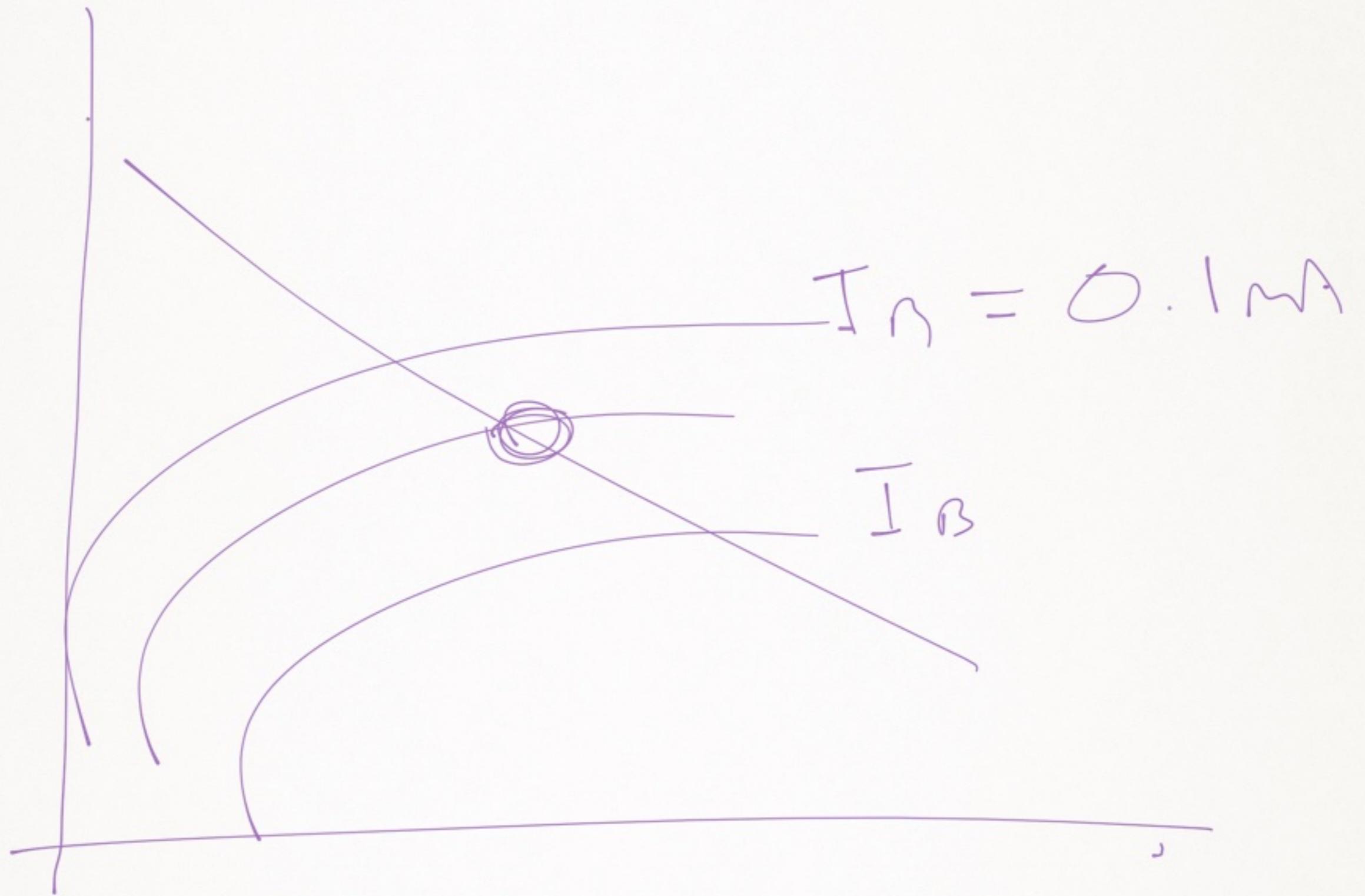\therefore circuit on pg. is same as basic bias circuit



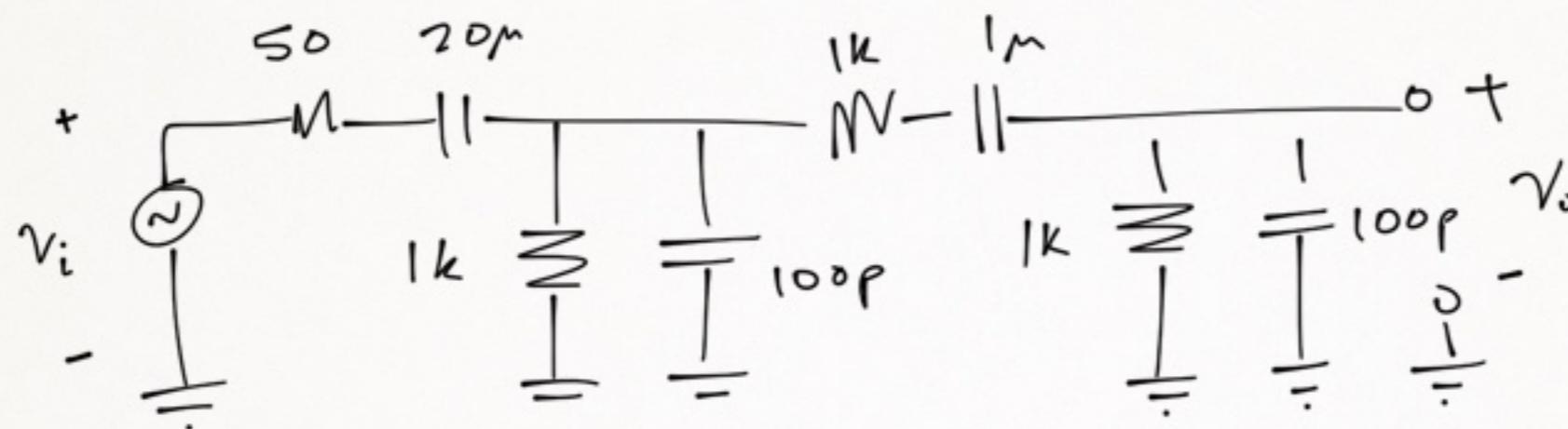



$$\omega_1 = \frac{1}{1.05k \cdot 20\mu} = 47.6 \frac{\text{rad}}{\text{s}}$$

$$\omega_2 = \frac{1}{1\mu(2k + 1k//50)} = 488.1 \frac{\text{rad}}{\text{s}} \rightarrow \omega_{3dB_1} = \sqrt{488.1^2 + 47.6^2} = 490.4 \frac{\text{rad}}{\text{s}}$$

$$\omega_3 = \frac{1}{2\mu(2k + 1k//50)} = 244.1 \frac{\text{rad}}{\text{s}} \rightarrow \omega_{3dB_2} = 249.7 \frac{\text{rad}}{\text{s}}$$

$$\omega_4 = \frac{1}{5} \omega_1 = 97.6 \frac{\text{rad}}{\text{s}} \rightarrow \omega_{3dB_3} = 108.6 \frac{\text{rad}}{\text{s}}$$
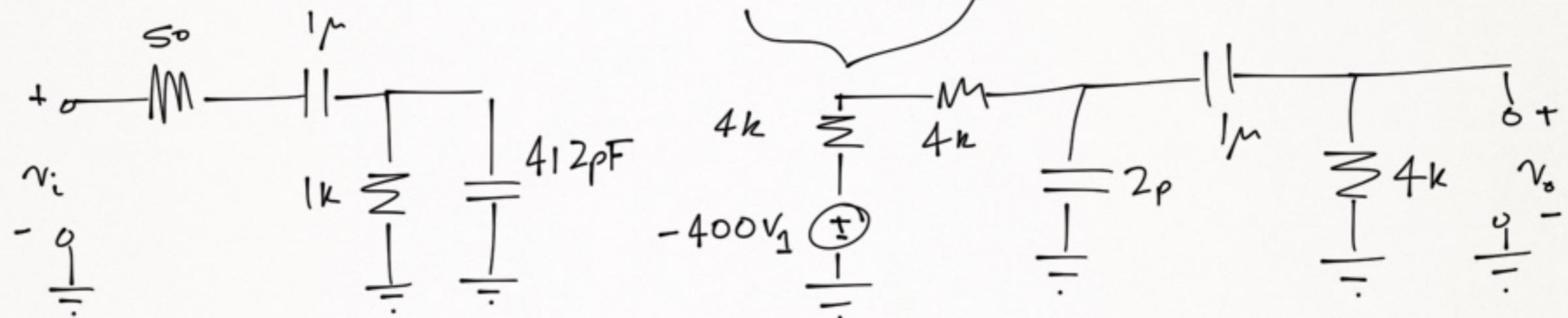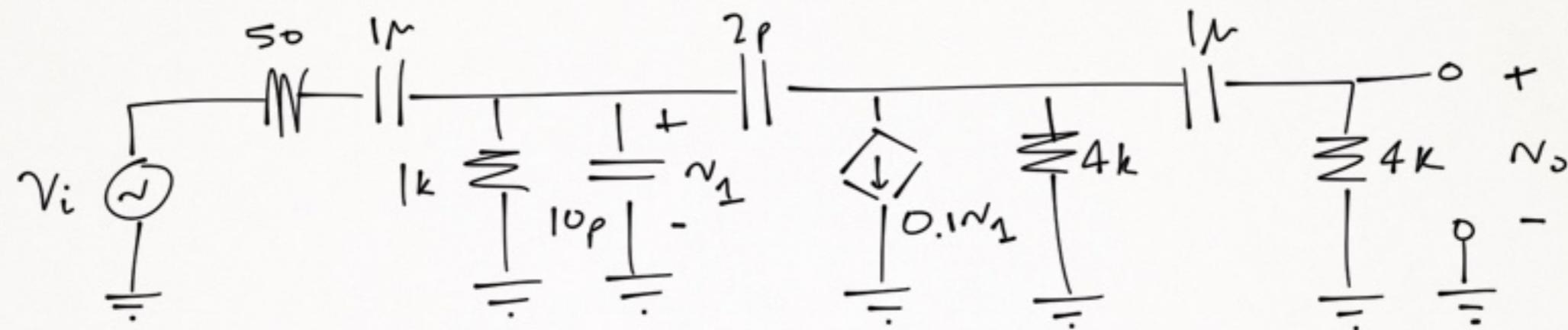
$$\omega_5 = \frac{1}{10} \omega_1 = 48.81 \frac{\text{rad}}{\text{s}} \rightarrow \omega_{3dB_4} = 66.18 \frac{\text{rad}}{\text{s}}$$



$$\omega_{IM} = \frac{1}{1.05k \cdot 1\mu} = \boxed{952.4 \frac{\text{rad}}{\text{s}}}$$

$$\omega_{IM} = \frac{1}{8k \cdot 1\mu} = \boxed{125 \frac{\text{rad}}{\text{s}}}$$

$$\omega_{412p} = \frac{1}{412p \cdot 50 // 1k} = \boxed{50.97 \text{ M} \frac{\text{rad}}{\text{s}}}$$

$$\omega_{2p} = \frac{1}{2p \cdot 2k} = \boxed{250 \text{ M} \frac{\text{rad}}{\text{s}}}$$

$$T(s) = -190 \times \frac{s}{s + 952} \times \frac{s}{s + 125} \times \frac{51 \cdot 10^6}{s + 51 \cdot 10^6} \times \frac{250 \cdot 10^6}{s + 250 \cdot 10^6}$$

midband

3dB calculated

3dB measured


$$\omega_{L3dB} \quad 150 \text{ rad/s}$$

$$\omega_{N3dB} \quad 8.025 \text{ rad/s}$$

$$\omega_{L3dB} = \sqrt{\omega_p^2 + -\zeta_f^2}$$



$$= \sqrt{151.6^2 + }$$

BIASING A TRANSISTOR

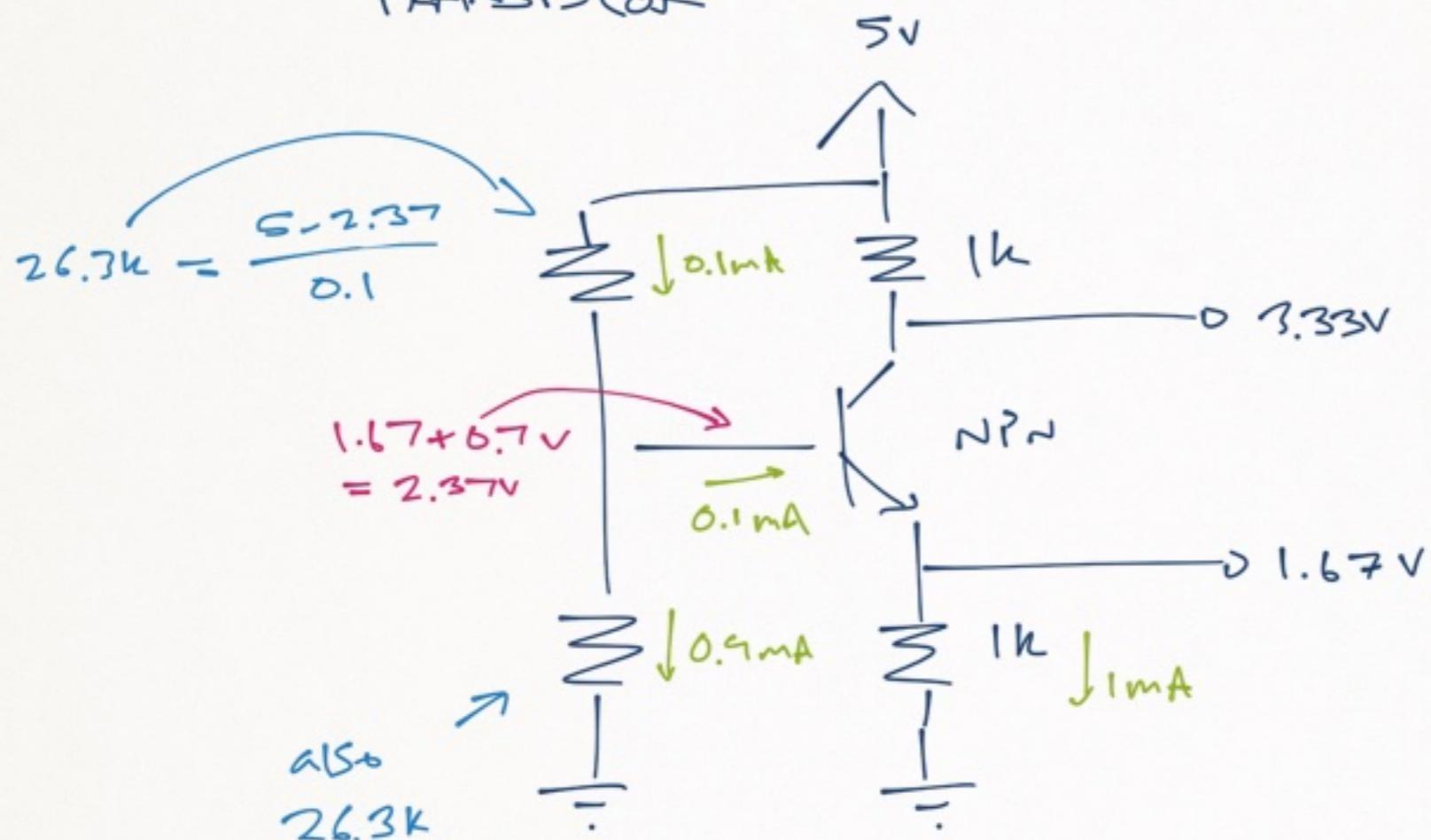


(voltage isn't
that much higher
(\approx we only picked
5V)

COMMON Emitter
Amplifier.

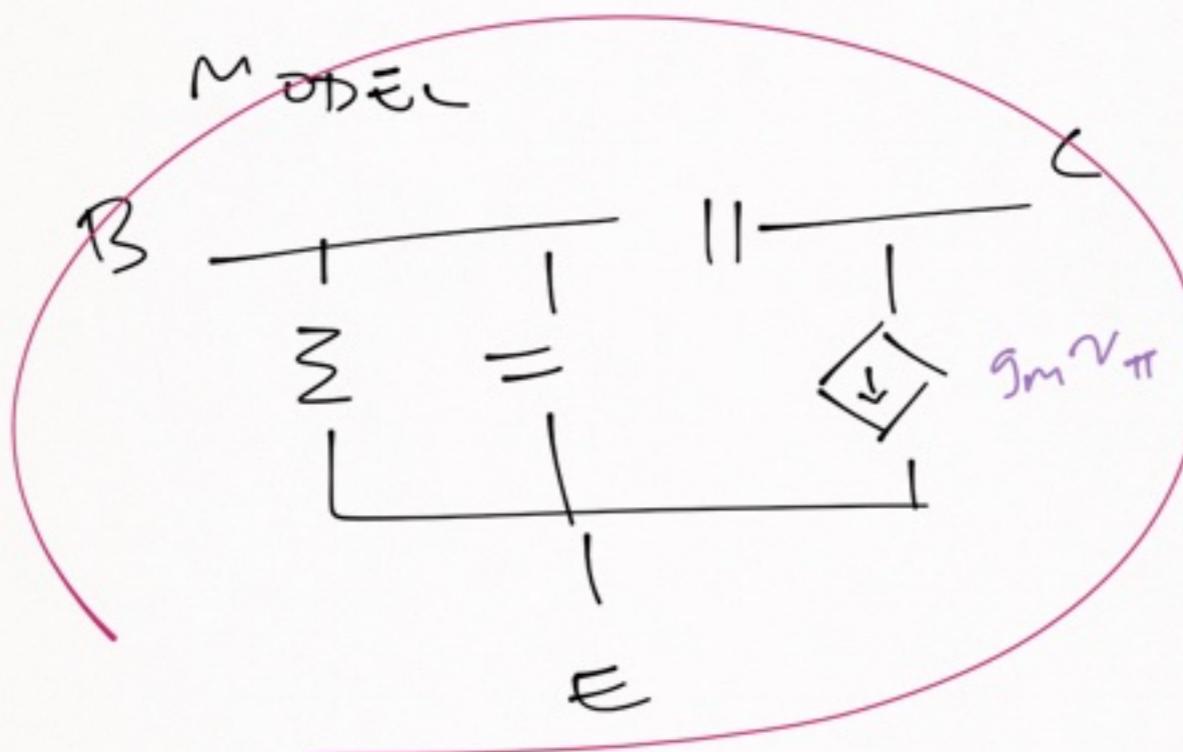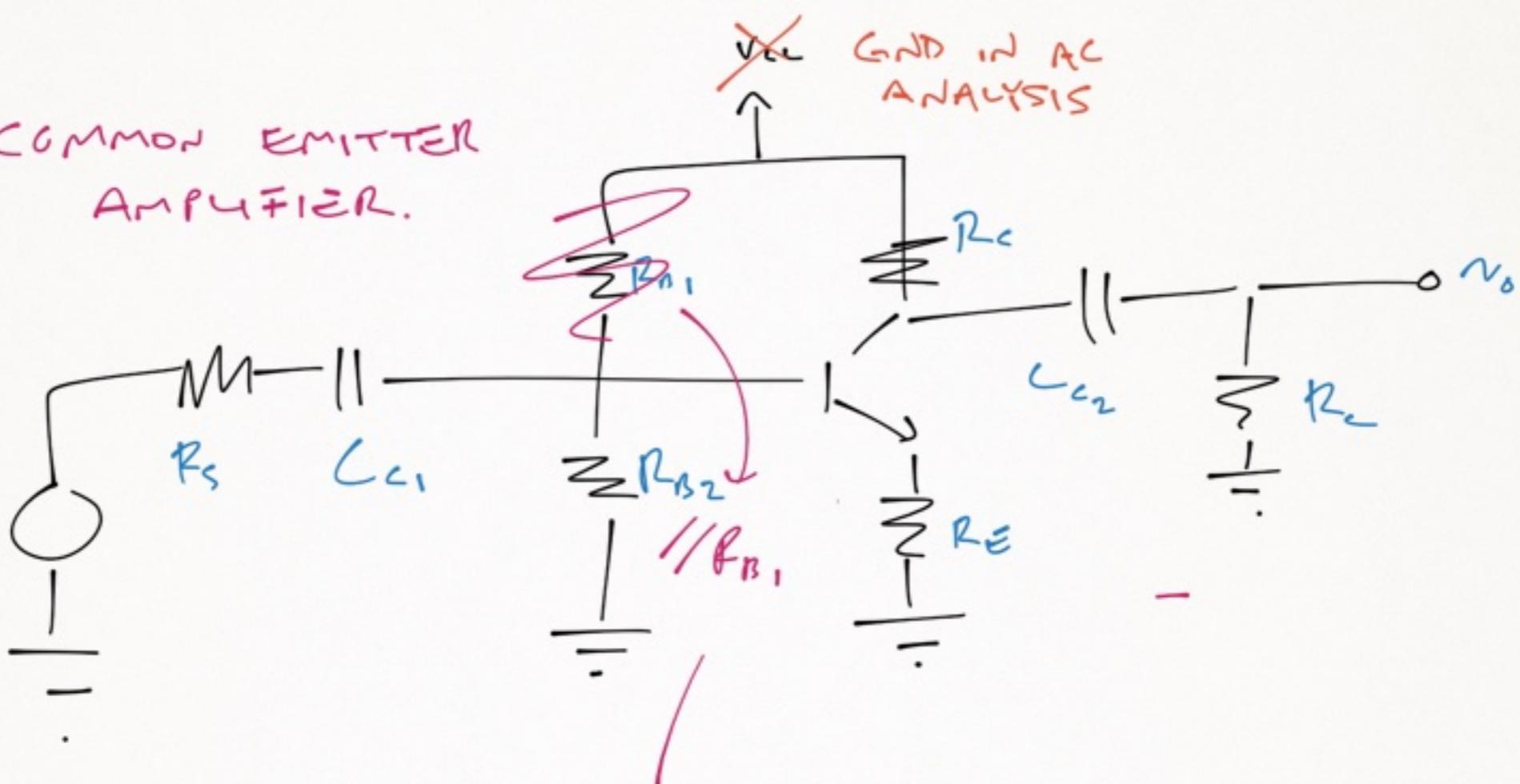

TURNS INTO P10.4

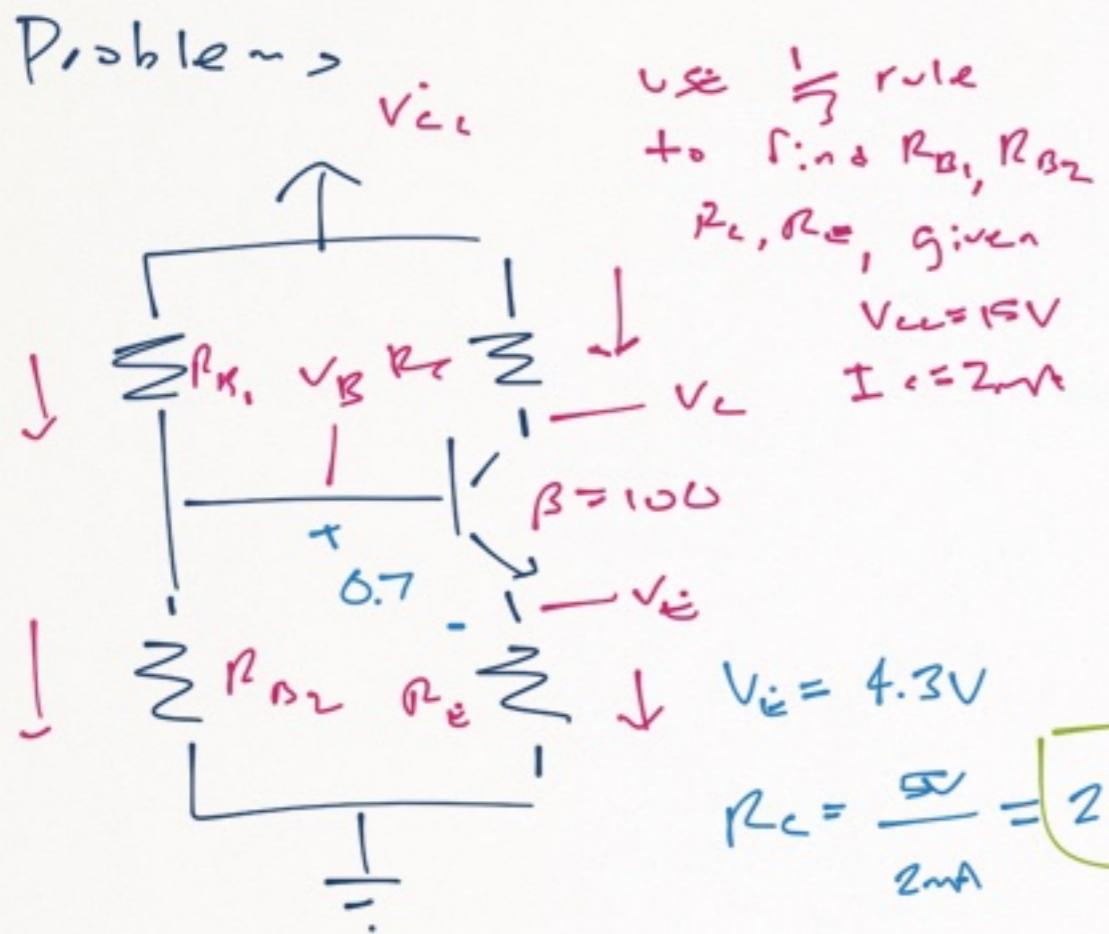

$$V_B = 5V$$


$$V_C = 10V$$

$$R_C = \frac{5V}{2mA} = 2.5k\Omega$$

$$R_E = \frac{4.3V}{2mA} = 2.15k\Omega$$

$$R_{B1} = \frac{15 - 5}{0.2mA} = 50k\Omega$$

$$R_{B2} = \frac{5V}{0.18mA} = 27.8k$$

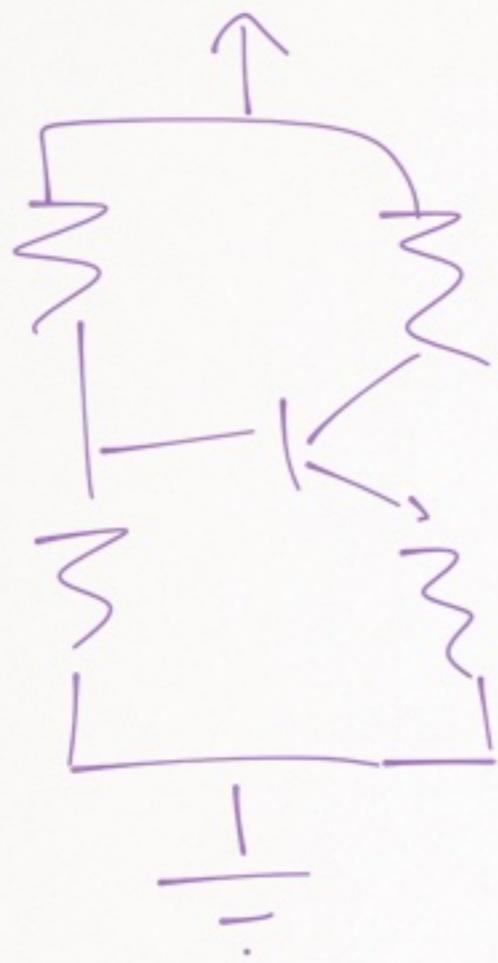

$$R_E = 8k$$

$$V_{CC} = 12V$$

$$V_c = 8V$$

$$V_E = 4V$$

$$I_E \approx I_C$$

$$I_E = \frac{4V}{8k} = 0.5mA$$

$$R_{B_1} = \frac{12V - 4.7V}{0.05mA} = 146k\Omega$$

$$R_{B_2} = \frac{4.7V}{0.045mA} = 104.4k\Omega$$



On freddled grunbluggly
The micturations are to me
Are plurdled gabblebotchits or a lurgid bee
...

DATASHEET 2N2222A.

$h_{ie} = 2 - 8 \text{ k}\Omega$ (input impedance)

$h_{oe} = 5 - 35 \mu\text{s}$ (output admittance)


$V_{CE} = 10\text{V}$

$I_C = 1\text{mA}$

$f = 1\text{kHz}$

$T = 25^\circ\text{C}$

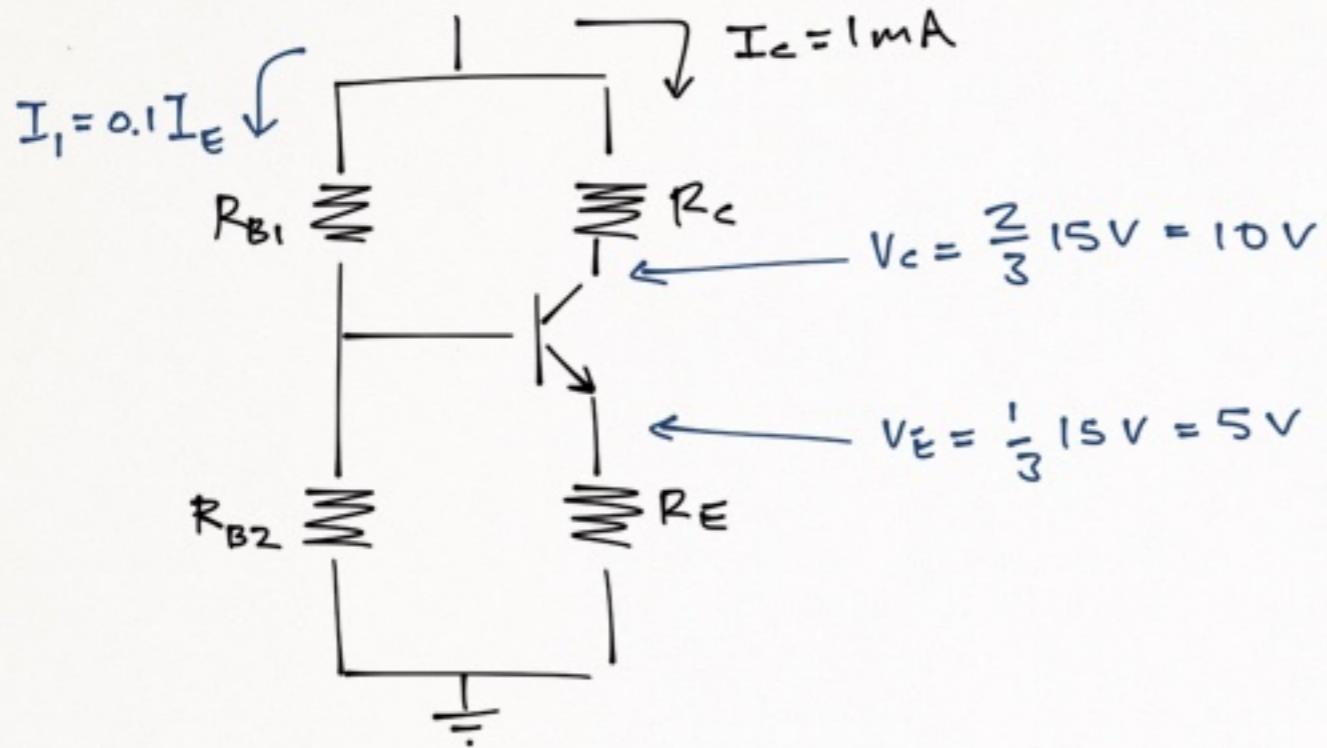BIASING USING $\frac{1}{3}$ RULE APPROXIMATIONS



$$R_C = \frac{1}{3} \frac{V_{CC}}{I_C} = \frac{1}{3} \frac{15}{1 \cdot 10^{-3}} = 5\text{k}\Omega$$

$$R_E \approx R_C = 5\text{k}\Omega$$

$$R_{B1} = \frac{\frac{2}{3} V_{CC} - 0.7\text{V}}{0.1 I_E} = 93\text{k}\Omega$$

$$R_{B2} \approx \frac{\frac{1}{3} V_{CC} + 0.7\text{V}}{0.1 I_E} = 57\text{k}\Omega$$

$$V_{CE} = 5\text{V}$$

$$I_C = 1\text{mA}$$

$$I_E = \frac{V_E}{R_E} = \frac{5\text{V}}{5\text{k}\Omega} = 1\text{mA}$$



source name

$\sim v_1$


start sweep 0

stop $750 \mu V$

step $10 \mu V$

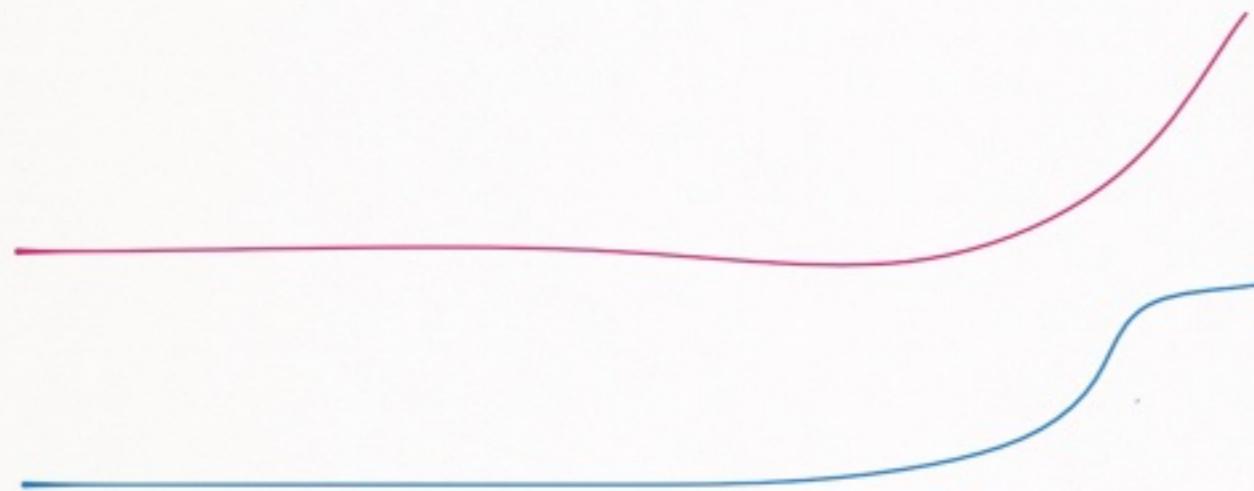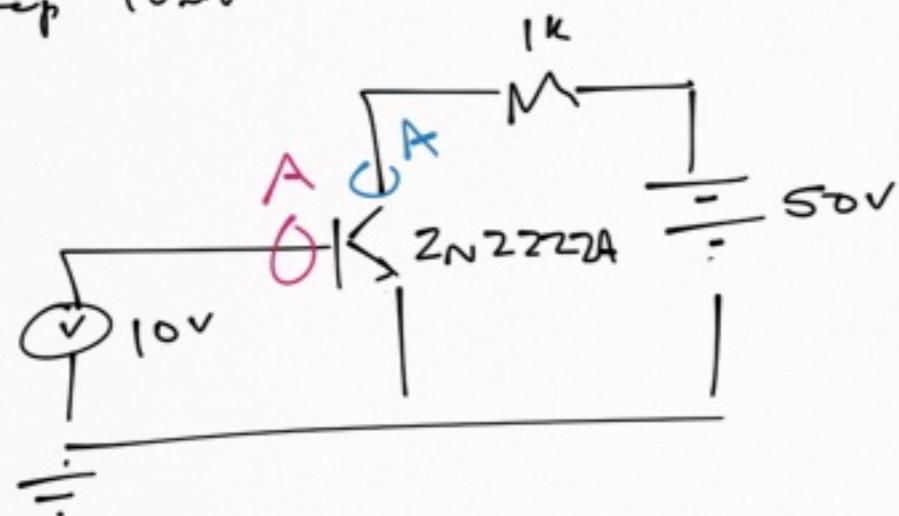

CASCODE

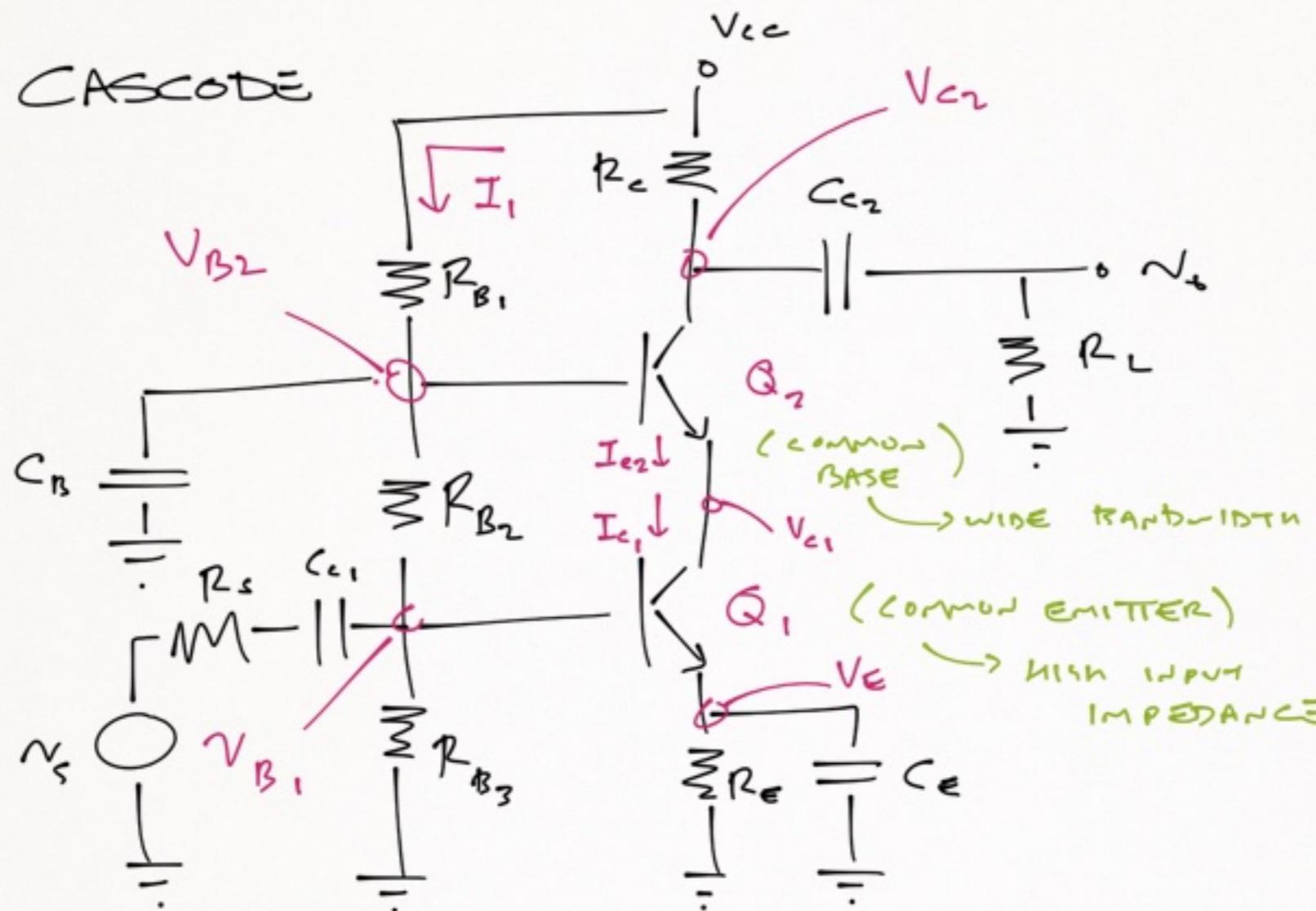

PICK A BIG $C_B \rightarrow$ shoves pole \rightarrow low freq.

USE $\frac{1}{4}$ RULE TO BIAS CASCODE,

DROP ACROSS EACH

$$V_{C2} = \frac{3}{4} V_{CC}, \quad V_{C1} = \frac{1}{2} V_{CC}, \quad V_E = \frac{1}{4} V_{CC}$$

$$V_{B2} = \frac{1}{2} V_{CC} + V_{BE}, \quad V_{B1} = \frac{1}{4} V_{CC} + V_{BE}$$

$$I_1 = 0.1 I_E$$

@ MIDBAND


V_C @ MIDBAND

~ THERE TO
ESTABLISH BIAS

C_{CE} IS S.C.

C_E SHORTED TO GND

SMALL SIGNAL MODEL

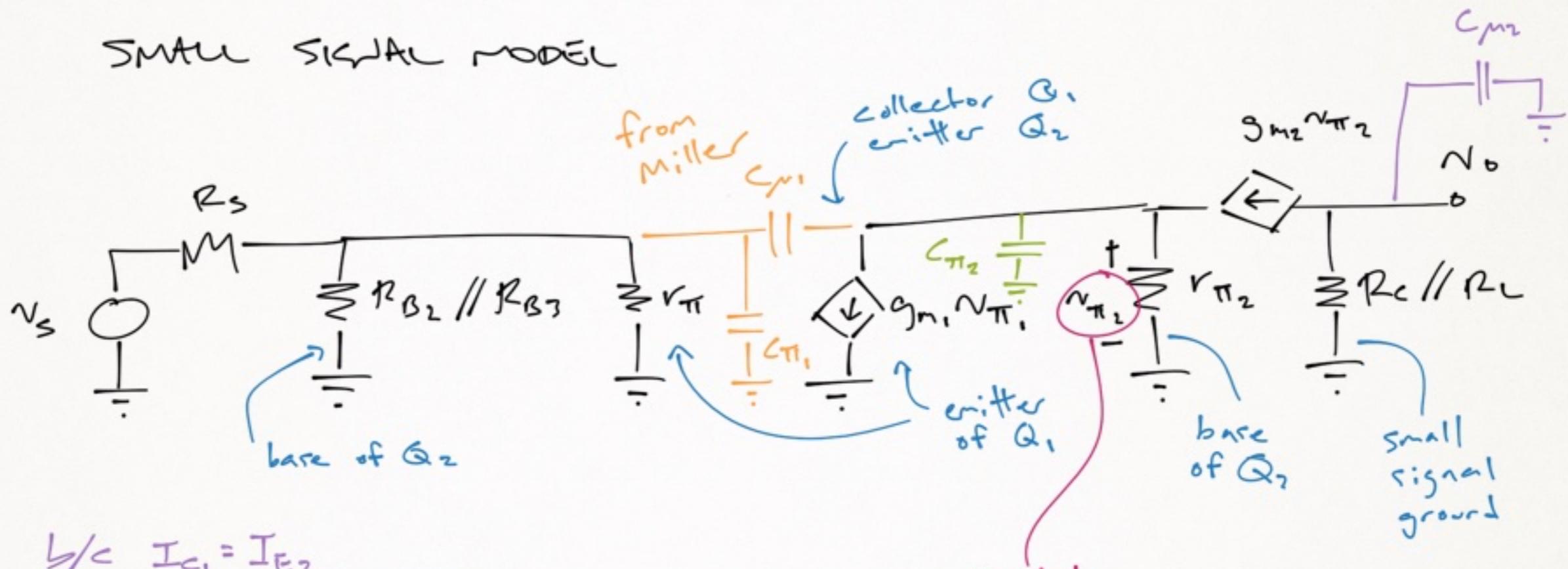

$$\text{b/c } I_{C1} = I_{E2}$$

$$\therefore \boxed{\pi_{\pi_2} = \pi_{\pi_1}}$$

$$I_{C1} \pi_{\pi_1} = \pi_{\pi_2} I_{E2}$$

$$\begin{aligned} & \frac{\pi_{\pi_1} \beta_1}{\gamma_T} \pi_{\pi_1} = \pi_{\pi_2} I_{B2} \frac{1 + \beta}{\gamma_T} \\ & \Rightarrow I_{C1} \frac{\beta_1}{\beta_1} \pi_{\pi_1} = \pi_{\pi_2} I_{C2} \left(\frac{1 + \beta_2}{\beta_2} \right) \\ & = \pi_{\pi_2} \frac{I_{C2}}{\alpha_2} \end{aligned}$$

Sum currents:

$$g_m \pi_{\pi_1} = \frac{\pi_{\pi_2}}{r_{\pi_2}} + g_{m2} \pi_{\pi_2}$$

$$\pi_{\pi_1} \frac{\beta_1}{r_{\pi_1}} = \pi_{\pi_2} \left(\frac{1 + \beta}{r_{\pi_2}} \right)$$

$$g_m = \beta / r_{\pi_1} \quad r_{\pi} = \frac{\pi_T}{I_B}$$

need to figure out


$$\omega_{np3} = \frac{1}{C_{\mu_2} R_C // R_L}$$

$\simeq r_o / (R_C // R_L)$

$$\omega_{np2} = \frac{1}{(C_{\pi_2} + 2C_{\mu_1}) \frac{r_{\pi_2}}{1+\beta}}$$

$\simeq^? \frac{1}{(C_{\pi_2} + 2C_{\mu_1})(R_C // r_{o1})}$

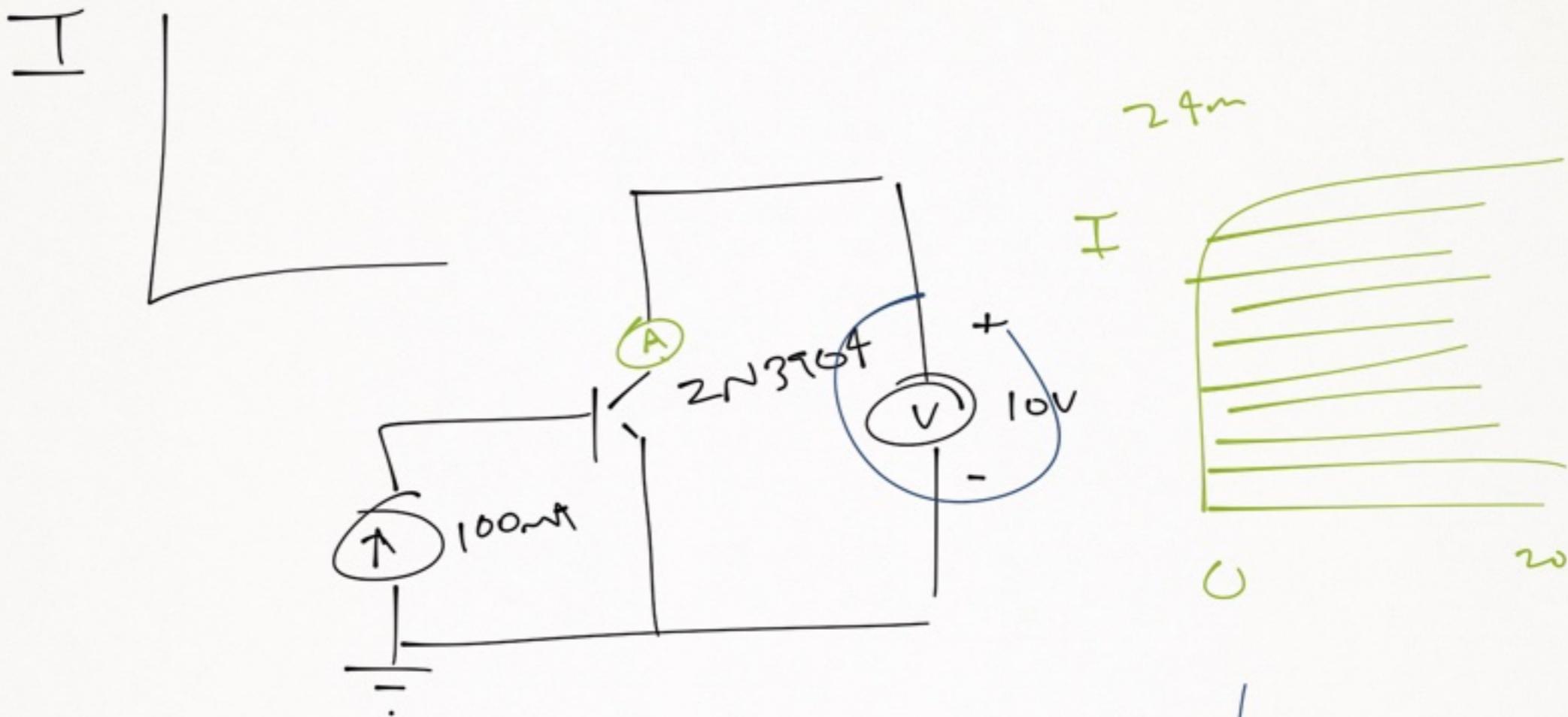
$$\omega_{np1} = \frac{1}{(R_s // R_{o2} // R_{o1} // r_{\pi})(C_{\pi_1} + 2C_{\mu_1})}$$



DC
ANALYSIS
SETUP

V_{S1}
 $0 \rightarrow 20$
step 10m

I_{S1}
 $0 \rightarrow 200\mu$
 10μ step

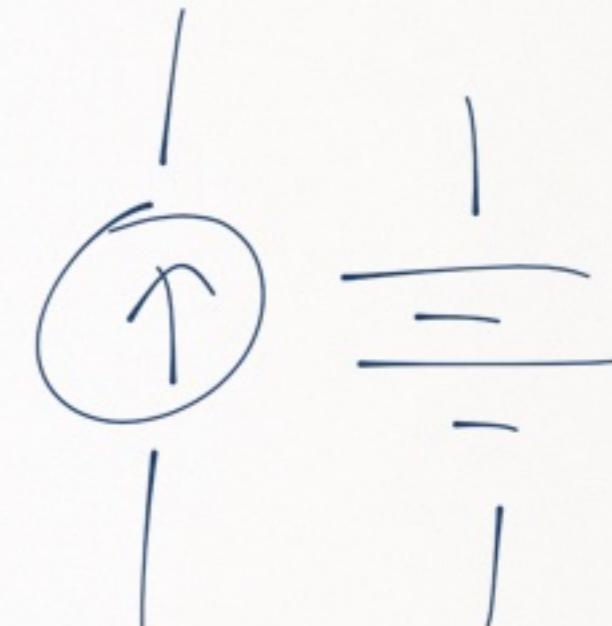

$$b) \text{ transconductance, } g_m = \frac{\delta i_c}{\delta v_{BE}} \Big|_{i_c=1mA}$$

$$I_c = 1mA \quad r_\pi, \beta, r_o \quad \text{UNKNOWN}$$

$$V_{CE} = 5V$$

$$\downarrow V_T = 25.8mV$$

$$r_\pi = \frac{v_{be}}{i_b} = \frac{\beta}{g_m} = \beta \frac{V_T}{I_c} = \frac{\beta}{\beta} \frac{V_T}{I_B}$$

$$\beta = \frac{\frac{i_c}{i_B}}{\text{DC value}} \leftarrow \begin{matrix} \text{instantaneous value} \\ \text{DC value} \end{matrix}$$

$$r_o = \left[\frac{\delta i_c}{\delta v_{CE}} \Big|_{v_{BE} = \text{constant}} \right]^{-1} \approx \frac{V_A}{I_c}$$

$$m = \frac{(3.850 - 3.568) \text{ mA}}{(11.1 - 2.265) \text{ V}} = 0.031919 \frac{\text{mA}}{\text{V}}$$

$$y = mx + b \longrightarrow b = 3.496 \text{ mA}$$

$$-V_A = x = \frac{-3.496 \text{ mA}}{0.031919 \frac{\text{mA}}{\text{V}}} = -109.5 \text{ V}$$

$$r_o \approx \frac{V_A}{I_c} = \frac{109.5 \text{ V}}{1 \text{ mA}} = 109.5 \text{ k}\Omega$$

$$\beta = \frac{I_c}{I_B} = \frac{1\text{mA}}{5.986\mu\text{A}} = \boxed{167.1}$$

$$r_{\pi} = \beta \frac{V_T}{I_C} = 167.1 \frac{25.2\text{mV}}{1\text{mA}} = \boxed{4.21\text{k}\Omega}$$

2N2222A:

calculated $h_{ie} = r_{\pi} = 4.21\text{k}\Omega$ } THESE
 datasheet $h_{ie} = 2-8\text{k}\Omega$ AGREE

calculated $h_{oe} = \frac{1}{r_o} = \frac{1}{109.5\text{k}\Omega} = 9.132\mu\text{s}$ } THESE
 datasheet $h_{oe} = 5-35\mu\text{s}$ AGREE

calculated $h_{fe} = \beta = 167.1$ } THESE ALSO
 datasheet $h_{fe} = 50-300$ AGREE

$$I_B = \frac{I_C}{\beta} = \frac{1mA}{167.1} \simeq 6.0\mu A \neq i_b$$

$$V_{be} = r_T i_b$$

$$i_c = I_C + \frac{I_C}{V_T} \cdot V_{be}$$

$$I_S = \frac{I_C}{\beta} = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}}$$

iv)

① FINDING DC-OPERATING POINT OF TRANSISTOR ($\frac{1}{3}$ BIAS VERSION)

$$V_B = V_{CC} \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) = 15V \cdot \left(\frac{57k\Omega}{93k\Omega + 57k\Omega} \right) = 5.7V$$

$$R_{B_T} = R_{B1} // R_{B2} = 35.3k\Omega$$

$$I_Q = \frac{V_B - V_{BE}}{\frac{R_{B_T}}{\beta + 1} + R_E} = \frac{5.7V - 0.7V}{\frac{35.3k}{167.1 + 1} + 5k} = 960\mu A$$

$$V_Q = V_{CC} - I_Q(R_C + R_E) = 15V - 960\mu A(5k\Omega + 5k\Omega) = 5.40V$$

$\boxed{Q\text{-POINT} = (V_Q, I_Q) = (5.40V, 0.960mA)}$


② FINDING DC-OPERATING POINT FROM APPROXIMATE RESISTANCES

$$V_B = V_{CC} \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) = 15V \left(\frac{56k}{91k + 56k} \right) = 5.71V$$

$$V_E = 5.71V - 0.7V = 5.01V$$

$$I_Q = \frac{V_E}{R_E} = \frac{5.01V}{5.1k\Omega} = 983\mu A, \quad V_Q \approx V_{CC} - V_E - I_Q \cdot R_C = 15 - 5.01 - 983\mu A \cdot 5.1k = 4.98V$$

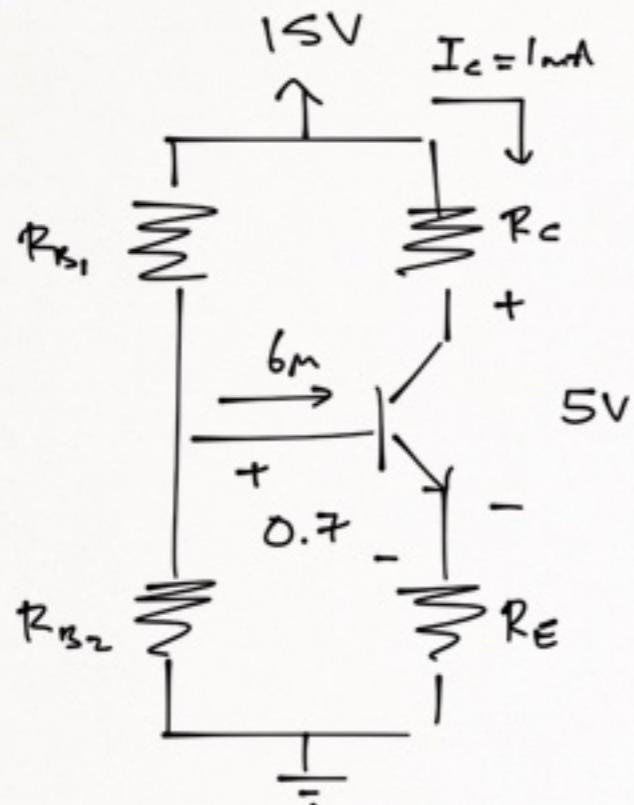$\boxed{Q\text{-POINT} = (4.98V, 0.983mA)}$



BIASING USING V_{π} , r_o , $\neq \beta$

$$I_B = \frac{I_C}{\beta} = \frac{1\text{mA}}{167.1} = 6\mu\text{A}$$

ASSUMPTIONS:

① $V_B = V_E + 0.7$

The voltage drop across R_C is approximately equal to R_E and current through R_C is approximately equal to current through R_E .

∴ safe assumption to choose

② $R_C = R_E$

$$\frac{15 - V_C}{R_C} = 1\text{mA}$$

$$\frac{V_E}{R_E} = 1\text{mA} + 6\mu\text{A}$$

$$R_C = R_E$$

$$V_B = V_E + 0.7$$

$$V_C = V_E + 5\text{V}$$

LINEAR ALGEBRA \rightarrow

↑ INSTEAD OF THIS ASSUMPTION
MAYBE JUST PICK AN R

$$R_C = 4.99\text{k}\Omega$$

$$V_C = 10\text{V}$$

$$V_E = 5.01\text{V}$$

$$V_B = 5.71\text{V}$$

$$\frac{15\text{V} - 5.71\text{V}}{R_{B_1}} = 6\mu + \frac{5.71}{R_{B_2}}$$

$$I_{B_1}$$

$$I_{B_2}$$

$$I_{B_1} = \frac{I_C}{\sqrt{\beta}} = \frac{1\text{mA}}{\sqrt{167.1}} = 77.4\mu\text{A}$$

$$R_C = 4.99\text{k}\Omega \quad R_{B_1} = 120\text{k}\Omega$$

$$R_E = 4.99\text{k}\Omega \quad R_{B_2} = 80\text{k}\Omega$$

(3) DC-OPERATING POINT FROM MEASURED VALUES

$$V_B = 15 \frac{80k}{80k+120k} = 6V$$


$$R_{B_T} = 80k // 120k = 48k$$

$$I_Q = \frac{\frac{5.71 - 0.7}{48k}}{167.1 + 1} = 950\mu A$$

$$V_Q = 15V - 950\mu A(4.99k + 4.99k) = 5.52V$$

Q-POINT = (5.52V, 0.950mA)

COMMON-Emitter

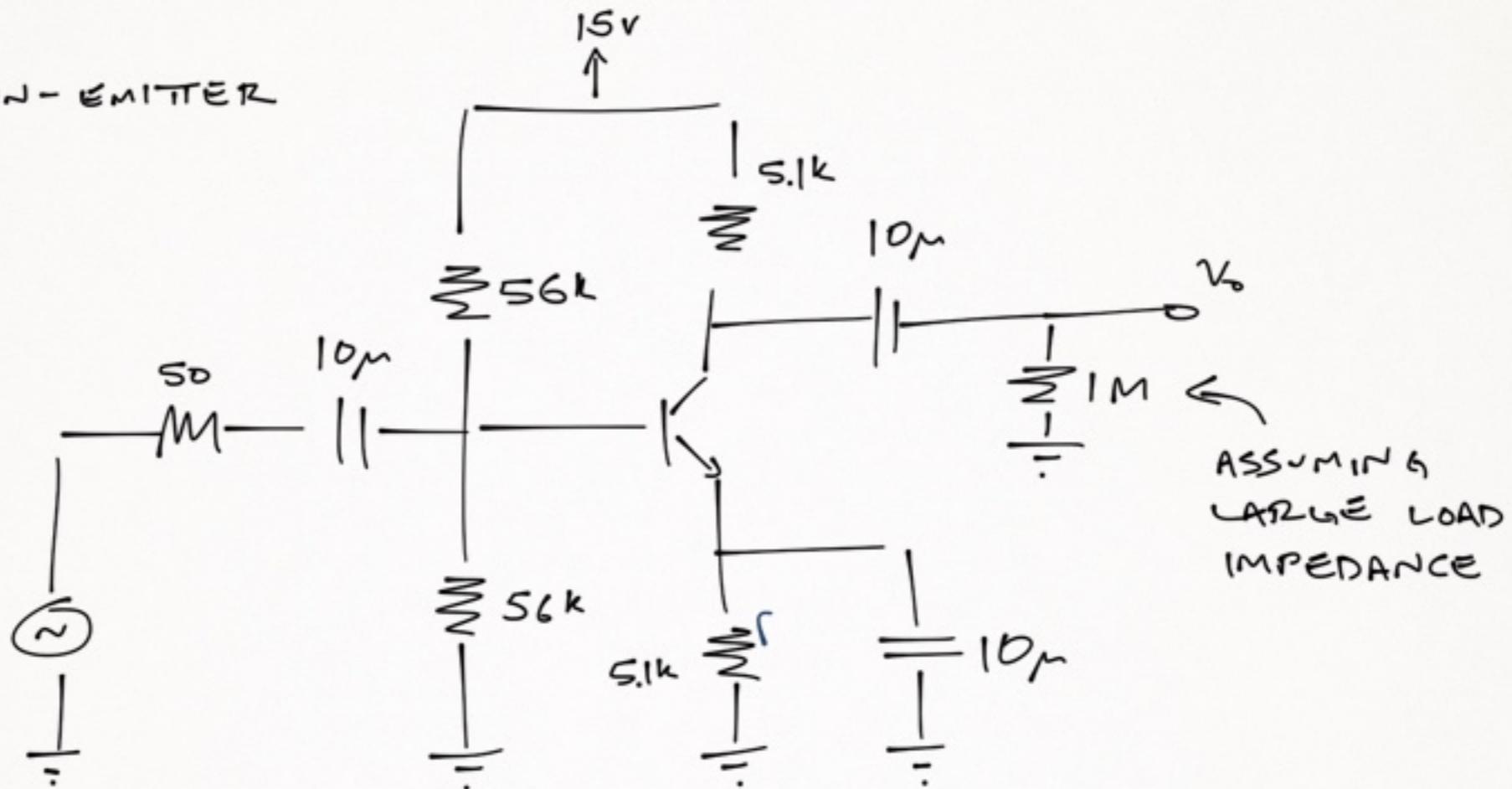


ASSUMING
LARGE LOAD
IMPEDANCE

FROM DATASHEET: $C_m = C_{CB} = 8 \text{ pF}$, $C_{\pi} = C_{EB} = 25 \text{ pF}$

P10.4

REVISIT.
USE CALC.
From Bottom

HIGH FREQ. MODEL

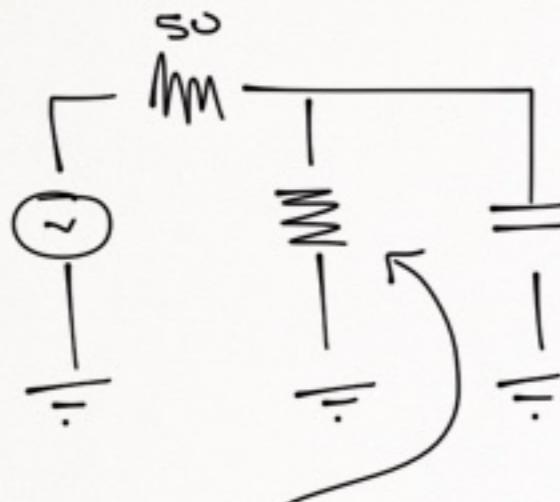


NOTE: WE ARE ASSUMING A
VERY LARGE LOAD
IMPEDANCE, 1M

$$C_{\pi} + C_{\mu} \left(1 + g_m R_L / R_c \right) = 2s_p + s_p \left(1 + \frac{167.1}{4.21k} \cdot 5.1k \right) = 1.65 \text{nF}$$

$$R_B = r_{\pi} \parallel R_{B_1} \parallel R_{B_2} = 4.21k \parallel 56k \parallel 91k = 3.75k \Omega$$

$$\omega_{n_{p1}} = \frac{1}{1.65n(R_s \parallel R_B)} = \frac{1}{1.65n(50 \parallel 3.75k)} = 12.3 \text{ M} \frac{\text{rad}}{\text{s}} = \boxed{1.95 \text{ MHz}}$$

↑
POLE

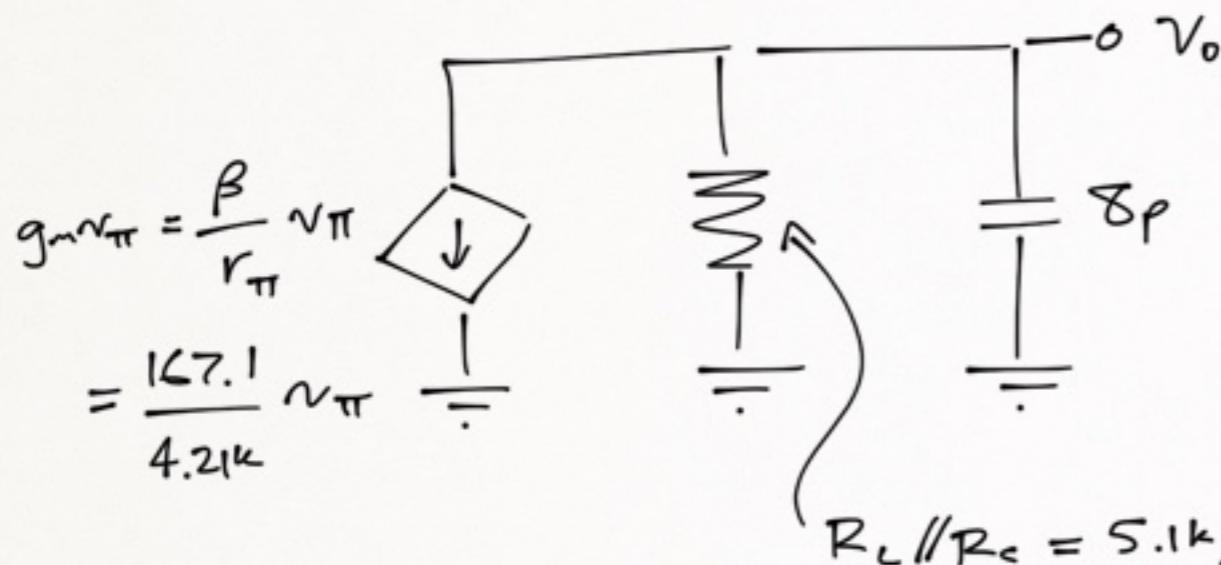

$$g_m v_{\pi} = \frac{\beta}{r_{\pi}} v_{\pi}$$


$$= \frac{167.1}{4.21k} v_{\pi}$$

$$R_L \parallel R_c = 5.1k \parallel 1M = 5.07 \mu\text{F}$$


$$\omega_{n_{p2}} = \frac{1}{R_L \parallel R_c \cdot C_{\mu}} = \frac{1}{1M \parallel 5.1k \cdot 8_p} = 24.6 \text{ M} \frac{\text{rad}}{\text{s}} = \boxed{3.92 \text{ MHz}}$$

↑
POLE

LOW FREQ. MODEL

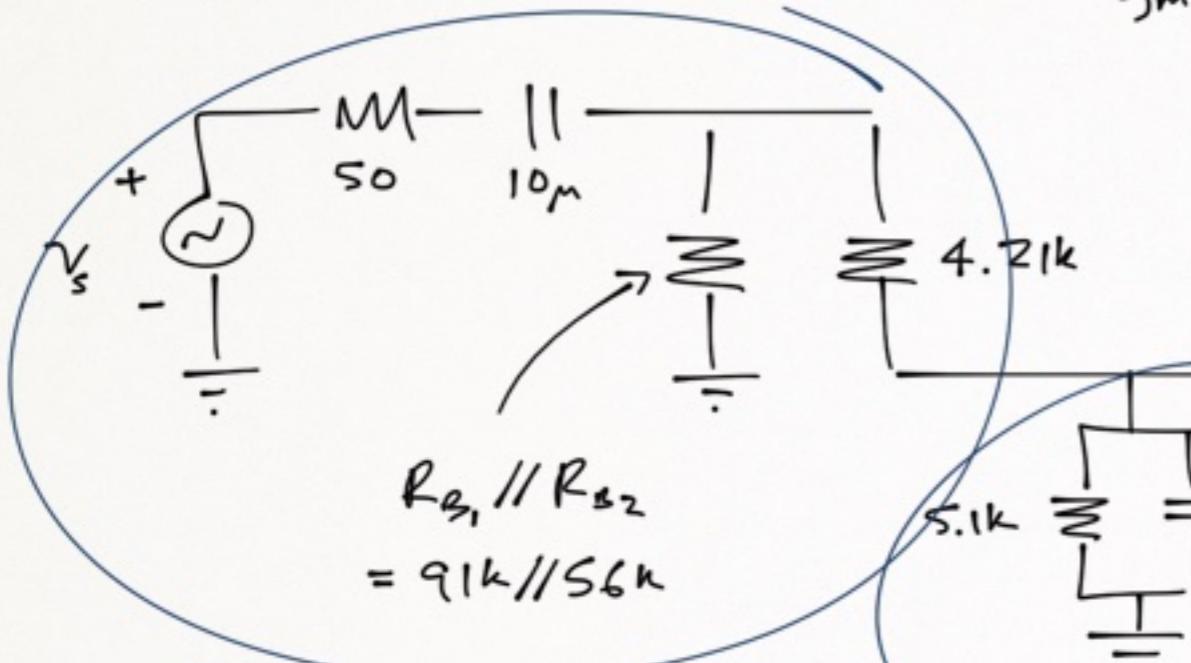
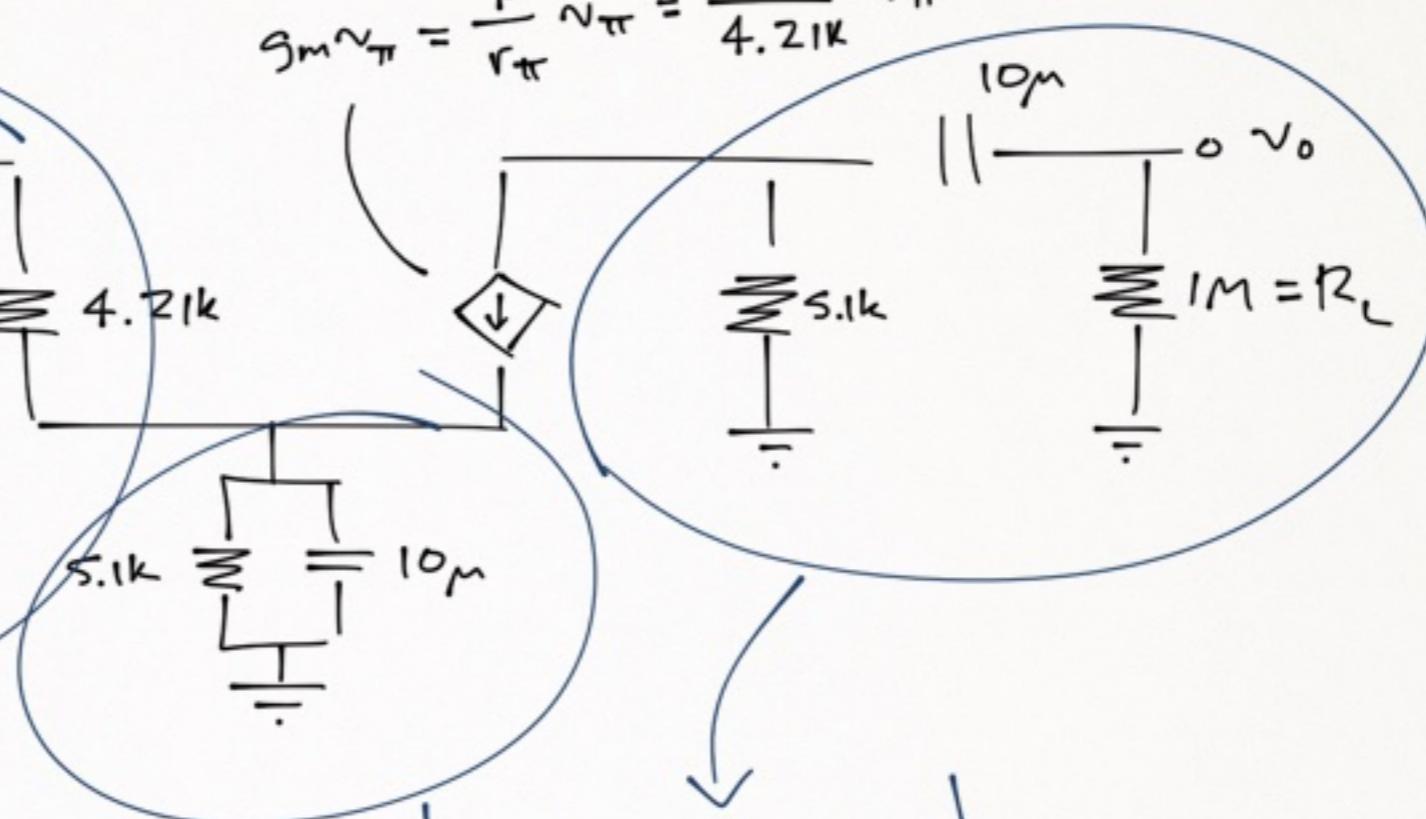
$$g_m v_\pi = \frac{\beta}{r_\pi} v_\pi = \frac{167.1}{4.21k} v_\pi$$



$$\omega_{P2L} = \frac{1}{R_S + R_{CB} // [r_\pi + (1+\beta)R_E]} C_{C_1}$$

$$= \frac{1}{50 + (56k // 91k) // (4.21k + 1(8.1 \cdot 5.1k))} 10\mu$$

$$= 3 \frac{rad}{s} = \boxed{477 \text{ MHz}} \leftarrow \text{POLE}$$

$$\omega_{P3L} = \frac{1}{R_E // \frac{r_\pi + R_{CB} // R_S}{1 + \beta}} C_E = 3.97k \frac{rad}{s}$$

$$= \boxed{631 \text{ Hz}} \leftarrow \text{POLE}$$

$$\omega_{LP2} = \frac{1}{10\mu (5.1k + 1M)}$$

$$= 100\mu \frac{rad}{s} = \boxed{15.8 \text{ MHz}}$$

POLE

$$\omega_{Z1L} = \omega_{Z2L} = \phi$$

$$\omega_{Z3L} = \frac{1}{R_E C_E} = \frac{1}{5.1k \cdot 10\mu}$$

$$= 19.6 \frac{rad}{s} = \boxed{3.12 \text{ Hz}}$$


ZERO

INPUT IMPEDANCE MEASURED FROM WAVE FUNCTIONS


$$Z_{in} = \frac{V_{ce1}}{I_{ce1}} = \frac{986.7 \mu V}{333.3 \mu A} = \boxed{2.96 k\Omega}$$

INPUT IMPEDANCE CALCULATED
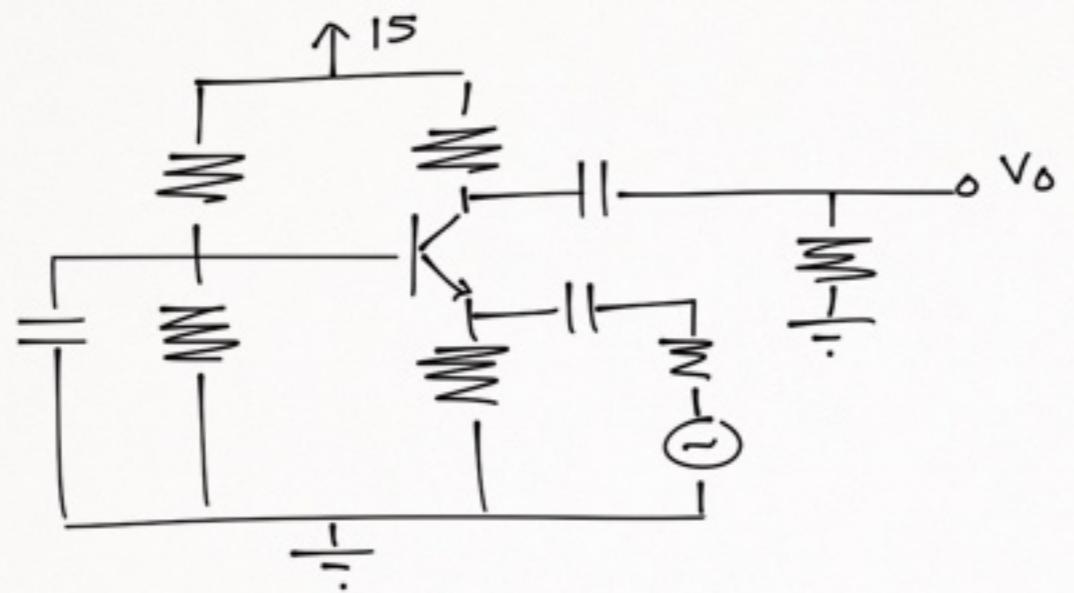
$$Z_{in} = r_\pi // R_{BQ} = r_\pi // R_B // R_{B2} = \boxed{3.76 k\Omega}$$



LOW FREQ. SMALL-SIGNAL MODEL

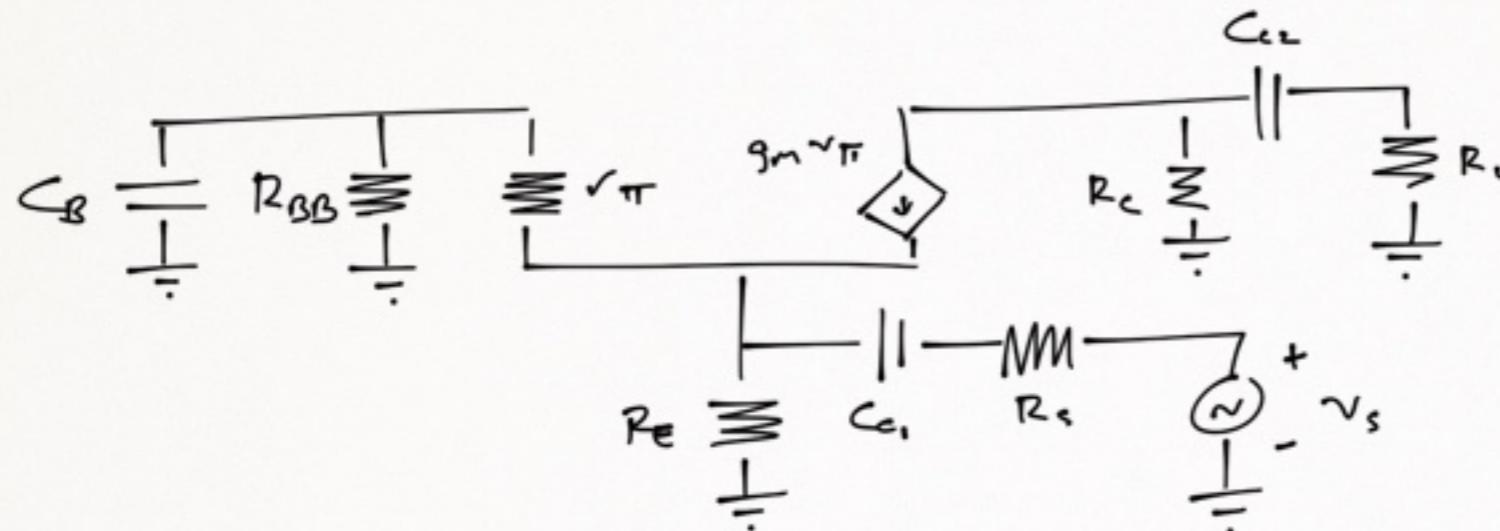


$$\omega_{LP1} = \frac{1}{C_B R_{BB}} = \frac{1}{10\mu(91k//56k)} = 2.88 \frac{\text{rad}}{\text{s}} = \boxed{459 \text{ mHz}}$$

$$\omega_{LP1} = \frac{1}{(R_C + R_L) C_{C2}} = \frac{1}{(5.1k + 1M) 10\mu} = 99.5 \text{ m} \frac{\text{rad}}{\text{s}} = \boxed{15.8 \text{ mHz}}$$


$$\begin{aligned} \omega_{LP2} &= \frac{1}{(R_{BB} // [r_\pi + (1+\beta)(R_E // R_S)]) C_B} = \frac{1}{(35.2k // [4.21k + 168.1(5.1k//50)]) 10\mu} \\ &= 10.9 \frac{\text{rad}}{\text{s}} = \boxed{1.73 \text{ Hz}} \end{aligned}$$

$$\omega_{LP3} = \frac{1}{\left(\frac{r_\pi}{1+\beta} // R_E + R_S\right) C_{E1}} = \frac{1}{\left(\frac{4.21k}{168.1} // 5.1k + 50\right) 10\mu} = 1.33 \frac{\text{rad}}{\text{s}} = \boxed{212 \text{ Hz}}$$

HIGH FREQ. SMALL-SIGNAL MODEL

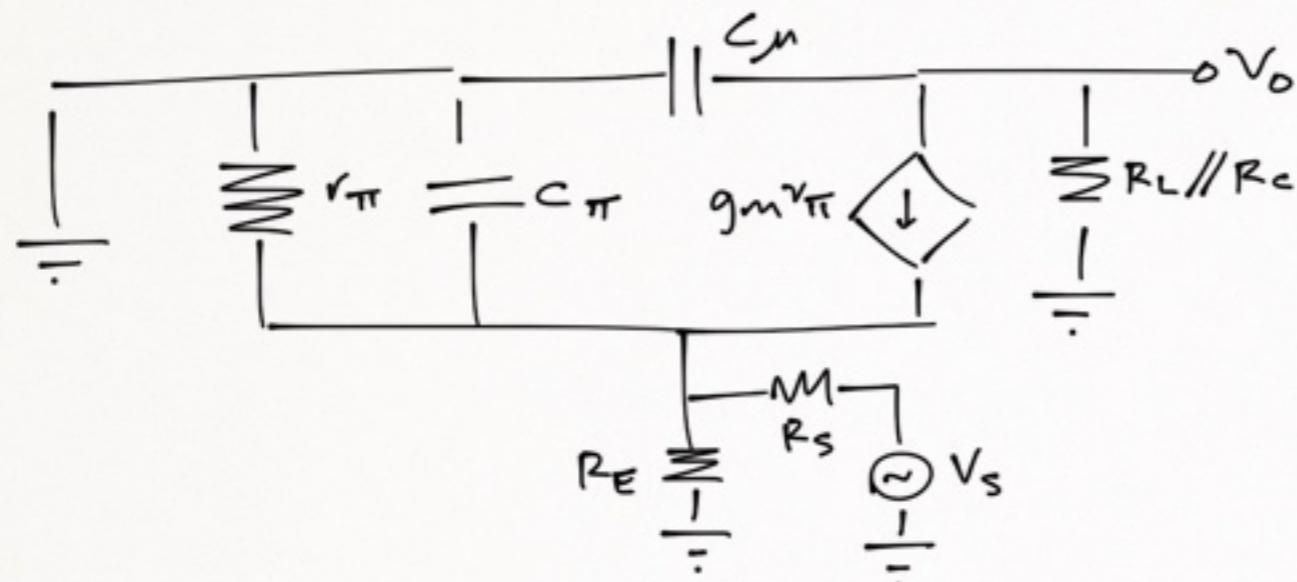

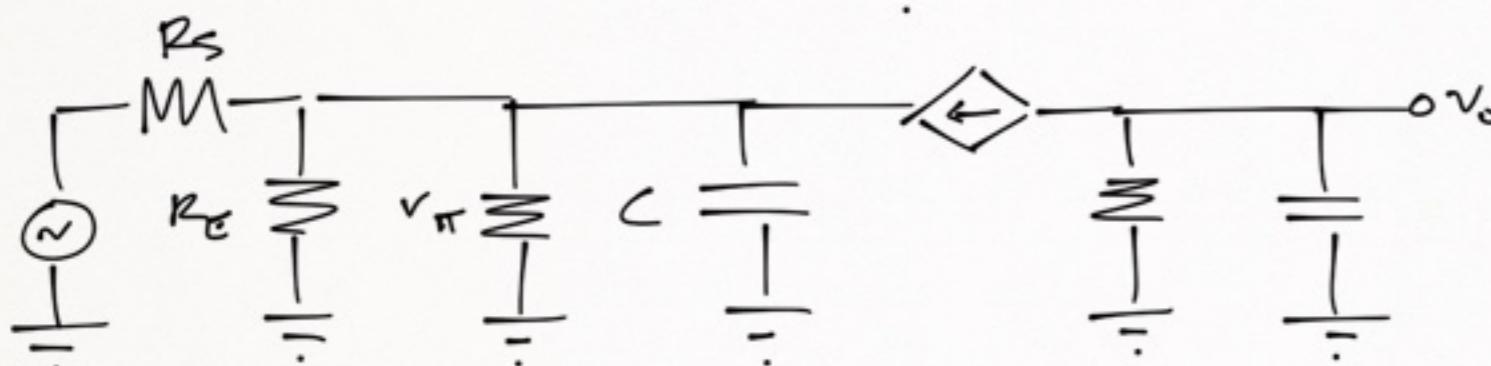COMMON-BASE AMPLIFIER
WITH HYBRID MODEL β
COUPLING \neq BYPASS CAPACITORS



CIRCUIT REORGANIZED
FOR READABILITY


$$\omega_{PH1} = \frac{1}{(R_E // R_S // \frac{r_\pi}{1+\beta}) C_\pi} = \frac{1}{(5.1k // 50 // \frac{4.21k}{1+167.1}) 25\text{pF}} = 2.40 \text{ G} \frac{\text{rad}}{\text{s}} = \boxed{383 \text{ MHz}}$$

$$\omega_{PH2} = \frac{1}{(R_L // R_C) C_\mu} = \frac{1}{(1M // 5.1k) 8\text{pF}} = 24.6 \text{ M} \frac{\text{rad}}{\text{s}} = \boxed{3.92 \text{ MHz}}$$

OCT 20 2014

PROBLEM SET #3

Q. 3 + 4.

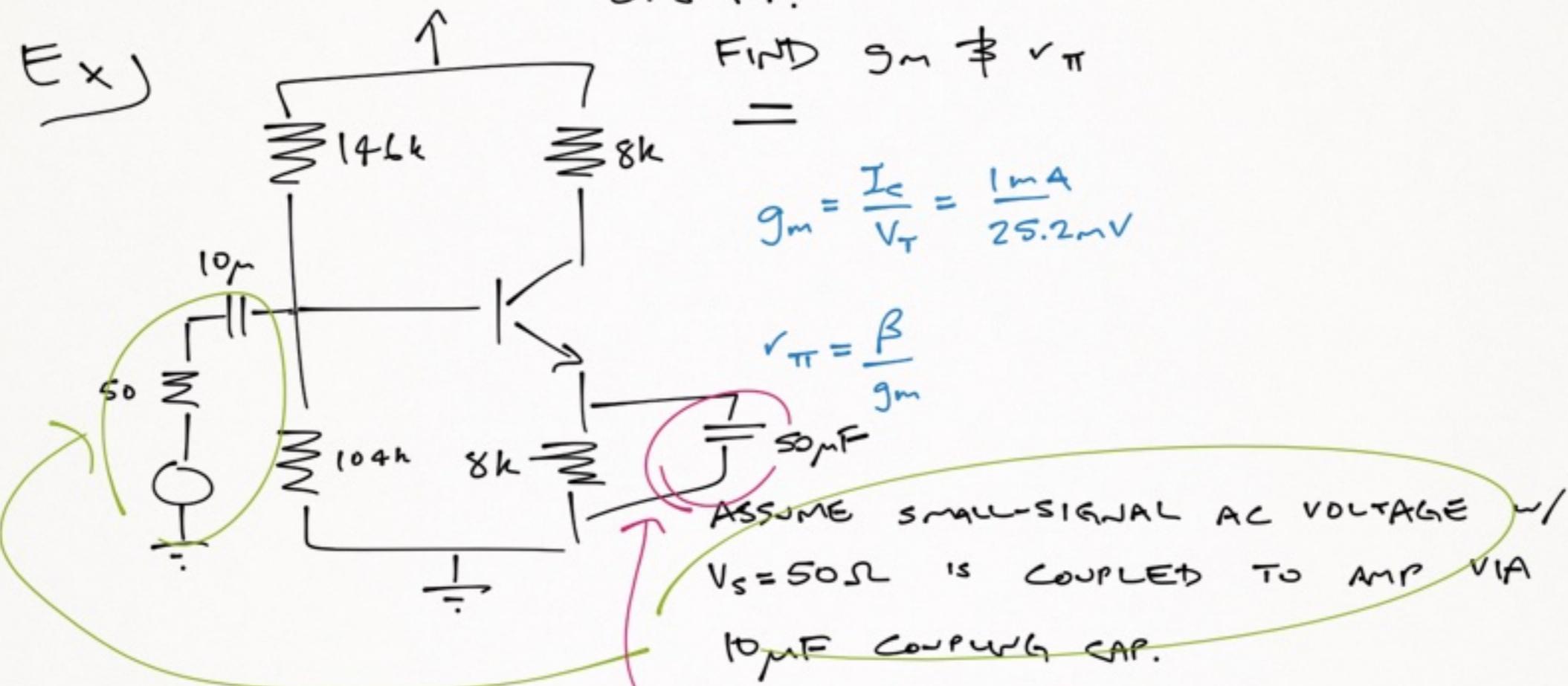


RE IS BYPASSED USING
50μF CAPACITOR.

$$C_\pi = 10\mu F, C_L = 2\mu F, r_o = \infty$$

FIND $A_v, \omega_{3dB}, \omega_{3dB}$.

Ex) cont'd

TRA₁ model

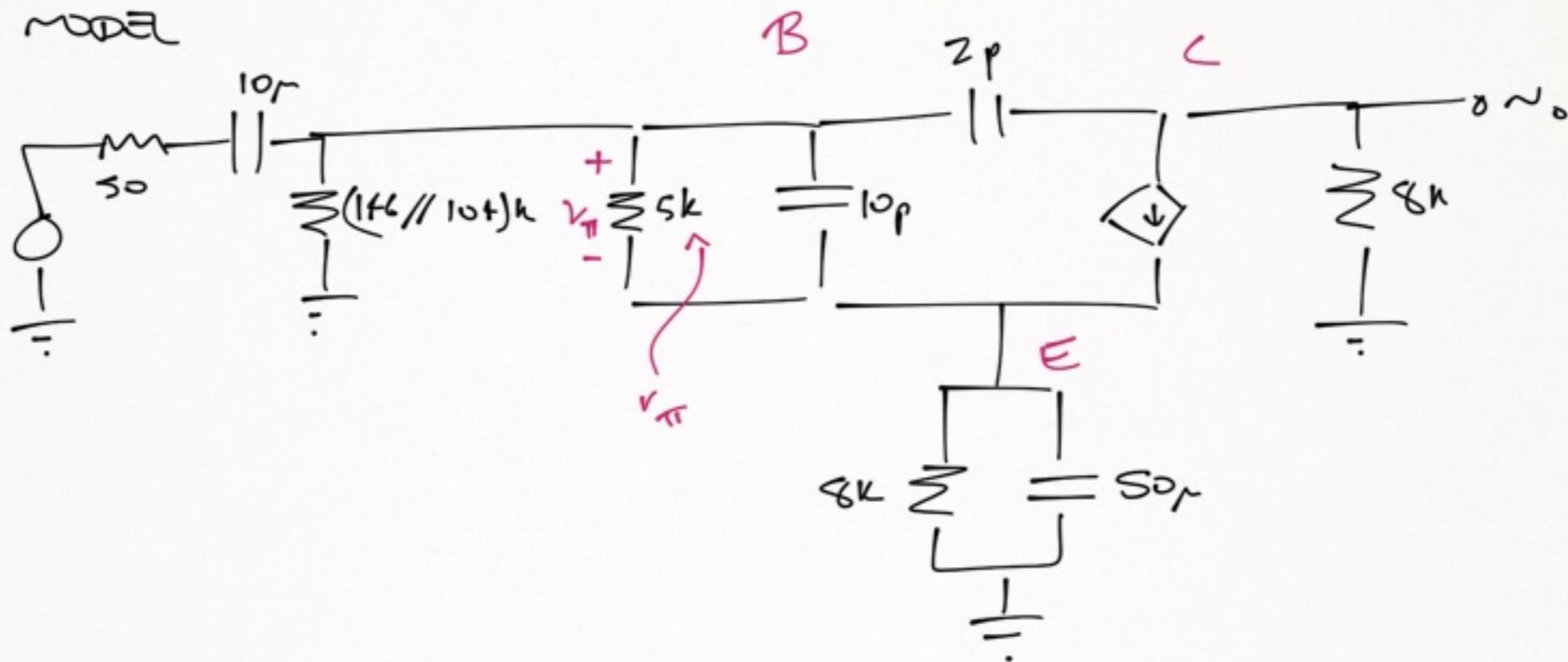


CALC. MIDBAND GAIN FIRST

↳ ALL CAPACITORS GONE


$10\mu F, 50\mu F \rightarrow$ SHORTS

$10 pF, Z_p \rightarrow$ OPEN CIRCS.

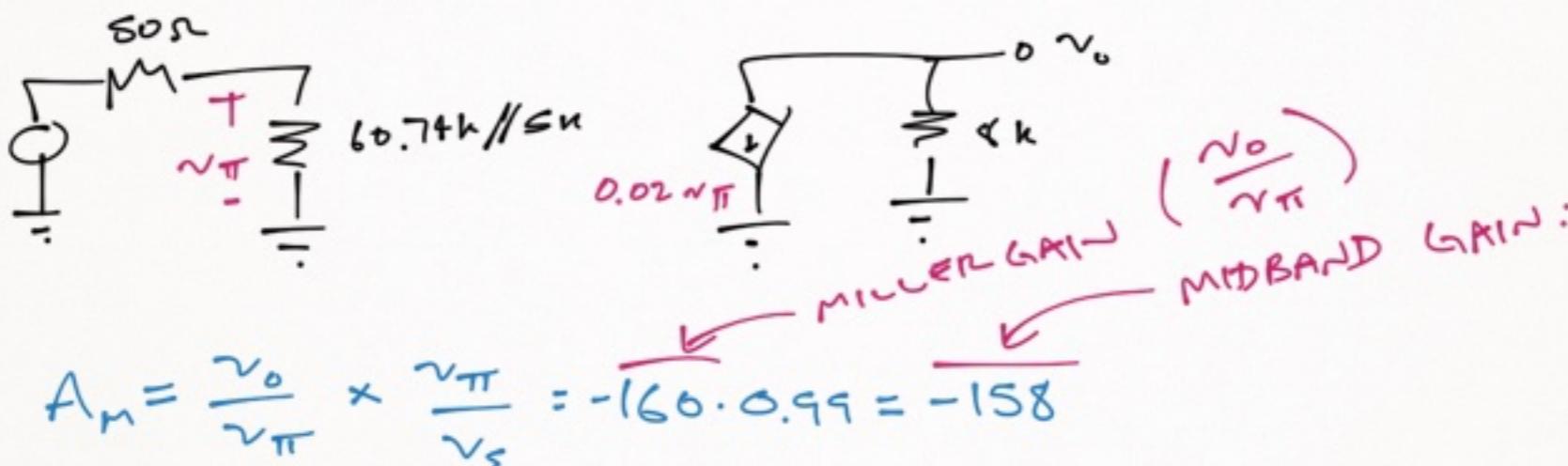


LOW FREQ.

don't care

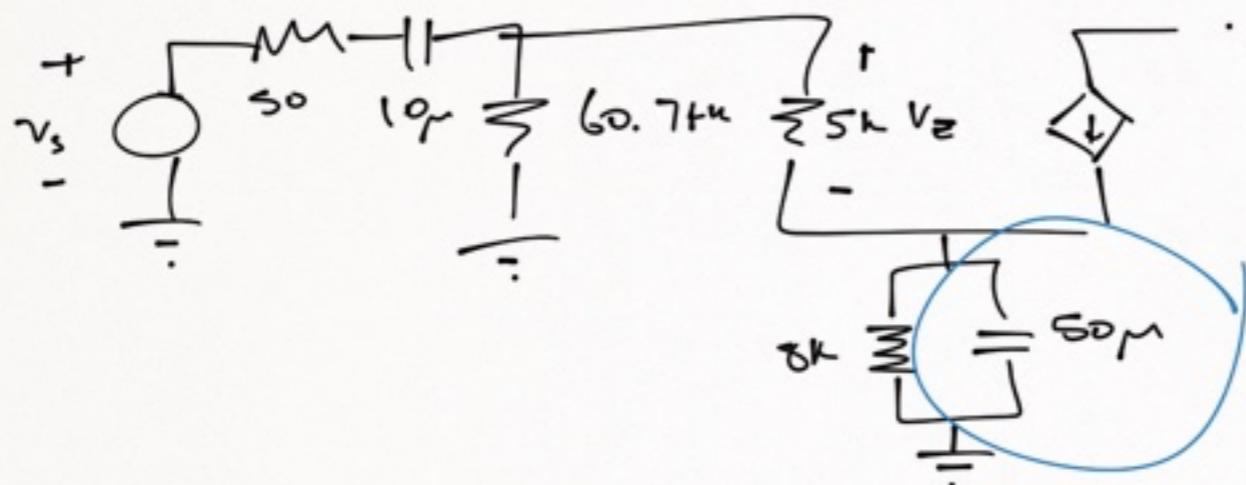

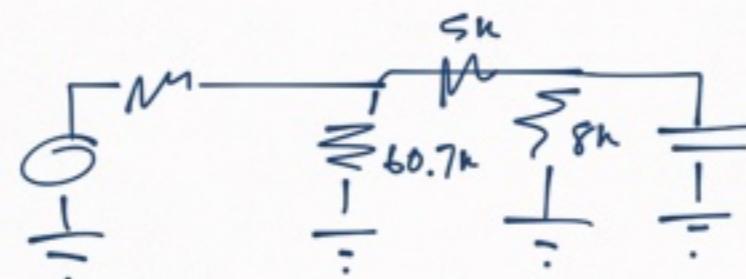- ① TRY short-circuit 10μ :: 50μ "sees" R ?



$$R = 8k \parallel \frac{5k + 60.7k \parallel 50\mu}{1+\beta}$$

$$v_{RL} = \frac{1}{R \cdot 50\mu} \approx \left(400 \frac{\text{rad}}{\text{s}}\right)$$

IF looking from Emitter to Base, everything looks

- ② TRY o.s. 50μ :: 10μ "sees"?

BASE TO Emitter, returning looks $\beta+1$ bigger

$$R = [60.7 \parallel (5k + 8k(\beta+1))] + 50 \approx 56.5k\Omega$$

$$\omega_{RL} = \frac{1}{10\mu \cdot 56.5k} = \left(1.8 \frac{\text{rad}}{\text{s}}\right)$$

VERY DIFF \neq CONSISTENT w/ ASSUMPTIONS
higher f goes w/ higher cap.

③ WHAT IF You short CE, som7 THEN 0.5 CC, 10μ

$$\omega_L = 21.4 \frac{m}{\mu},$$


ω_{DB} is highest freq. pole

$$T_{3dB} = \sqrt{T_{p1}^2 + T_{p2}^2}$$

ASSUME C_1 IS FIRST POLE \nmid CALC. ω

ASSUME C_2 IS FIRST POLE \nmid CALC. ω

WHICHEVER HAS LOWER ω , IS FIRST POLE

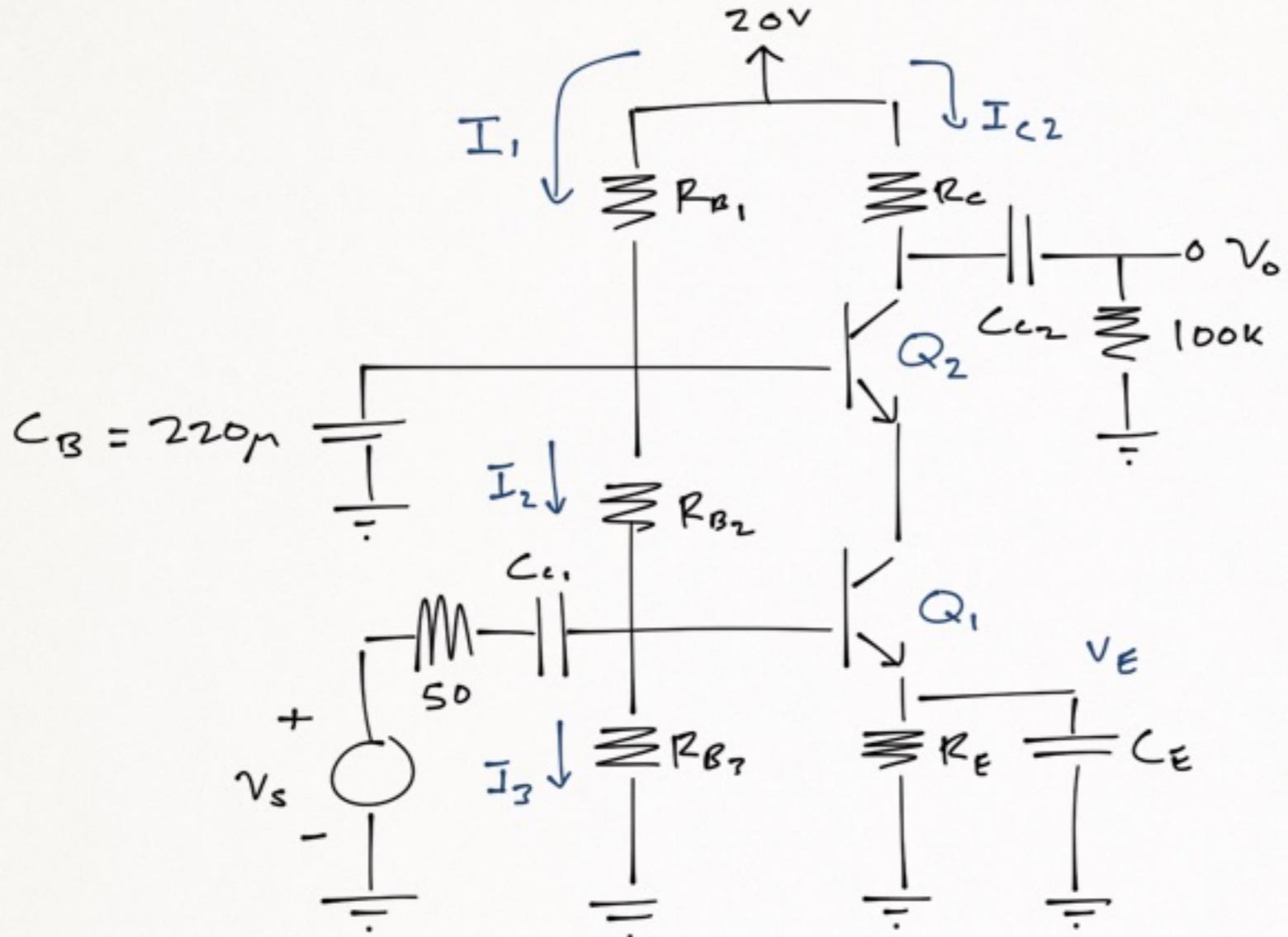

ASSUMPTIONS

$$R_c \approx R_E$$

$$V_{BE1} = V_{BE2} = 0.7V$$

$$I_1 = 0.1 I_E, \beta = 150$$

$$V_T = 26mV$$

FROM $\frac{1}{4}$ RULE

$$V_{C1} = \frac{1}{2} V_{CC} = \boxed{10V} = V_{E2}$$

$$V_{C2} = \frac{3}{4} V_{CC} = \boxed{15V}$$

$$V_{E1} = \frac{1}{4} V_{CC} = \boxed{5V}$$



$$V_{B1} = \frac{1}{4} V_{CC} + V_{BE} = \boxed{5.7V}$$

$$V_{B2} = \frac{1}{2} V_{CC} + V_{BE} = \boxed{10.7V}$$

$$I_{E1} \approx I_{C1} \approx I_{E2} \approx I_{C2}$$

$$G_{AV} = 45dB$$

AT MIDBAND

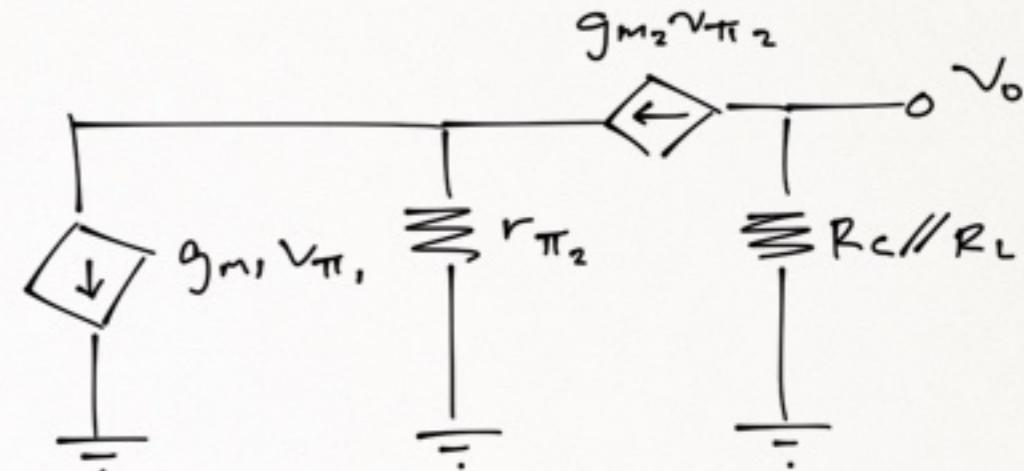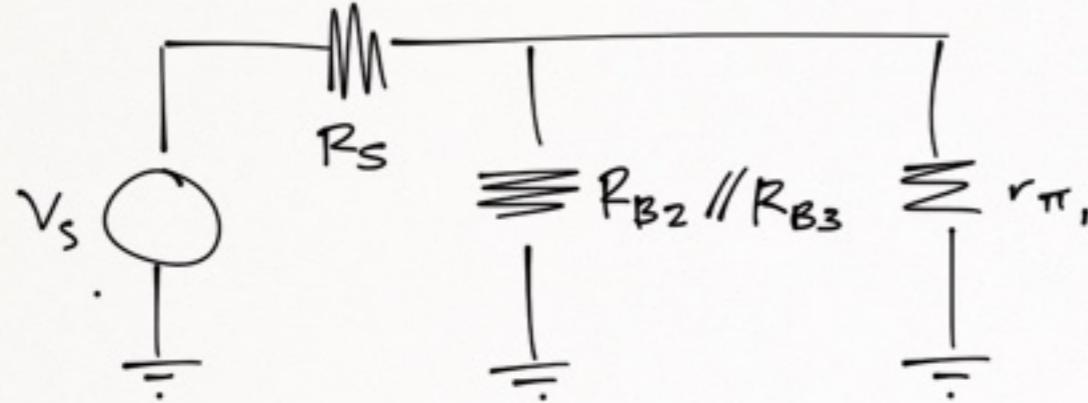

$$A_v = \frac{V_o}{V_i} = \frac{V_o}{V_{\pi_1}} \geq -50 \rightarrow \sim 34 \text{ dB}$$

$$V_{\pi_1} = V_{\pi_2}$$

MEASURED INPUT IMPEDANCE @ MIDBAND = $r_{in} = \frac{\text{measured } V_{in}}{\text{measured } i_{in}}$

$\left \begin{array}{l} \text{measured } V_{in} = 706 \mu\text{V} \\ \text{measured } i_{in} = 94.2 \text{nA} \\ \hline r_{in, \text{measured}} = 7.5 \text{k}\Omega \end{array} \right.$	$\left \begin{array}{l} V_s = 1 \text{ mA} \\ f = 50 \text{ Hz} \end{array} \right.$
--	---

$$I_{C2} = \frac{V_{cc} - V_{C2}}{R_C} = \frac{5V}{10k} = 500 \mu\text{A} \approx I_{C1} = I_E = I_{E2}$$

$$I_I = 0.1 \cdot I_E \approx 0.1 I_{C2} = 50 \mu\text{A}$$

$$R_{B1} = \frac{V_{B2} - V_{B1}}{I_{B1}} = \frac{20 - 10.7}{50 \mu} = \boxed{186 \text{k}\Omega}$$


$$I_{B1} = I_{B2} = \frac{I_{C1}}{\beta_1} = \frac{I_{C2}}{\beta_2} = \frac{500 \mu\text{A}}{100} = 5 \mu\text{A}$$

$$R_{B2} = \frac{V_{B2} - V_{B1}}{I_I - I_{B1}} = \frac{5}{45 \mu} = \boxed{111 \text{k}\Omega}$$

$$R_{B3} = \frac{V_{B1}}{I_I - 2I_{B1}} = \frac{5.7}{40 \mu} = \boxed{143 \text{k}\Omega}$$

$$R_E = \frac{V_E}{I_{E2} + 2I_B} = \frac{5}{510 \mu} = \boxed{9.8 \text{k}\Omega}$$

HIGH FREQ. MODEL

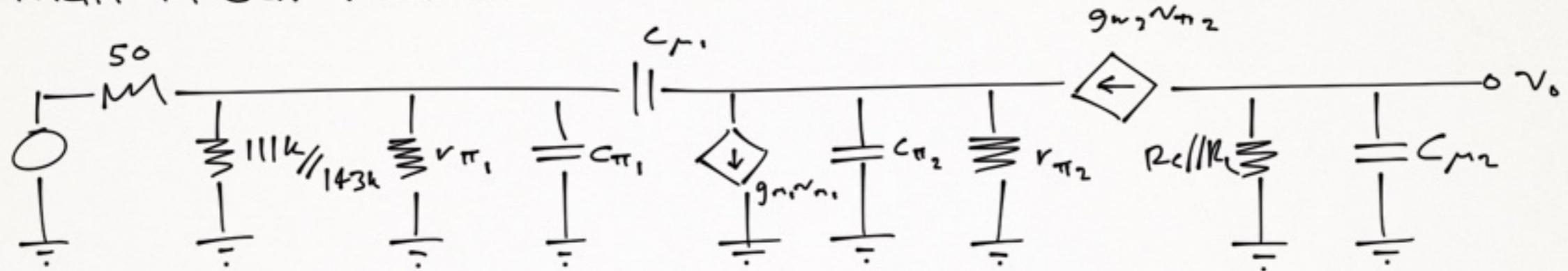

$$r_{\pi_1, 2 \text{ MEASURED}} = 7.33 \text{ k}\Omega$$


$$\omega_{np1} = \frac{1}{C_{\mu_2} R_c // R_L} = \frac{1}{8\rho (10k // 100k)} = \boxed{2.19 \text{ MHz}}$$

$$\omega_{np2} = \frac{1}{(C_{\pi_2} + 2C_{\mu_1}) \frac{r_{\pi_2}}{1+\beta}} = \frac{1}{(2S_p + 2\cdot 8_p) \left(\frac{7.33k}{1+100}\right)} = \boxed{53.5 \text{ MHz}}$$

$$\begin{aligned} \omega_{np3} &= \frac{1}{(R_s // R_{B2} // R_{B3} // r_{\pi_1})(C_{\pi_1} + 2C_{\mu_1})} = \frac{1}{(50 // 110k // 140k // 7.33k)(2S_p + 2\cdot 8_p)} \\ &= \boxed{78.2 \text{ MHz}} \end{aligned}$$


MEASURED VALUES

MIDBAND GAIN ~ 45 dB

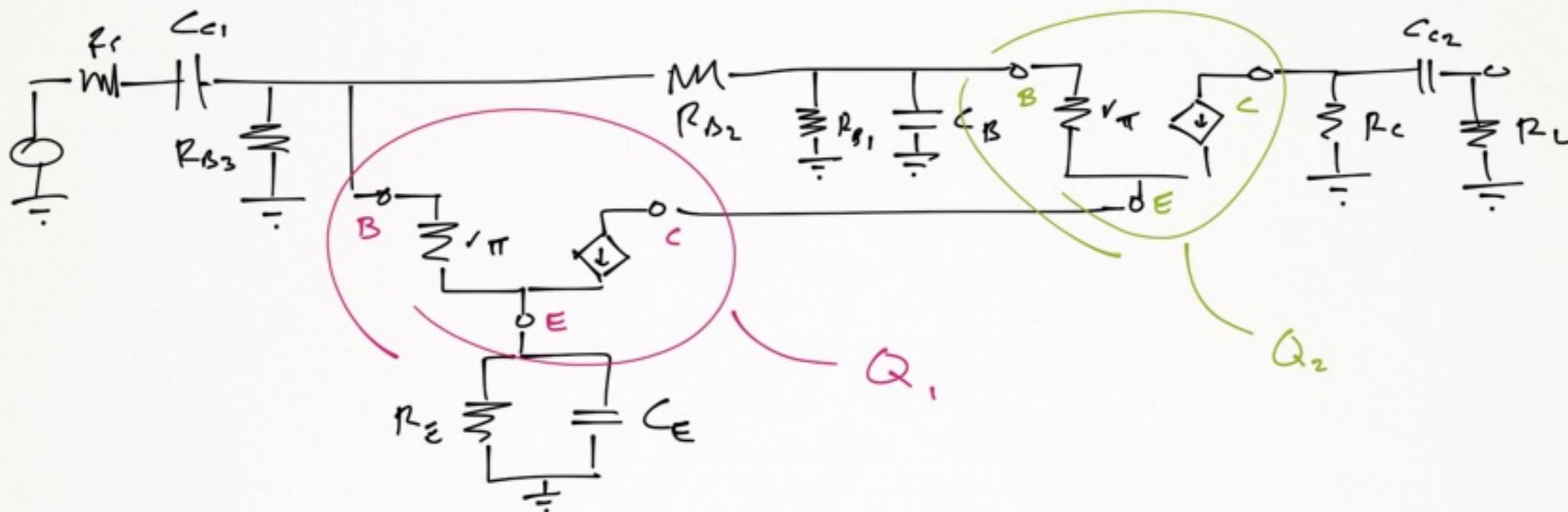

LOW FREQUENCY ANALYSIS
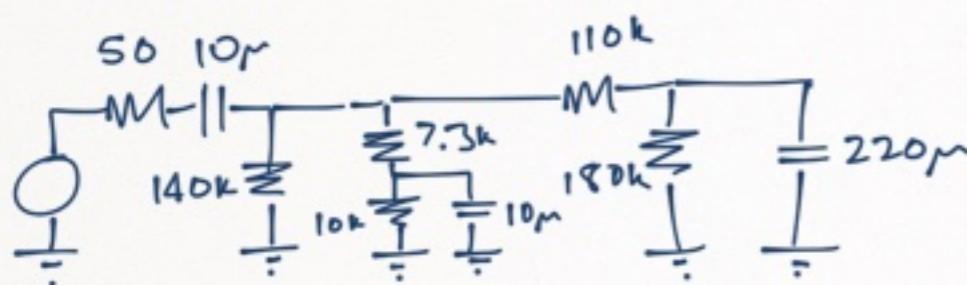
$$\omega_{LP1} = \frac{1}{C_{C2}(R_C + R_L)} = \frac{1}{10\mu(10k + 100k)} = 909 \text{ rad/s} = 145 \text{ mHz}$$



OPENING $C_{C1} \neq C_E$

$$\begin{aligned} \omega_{PH1} &= \frac{1}{C_E [(R_{B3}/(r_\pi + R_E) + R_{B2})/R_{S1}]} \\ &= \frac{1}{220\mu [(140k/17.3k + 110k)/180k]} \\ &= 61.46 \text{ rad/s} = 9.78 \text{ mHz} \end{aligned}$$

SHORTING $C_B \neq$ OPENING C_E

$$\begin{aligned} \omega_{PH2} &= \frac{1}{C_{C1} [R_{B2}/(r_\pi + (\beta+1)R_E) / (R_{B3} + R_S)]} \\ &= \left(10\mu [110k/(7.3k + 101 \cdot 10k)] / 140k + 50 \right)^{-1} \\ &= 1.72 \text{ rad/s} = 274 \text{ mHz} \end{aligned}$$

1. BIAS USING ①, FIND Q
2. BIAS USING ②, FIND Q
3. BIAS USING ③, FIND Q

$$r_{\pi} = 4.2 \text{ k}\Omega$$

$$r_o = 107.5 \text{ k}\Omega$$

$$\beta = 167.1$$

k_3 RULE BIAS SAME FOR ALL TRANSISTORS

2N3904

$$m = \frac{(1.18 - 1.35) \mu}{(1.05 - 1.62)} = 11.667 \mu \frac{\text{A}}{\text{V}}$$

$$y = mx + b$$

$$1.352 \cdot 10^{-3} = (11.667 \mu)(1.62) + b$$

$$1.1628 \cdot 10^{-3} = b$$

$$-V_A = x = \frac{-1.1628 \mu}{11.667 \mu} = 99.62$$

$$r_o = \frac{99.66}{1 \mu} = \boxed{99.66 \text{ k}\Omega}$$

$$\beta = \frac{1 \text{ mA}}{I_B} = \frac{1 \mu}{8.12 \mu}$$

$$= \boxed{123.14}$$

$$r_{\pi} = 123.14 \cdot 25 \mu = \boxed{3.10 \text{ k}\Omega}$$

$$m = \frac{3.819\mu - 4.360\mu}{2.434 - 18.21} = 34.293\mu \frac{A}{V}$$

$$y = mx + b$$

$$(3.819\mu) = (34.293\mu)(2.434) + b$$

$$b = 3.7234 \text{ m}$$

$$-V_A = x = \frac{-b}{m} = \frac{-3.7234 \text{ m}}{34.293\mu} = \boxed{108.57k}$$

$$\beta = \frac{I_C}{I_R} = \frac{1\text{mA}}{6.53\mu\text{mA}} = \boxed{153.12}$$

$$r_\pi = \beta \frac{25.2\text{mV}}{1\text{mA}} = 153.12 \frac{25.2\text{mV}}{1\text{mA}} = \boxed{3.86k}$$

23904 BIAS #1

$$I_B = \frac{I_{MA}}{\beta} = \frac{1mA}{123.1} = 8.12\mu A$$

$$\begin{aligned}V_C &= 10.02 \\V_B &= 5.7207 \\V_E &= 5.0202 \\R_E = R_C &= 4.9795k\end{aligned}$$

$$\begin{aligned}R_{B1} &= 102.96k \\R_{B2} &= 69.75k\end{aligned}$$

$$V_B = 6.0578 V$$

$$I_Q = 1.0081 mA$$

$$V_Q = 15 - I_Q(R_C + R_E) =$$

$$V_Q = 4.9595$$

24401 BIAS #1

$$I_B = \frac{I_{MA}}{153.1} = 6.53\mu A$$

$$V_C = 10.016$$

$$V_B = 5.7103$$

$$V_E = 5.0163$$

$$R_C = R_E = 4.9837k$$

$$V_Q = V_C - I_Q(R_C + R_E) = 4.9695$$

$$R_{B1} = 114.87 k$$

$$R_{B2} = 76.947 k$$

$$V_B = \frac{R_{B2}}{R_{B1} + R_{B2}} \cdot V_C = 6.0172$$

$$I_Q = \frac{V_B - V_{BE}}{\frac{R_{B1} // R_{B2}}{\beta + 1} + R_E} = 1.0063 mA$$

FOR BOTH TRANSISTORS:

2d)

COMPARE:

BODE POLES + ZEROS
CALC. POLES + ZEROS

PICK MIDBAND FREQ
→ DO SATURAT. + TURB

$$\omega_{P1L} = \frac{1}{C_{c2}(3.1k+M)} = 15.8 \text{ Hz}$$

$$\omega_{P2L} = \frac{1}{[R_s + R_{B2} \parallel (r_\pi + (1+\beta)R_e)] C_{c1}} = 483 \text{ Hz}$$

$$\omega'_{P2L} = \frac{1}{\left(R_e \parallel \frac{r_\pi + R_{B2} \parallel R_s}{1+\beta} \right) C_e} = 630 \text{ Hz}$$

$$\omega_{z3L} = \frac{1}{R_e C_e} = 3.12 \text{ Hz}$$

$$\omega_{HP2} = \frac{1}{R_L \parallel R_C \cdot C_B} = 3.92 \text{ MHz}$$

$$\omega_{HP1} = \frac{1}{[C_\pi + g_m (1 + \frac{\beta}{r_\pi} R_L \parallel R_C)] (R_L \parallel R_B)}$$

$$r_\pi = 3.16 k$$

$$V_o = 79.6 \text{ mV}$$

$$\beta = 123.1$$

$$r_{T1} = 3.86 k$$

$$r_o = 108.1 k$$

$$\beta = 153.1$$

$$89.17 \text{ kHz}$$

$$86.82 \text{ kHz}$$

5th ed. pg 490

$$C_{\pi} = C_{de} + C_{je}$$

$$C_{de} = \pi_F g_m$$

$$C_{je} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{V_{Oe}}\right)^m}$$

FAIRCHILD DATASHEETS

$$g_m = \frac{I_c}{V_T} \quad r_o = \frac{|V_A|}{I_c} \quad r_{\pi} = \frac{\beta_0}{g_m}$$

$$C_{je} \equiv 2 C_{je0}$$

$$C_m = \frac{C_{je0}}{\left(1 + \frac{V_{CE}}{V_{Oe}}\right)^m}$$

2N2222A

$$C_m = \frac{C_{jco}}{\left(1 + \frac{V_{CB}}{V_{OC}}\right)^m}$$


$$C_{\pi} = \frac{g_m}{2\pi f_T} - C_m$$

↑
unity gain
bandwidth

(DATASHEET)

FUNCTION OF $I_C + V_{CE}$

TRY SHORTING $C_B \neq C_C$

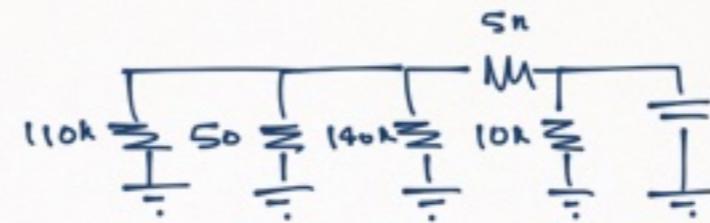

$$\omega_{HP3} = \frac{1}{C_E \left[\frac{(R_S // R_{B2} // R_{B1}) + r_T}{\beta + 1} // R_E \right]} = \frac{1}{10\mu \left[\frac{(50 // 140k // 110k) + 7.3k}{101} // 10k \right]} = 23.7 \frac{rad}{s} = [3.77 \text{ Hz}]$$


TRY SHORTING $C_B \neq$ OPENING C_C

$$\omega_{HP3} = \frac{1}{C_E \left[\frac{(R_{B2} // R_{B1}) + r_T}{\beta + 1} // R_E \right]} = \frac{1}{10\mu \left[\frac{(140k // 110k) + 7.3k}{101} // 10k \right]} = 22.6 \frac{rad}{s} = [3.60 \text{ Hz}]$$

POLE CORRESPONDING TO C_E IS AT $\boxed{\sim 3.7 \text{ Hz}}$

DON'T DO $\frac{V_T}{I_C}$ 'S ROLE ON BIASED/PREVIOUSLY DESIGNED CIRCUITS

Ex) How to:

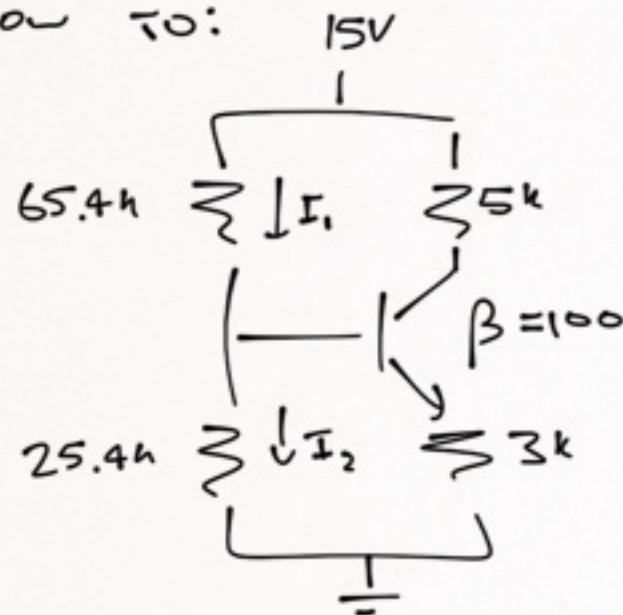

FIND $I_1, I_2, I_c, I_e, g_m, \text{ and } r_\pi$

DO THEV. OR LEFT SIDE OF CIRCUIT:

$$V_{BB} = 15V \cdot \frac{25.4k}{65.4k + 25.4k} = 4.2V$$

$$R_{BB} = 65.4k / 25.4k = 18.3k$$

TO GET $I_1 \neq I_2$

$$V_E = R_E \cdot I_E = 3k \cdot 1.11mA = 3.33V$$


$$V_B = V_E + 0.7 = 4.03V \approx 4V$$

$$I_1 = \frac{15 - V_B}{65.4k} = \frac{15 - 4V}{65.4k} = 0.165mA$$

$$I_2 = \frac{4V}{25.4k} = 0.157mA$$

$$g_m = \frac{I_C}{V_T} = \frac{1.1mA}{25mV} = 44mS$$
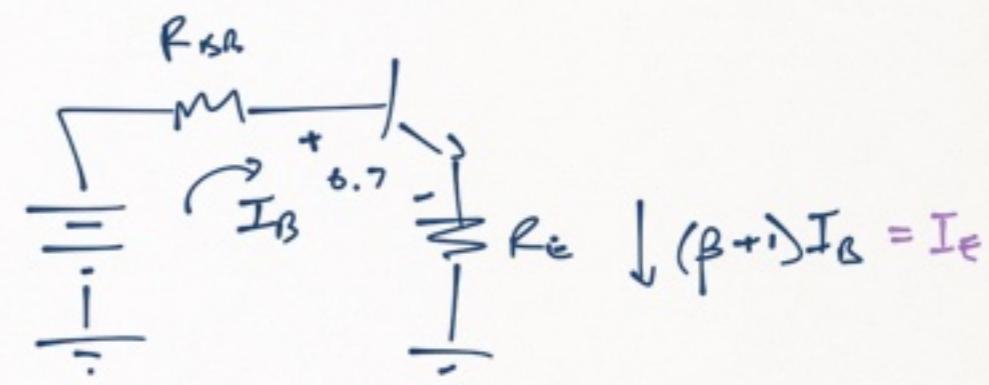
$$r_\pi = \frac{V_T}{I_C} = \frac{100}{44mS} = 2.27k$$




$$V_{BB} = I_B R_{BB} + 0.7 + (1+\beta) I_B R_E$$

$$I_B = \frac{V_{BB} - 0.7V}{(1+\beta) R_E + R_{BB}} = \frac{3.5V}{30.3k + 18.3k} = 11\mu A$$

$\uparrow \quad \uparrow \quad \uparrow$
100 3k 18.3k

$$I_C = \beta I_B = 1.1mA$$

$$I_E = (1+\beta) I_B = 1.11mA$$

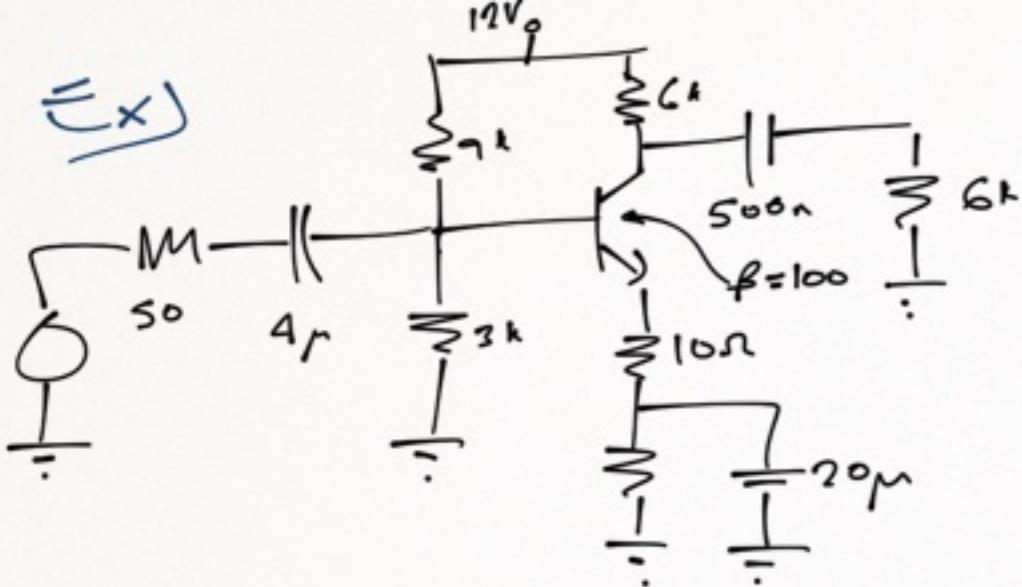


DRAW LOW F CIRCUIT, MIDBAND,
AND HIGH F CIRCUIT.

= PERIODE MIDBAND GAIN $A_m \neq F_1(s)$

$$V_{BB} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}} = 12 \cdot \frac{3}{9+3} = 6V$$

$$R_{BB} = 9k \cdot \frac{3}{9+3} = 2.25k$$
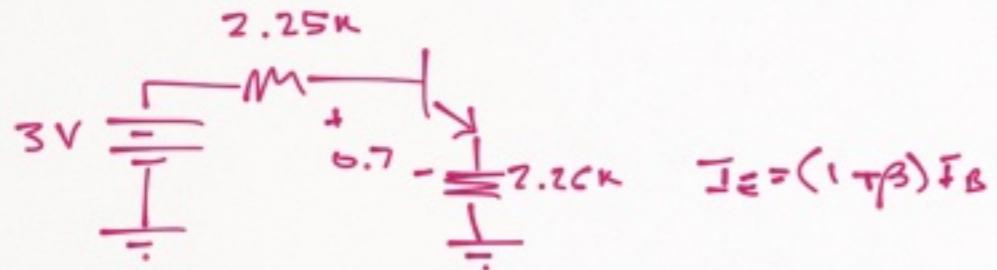
$$R_{B1} // R_{B2} = R_{B1} \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right)$$



$$I_B = \frac{V_{BB} - V_{BE}}{(1+\beta)R_E + R_{BB}} = \frac{7.3V}{(101 \cdot 2.25k) + 2.25k} \approx 10\mu A$$

$$I_C = 1mA$$


$$g_m = 40mS = \left(\frac{I_C}{V_T} = \frac{1mA}{25mV} \right)$$

$$r_{\pi} = 2.5k$$



Ex Cont'd

MIDBAND

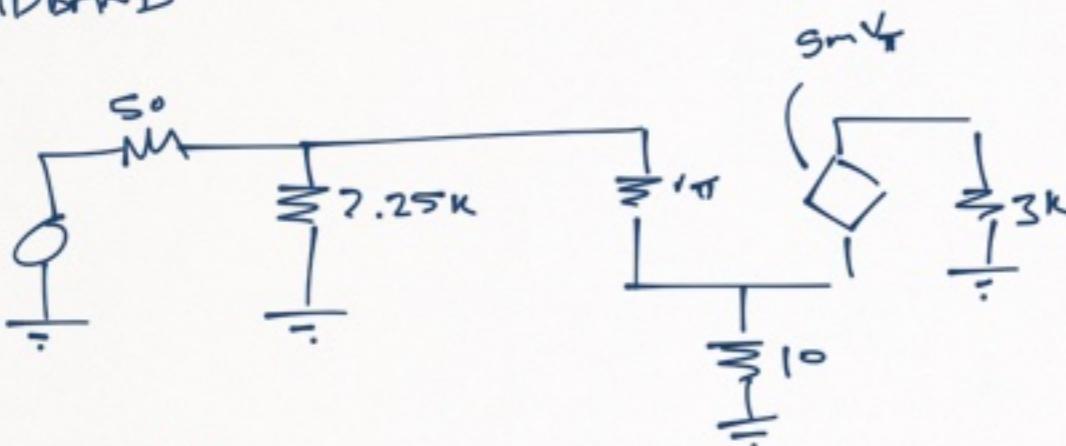

POLES?

$$\text{POLE FOR } 500\text{rF JAP} = \frac{1}{500\text{rF} \cdot 12k}$$

$$\text{POLE FOR } 4\mu\text{F CAP} = \frac{1}{4\mu\text{F}(50 + 2.25k)} \quad (?)$$

$\hookrightarrow \text{O.S. } 20\mu$ $\approx 3k/50 \approx 50$

$$\text{POLE FOR } 20\mu\text{F CAP} = \frac{1}{20\mu\text{F}(2.25k/\parallel [10 + 1\pi + 2.25k/50])} \quad |_{101}$$

ZEROS?

Look AT WHEN $I_B = \phi$

WHEN ADMITTANCE $T = R_E + jC_E = \beta$
($y_E = \phi$)

$$\therefore I_B = \phi$$

$$\omega_z = \frac{1}{20\mu\text{F} \cdot 2.25k}$$

$B \rightarrow E$

$\sim \sim \sim \sim \sim \sim$ ✓ 1

$C_{C_1} \neq C_{C_2}$ DON'T LET ANY I THROUGH
AT DC \therefore THEIR ZEROS ARE AT ZERO

$$V_T = V_R \cdot \frac{r_T}{r_T + (1+\beta)10} = 0.712 \cdot V_B$$

\uparrow
MAGNIFYING
LOOKING INTO
EMITTER

$$V_o = -g_m \cdot 3k = -120 V_T$$

$$V_B = V_s \cdot \frac{2.25k/3.51k}{50 + 2.25k/3.51k} = V_s \cdot \frac{1.38}{1.43}$$

$$A_M = \frac{V_o}{V_s} = \frac{V_o}{V_T} \cdot \frac{V_T}{V_B} \cdot \frac{V_B}{V_s}$$

$$= -120 \cdot 0.712 \cdot \frac{1.38}{1.43} = -82 \frac{V}{V}$$

MIDTERM #1 REVIEW


AC { DC SOURCES APPEAR LIKE GROUNDS
@ HIGH FREQUENCY \rightarrow CAPACITOR IS SHORT
@ LOW FREQUENCY \rightarrow CAPACITOR IS BREAK

DC \rightarrow @ SS CAPACITORS ARE OPEN CIRCUITS

- PASSIVE DEVICES WORK AT ANY VOLTAGE/CURRENT
 - ex. RESISTORS, CAPACITORS
- ACTIVE DEVICES NEED CERTAIN VOLTAGES/CURRENTS TO WORK RIGHT (BIASING)
 - ex. TRANSISTORS

TRANSISTOR REVIEW

- NO MOVING PARTS, INCREDIBLY TINY

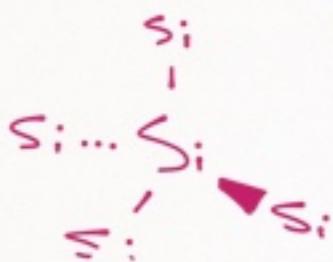

Si has 4 VALENCE e^- \therefore FORMS TETRAHEDRAL CRYSTAL


\rightarrow Si HAS ALL BONDED, NOT MANY FREE e^- \therefore PURE Si IS NOT CONDUCTIVE

\rightarrow DOPED w/ PHOSPHORUS (5 VALENCE e^-) \therefore EXTRA FREE e^- TO CONDUCT

\rightarrow N-TYPE ("moving Negative charge")

\rightarrow DOPED w/ BORON (3 VALENCE e^-) \therefore EXTRA H^+ FOR e^- TO MOVE

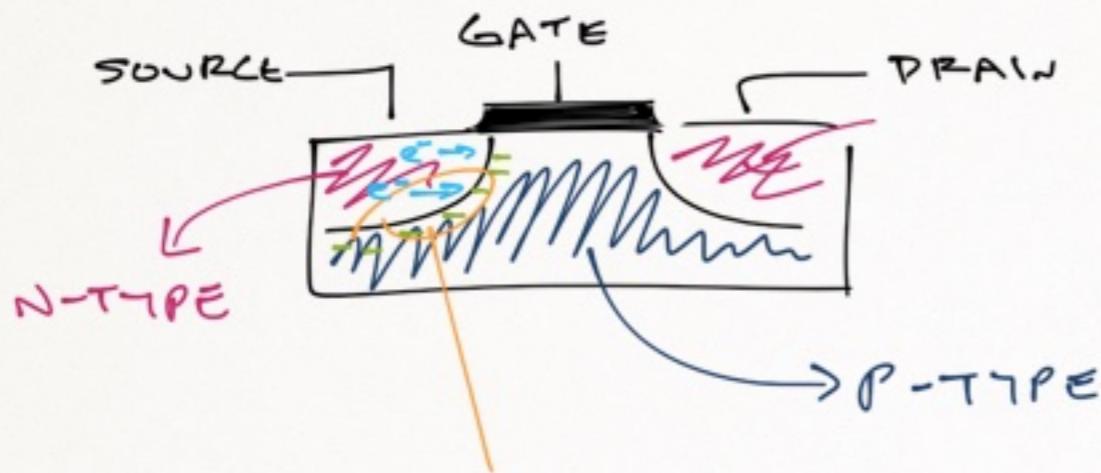\rightarrow P-TYPE ("moving Positive charge")



DEPLETION LAYER

→ WHERE ALL FREE e^- IN N-TYPE HAVE FILLED NEARBY h^+ IN P-TYPE

↳ THIS RESULTS IN P-TYPE BEING NEGATIVELY CHARGED
AND REPELLING ANY MORE e^- DRAIN OFFERS

↳ "OPEN CIRCUIT"


↳ HOWEVER, IF YOU APPLY +VOLTAGE FROM GATE
THEN NEGATIVE CHARGE BALANCED $\neq e^-$ FROM
SOURCE ATTRACTED \neq DEPLETION LAYER SHRINKS

→ SO e^- CAN MOVE TO h^+ IN AREA
NEXT TO GATE CREATING A CONNECTION
B/W SOURCE \neq DRAIN

↳ "SHORT CIRCUIT"


NOTES PRE MIDTERM #1

COMMON-Emitter
AMPLIFIER

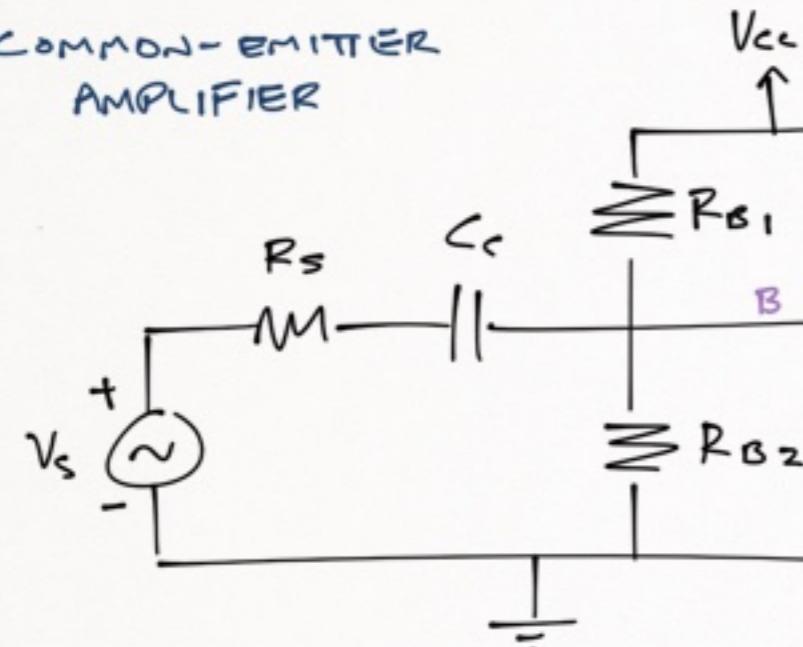


WHEN MODELING SMALL SIGNAL EQUIVALENT CIRCUIT, DC SOURCE IS SEEN AS GROUND BY AC

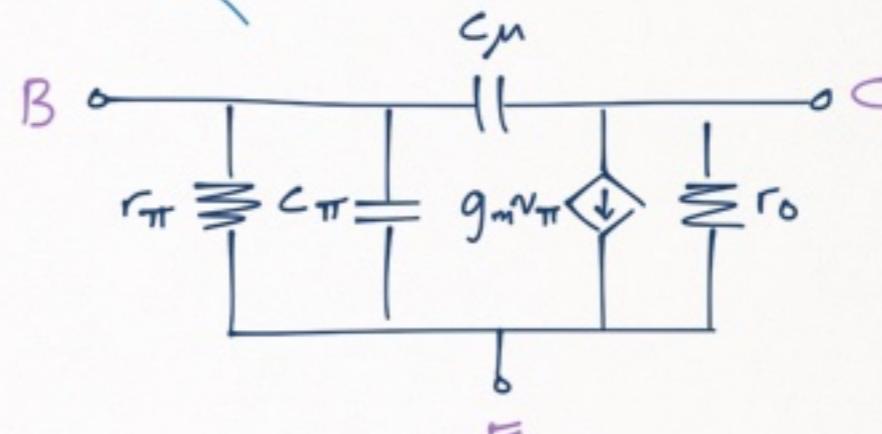
FOR TRANSISTORS, WE USE THE HYBRID-\$\pi\$ SMALL SIGNAL MODEL




SMALL SIGNAL MODEL

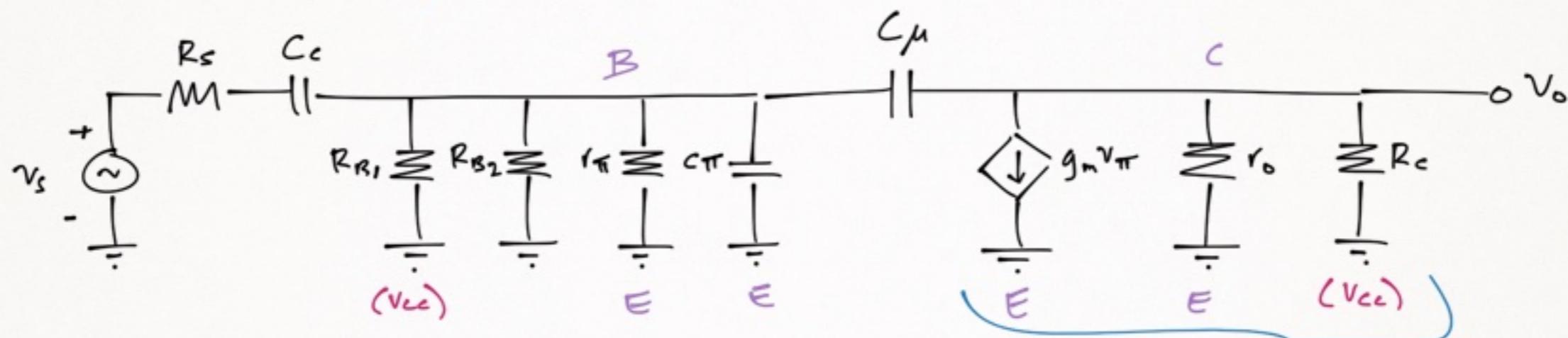

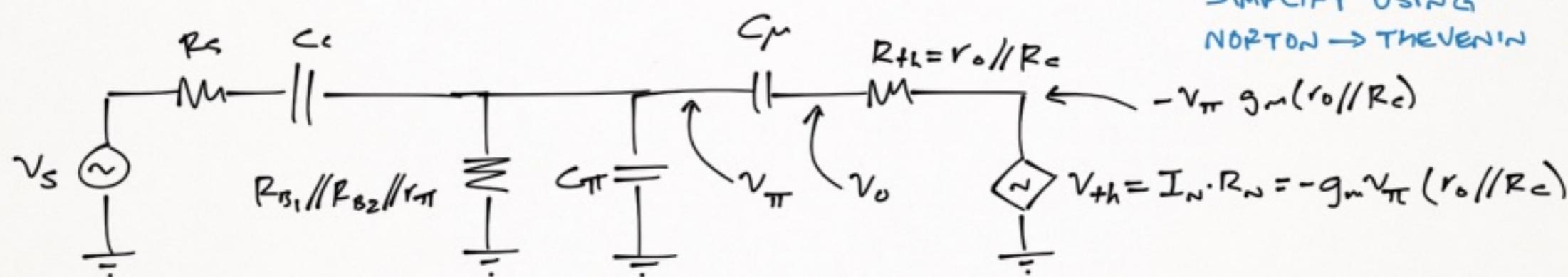SIMPLIFY USING
NORTON \$\rightarrow\$ THEVENIN



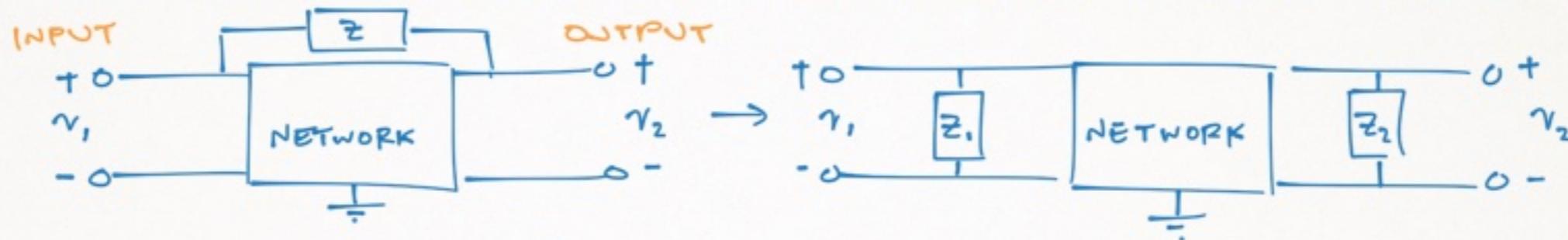REMOVE CAPACITOR SEPARATING BRANCHES USING MILLER'S THEOREM



$$\text{MILLER'S GAIN, } k = \frac{v_2}{v_1}$$

$$z_1 = z \frac{1}{1-k}$$


$$z_2 = z \frac{k}{k-1}$$

$$z = \frac{1}{j\omega C_\mu} + r_o // R_c$$

$$z_1 = \frac{z}{1-k} = \frac{\frac{1}{j\omega C_\mu} + r_o // R_c}{1-k}$$



$$k = \frac{v_2}{v_1} = \frac{-\gamma_\pi g_m(r_o // R_c)}{\gamma_\pi} = -g_m(r_o // R_c)$$

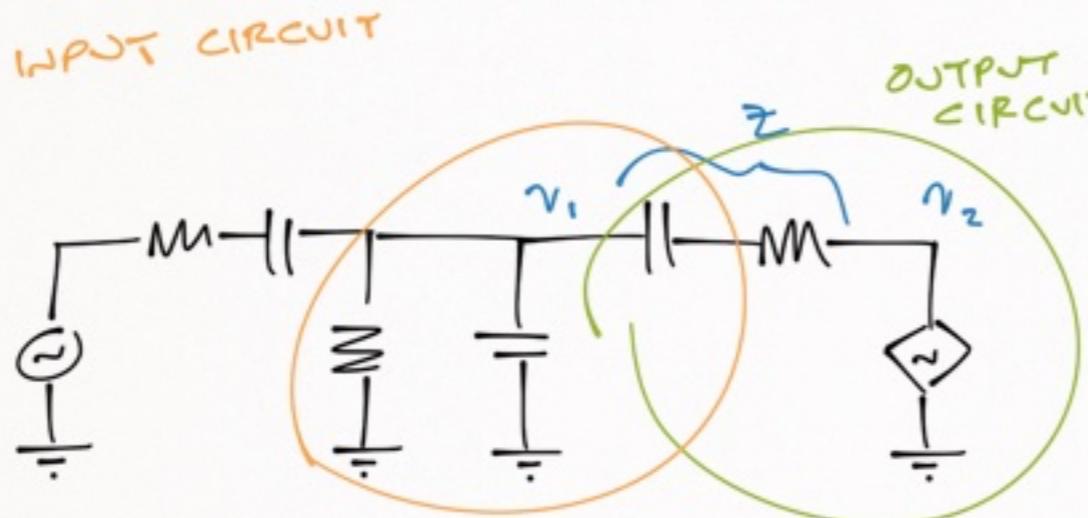
$$\begin{aligned} &= \frac{1}{j\omega C_\mu(1-k)} + \frac{r_o // R_c}{1-k} \\ &= \boxed{\frac{1}{j\omega C_\mu(1+g_m(r_o // R_c))} + \frac{r_o // R_c}{1+g_m(r_o // R_c)}} \end{aligned}$$





$$z_2 = z \frac{k}{k-1} = \frac{z}{1 - \frac{1}{k}}$$
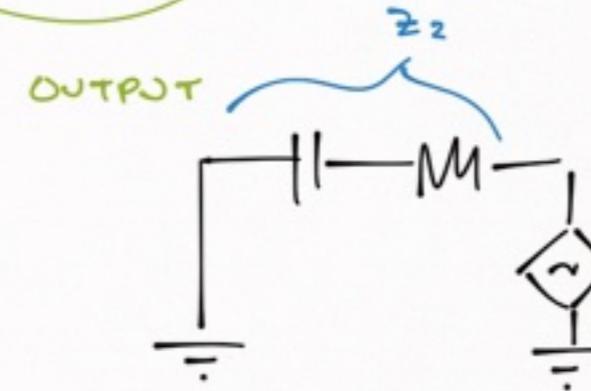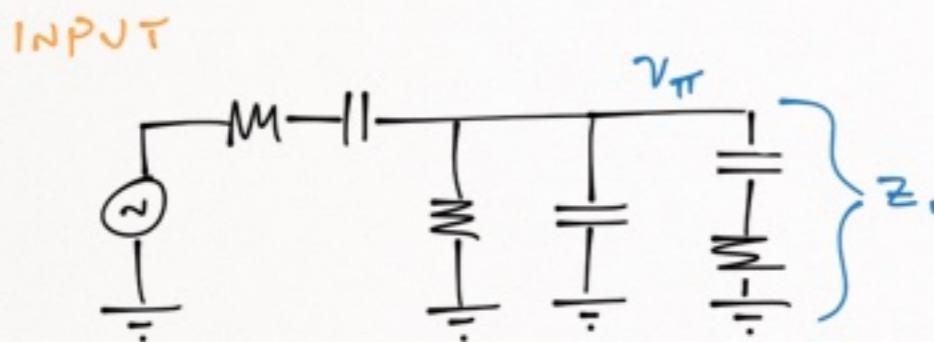
$$= \boxed{\frac{1}{j\omega C_\mu(1 - 1/k)} + \frac{r_o // R_c}{1 - 1/k}}$$





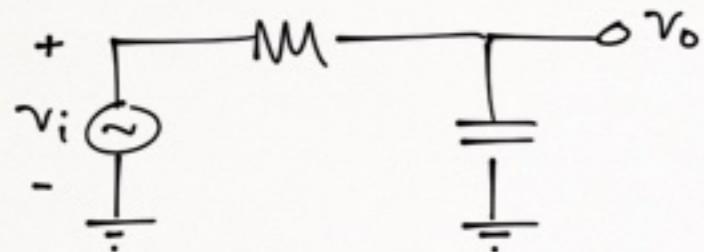

LOW PASS FILTER

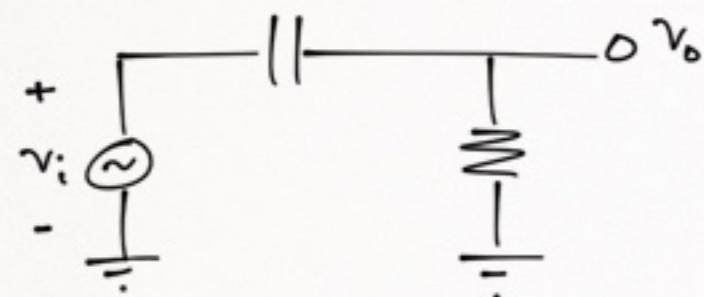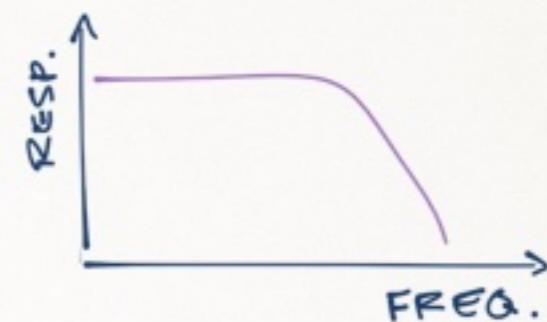


HIGH PASS FILTER

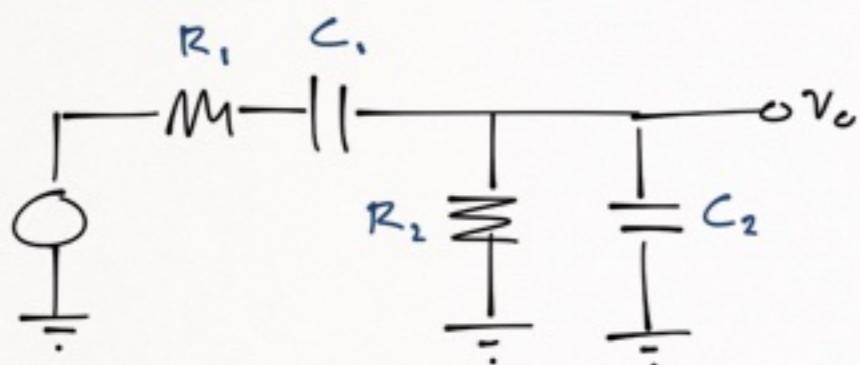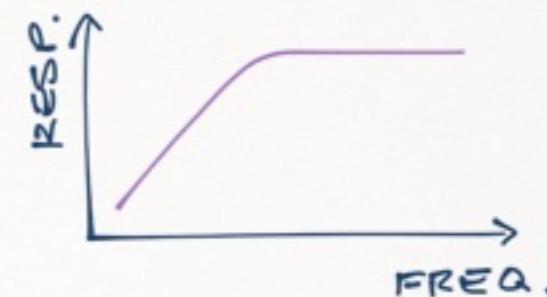

BAND PASS FILTER

$C_1 \gg C_2$ REQUIRED

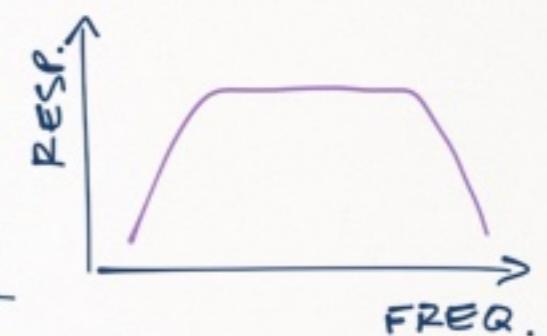

@ HIGH FREQ, LARGE C = SHORT CIRCUIT




→ HIGH PASS

BANDPASS POLES

$$\omega_{p_1} \approx \frac{1}{C_1(R_1 + R_2)}$$

$$\omega_{p_2} \approx \frac{1}{C_2(R_1 // R_2)}$$

@ LOW FREQ, SMALL C = OPEN CIRCUIT

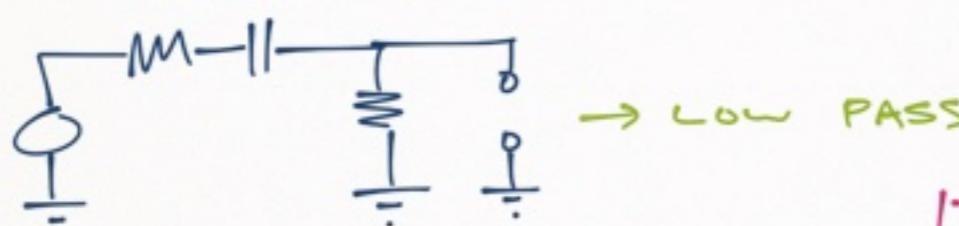

→ LOW PASS


DC GAIN

$$A_M = \frac{R_2}{R_1 + R_2}$$

TRANSFER FUNCTION

$$T(s) = \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \cdot \frac{s}{s + \omega_{p_1}} \cdot \frac{\omega_{p_2}}{s + \omega_{p_2}}$$

FREQUENCY RESPONSE

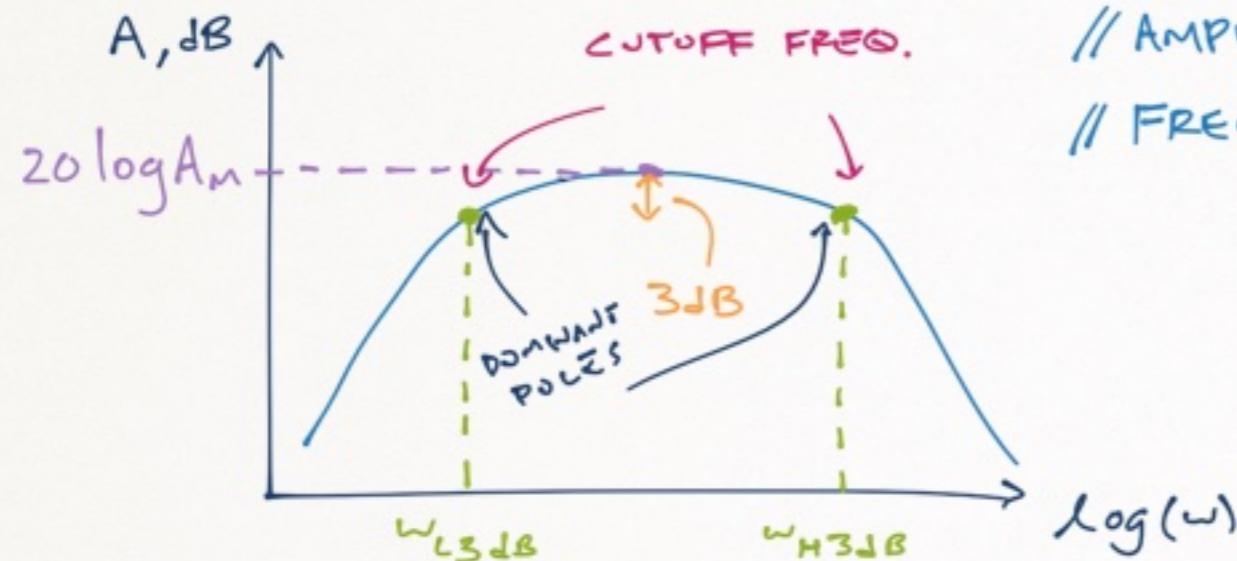

// AMPLIFIERS CAN AMPLIFY MANY DIFFERENT
// FREQUENCIES SIMULTANEOUSLY ex. MUSIC

IF YOU KNOW THE LOCATIONS
OF THE POLES ≠ ZEROS, YOU CAN
APPROXIMATE THE CUTOFF FREQUENCIES.

$$\omega_{L3dB} = \sqrt{\omega_{P1L}^2 + \omega_{P2L}^2 \dots + \omega_{PNL}^2 - 2\omega_{z1L}^2 - 2\omega_{z2L}^2 \dots - 2\omega_{zNL}^2}$$

$$\frac{1}{\omega_{H3dB}^2} = \frac{1}{\omega_{P1H}^2} + \dots + \frac{1}{\omega_{PNH}^2} - \frac{2}{\omega_{z1H}^2} - \dots - \frac{2}{\omega_{zNH}^2}$$

IF YOU DON'T KNOW THE POLES/ZEROS USE OPEN-CIRCUIT/CLOSED-CIRCUIT
TIME CONSTANT METHOD


$$\omega_{L3dB} \approx \sum_{i=1}^n \frac{1}{C_i R_{iL}}$$

R_{iL} IS THE RESISTANCE
SEEN BY THE ith LOW-FREQUENCY CAPACITOR
↳ ie. large
ALL OTHERS BEING SHORTS

$$\omega_{H3dB} \approx \frac{1}{\sum_{i=1}^n C_i R_{iH}}$$

R_{iH} IS THE RESISTANCE
SEEN BY THE ith HIGH-FREQUENCY CAPACITOR
↳ ie. small
ALL OTHERS BEING BREAKS

BJT

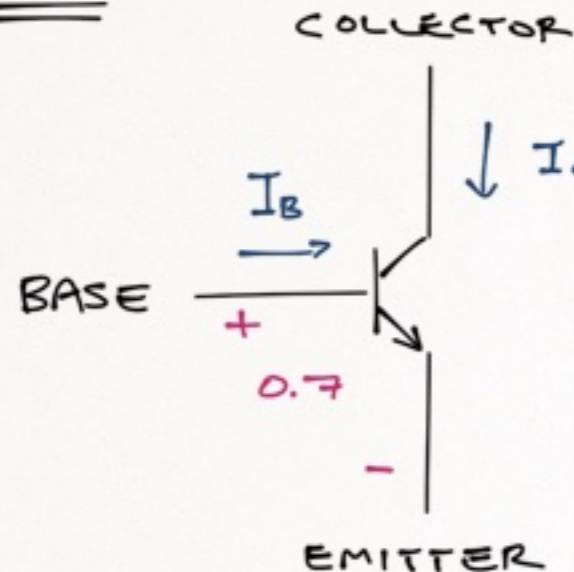

TRANSISTOR PARAMETERS current gain factor

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$V_T = 25 \text{ mV}$
(@ $T = 300 \text{ K}$)
thermal voltage

$$V_{BE} = 0.7$$

$$\beta = 100$$

(FOR Si BJT) (UNLESS TOLD OTHERWISE)

NOTATION:
 $A_B \rightarrow \text{DC VALUE}$
 $A_b \rightarrow \text{COMPLEX VALUE}$
 $a_b \rightarrow \text{INSTANTANEOUS VALUE}$
 $\alpha_b \rightarrow \text{SMALL SIGNAL AC VALUE}$


ex. $i_c = I_c + i_c$

HYBRID-PI MODEL FOR BJT


$$r_\pi = \frac{V_{be}}{i_L} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

$$r_o = \left[\frac{s}{sV_{CE}} \frac{i_c}{V_{BE} = \text{constant}} \right]^{-1} \approx \frac{V_A}{I_C}$$

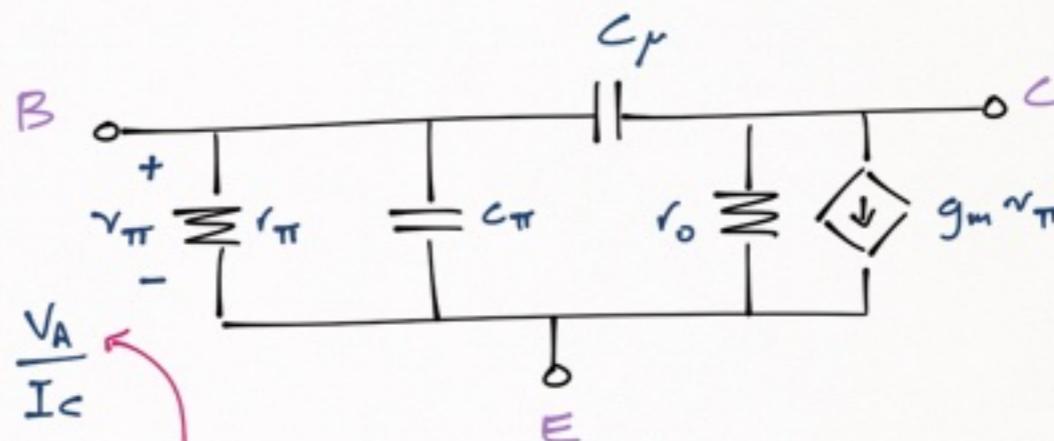much of the time,
we can get away with
assuming this is infinite




early voltage

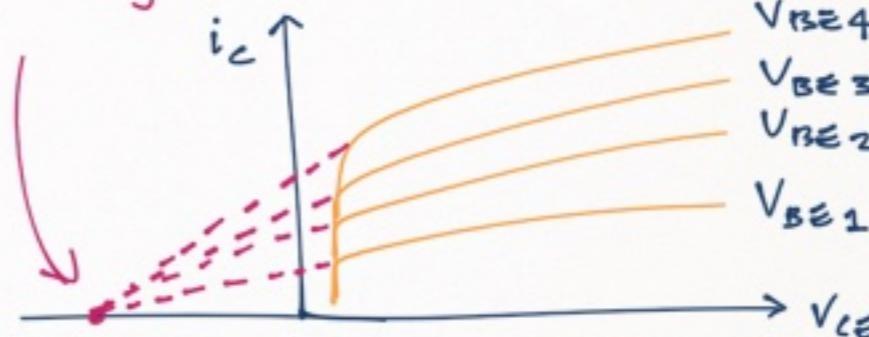


Changing value of I_B


BIASING THE BJT

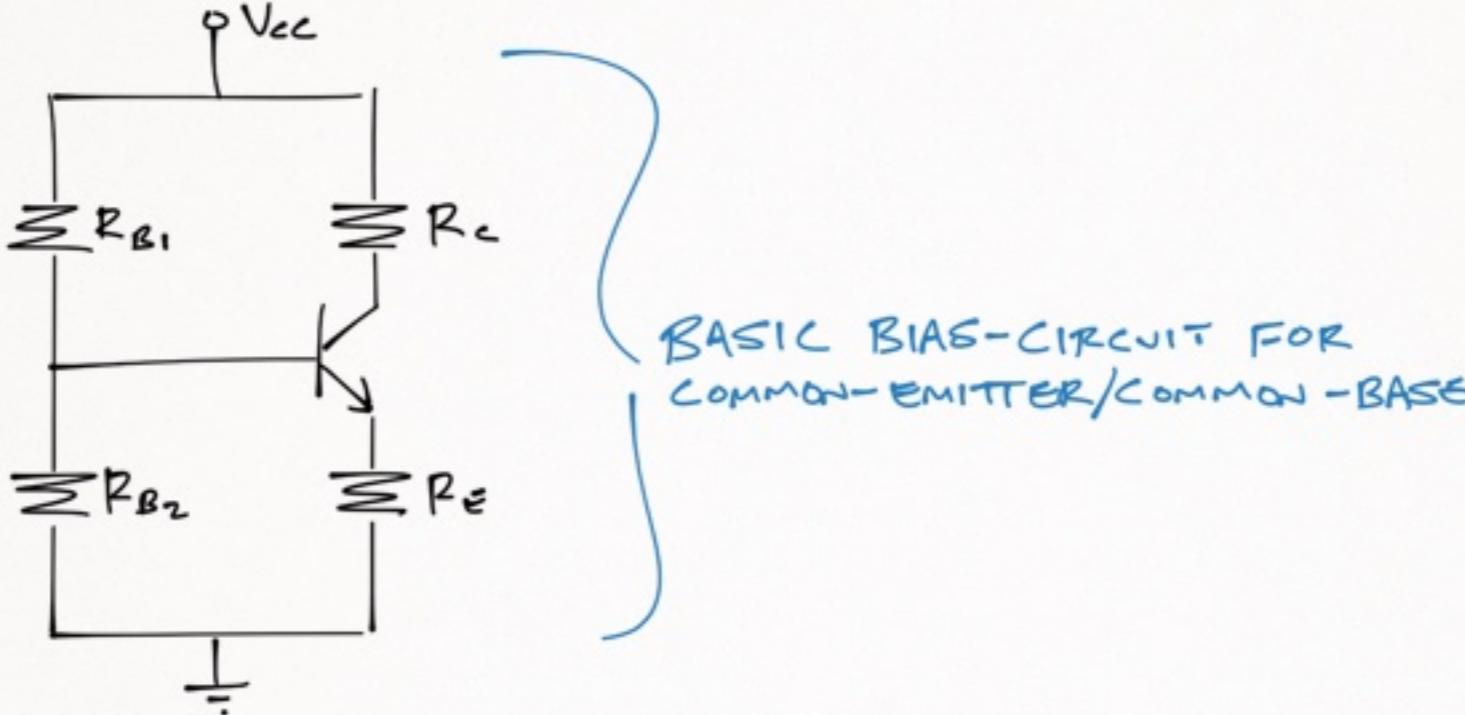

FINDING THE DC OPERATING POINT

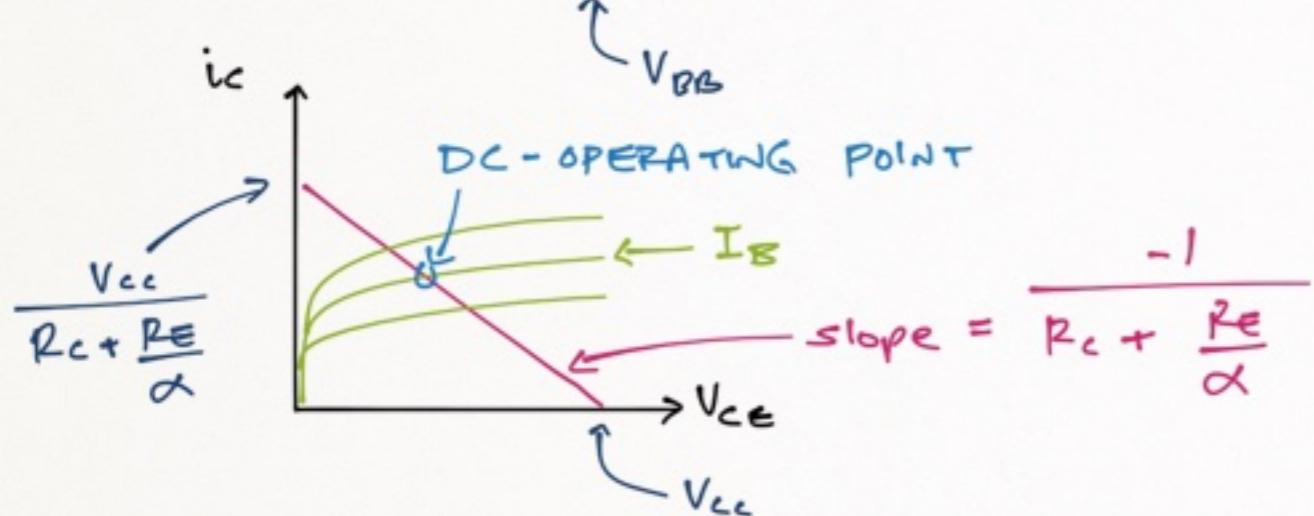

$\frac{1}{3}$ rd RULE TO BIAS TRANSISTOR

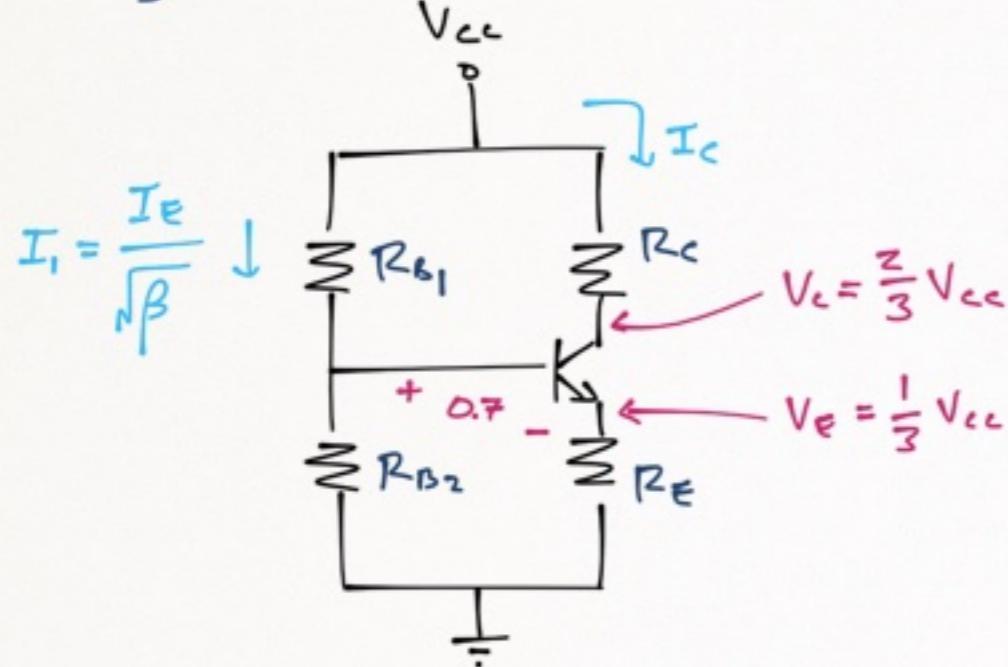

$$R_c = \frac{1}{3} \frac{V_{cc}}{I_c}$$

$$R_E \approx R_c$$

$$V_B = V_E + 0.7$$

$$I_B = \frac{I_c}{\beta}$$

$$R_{B_1} = \frac{\frac{2}{3}V_{cc} - 0.7V}{\frac{I_E}{\sqrt{\beta}}}$$



$$V_E = \frac{1}{3} V_{cc}$$

$$I_E = I_B (\beta + 1) = \frac{V_E}{R_E}$$


$$I_i = \frac{I_E}{\sqrt{\beta}}$$

$$R_{B_2} = \frac{\frac{1}{3}V_{cc} + 0.7V}{I_E \left(\frac{1}{\sqrt{\beta}} - \frac{1}{\beta+1} \right)}$$

COMMON Emitter AMPLIFIER

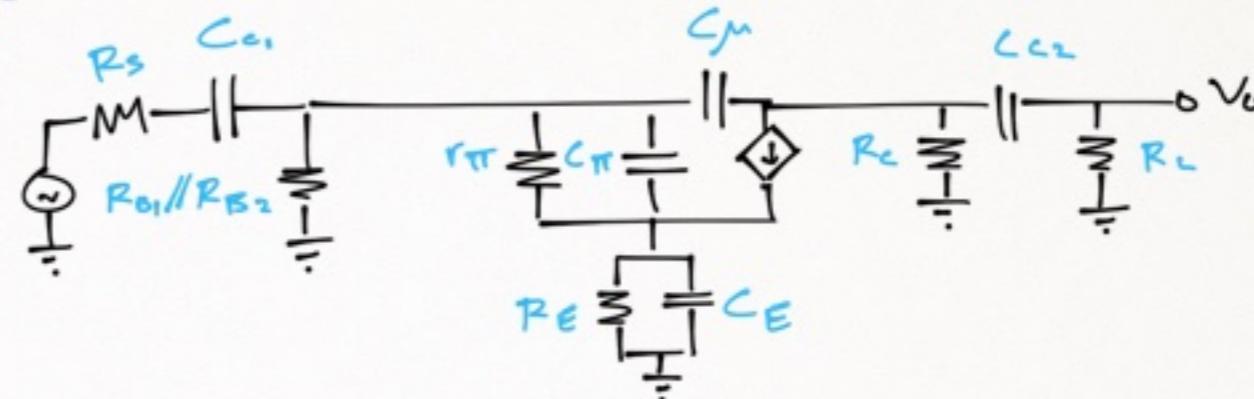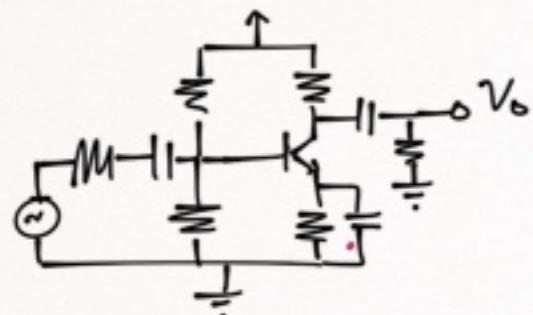

LOW FREQUENCY SMALL-SIGNAL MODEL

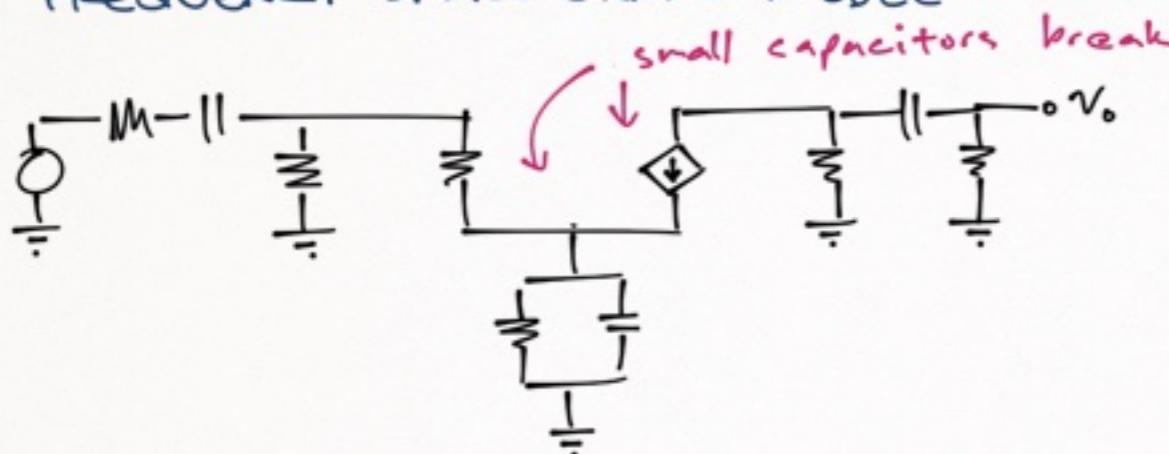


$$r_{\pi} = \frac{V_T}{I_B} = V_T \frac{(R_{B1}/R_{B2} + (\beta+1)R_E)}{V_{cc} \frac{R_{B2}}{R_{B1}+R_{B2}} - 0.7}$$

$$A_M = -\frac{\beta}{r_{\pi}} (R_C/R_L) \frac{R_{B1}/R_{B2}/r_{\pi}}{R_{B1}/R_{B2}/r_{\pi} + R_S}$$

$$\omega_{z1L} = \omega_{z2L} = \phi$$

$$\omega_{z3L} = \frac{1}{R_E C_E}$$

HIGH FREQUENCY SMALL-SIGNAL MODEL

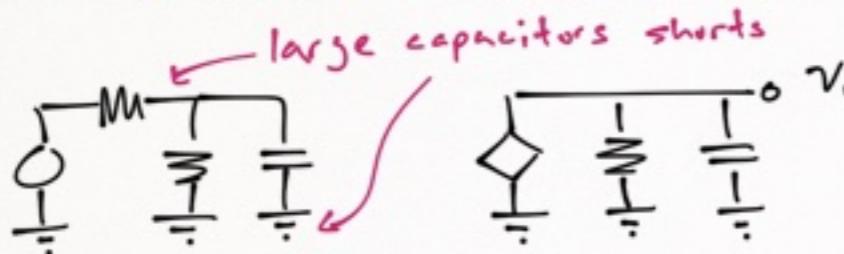


$$\omega_{p1L} = \frac{1}{(R_C + R_L) C_{o2}}$$

$$\omega_{p2L} = \frac{1}{(R_S + R_{B1}/R_{B2}/r_{\pi}) C_{o1}}$$

if C_E open:
 $r_{\pi} + (1+\beta)R_E$

MIDBAND SMALL-SIGNAL MODEL

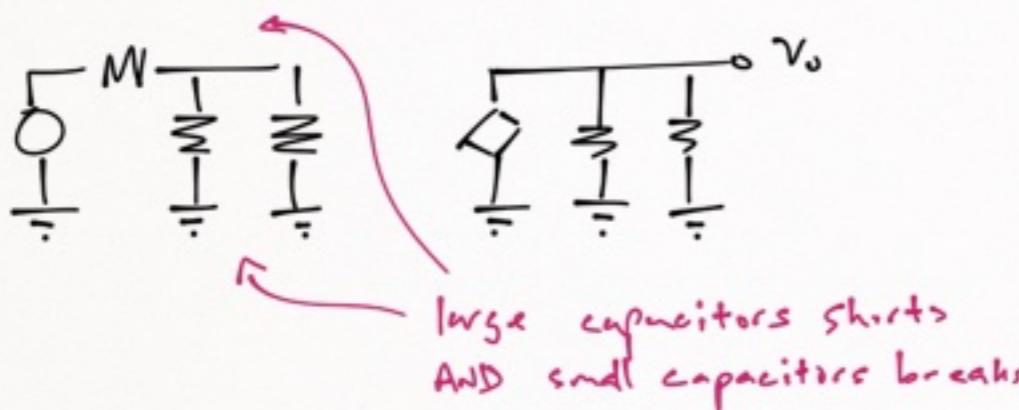



$$\omega_{p3L} = \frac{1}{(R_E \parallel \frac{r_{\pi} + R_{B1}/R_{B2}}{1+\beta}) C_E}$$

if C_E short:
 $\parallel 50$


$$\omega_{p1H} = \frac{1}{C_{pi} [R_L \parallel R_C]}$$

$$\omega_{p2H} = \frac{1}{[C_{pi} + C_{pi}(1 + g_m R_L \parallel R_C)] (R_S \parallel R_E)}$$


COMMON BASE AMPLIFIER

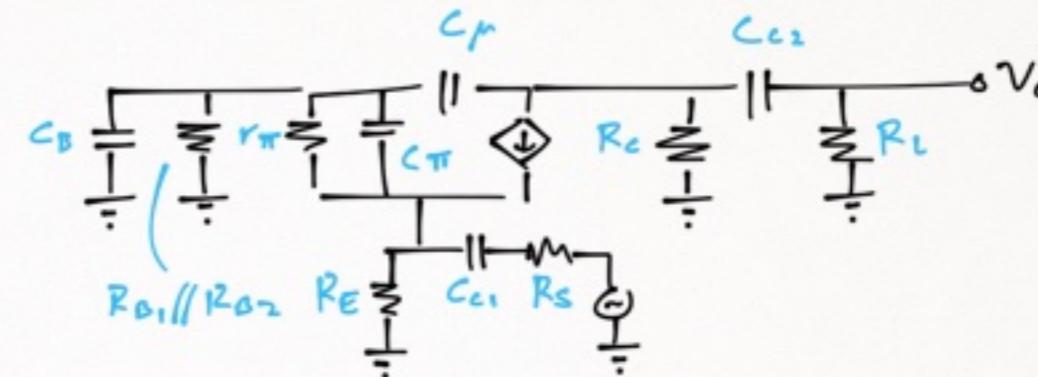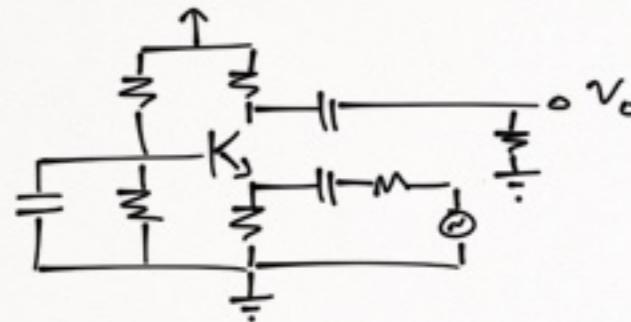


LOW FREQUENCY SMALL SIGNAL MODEL

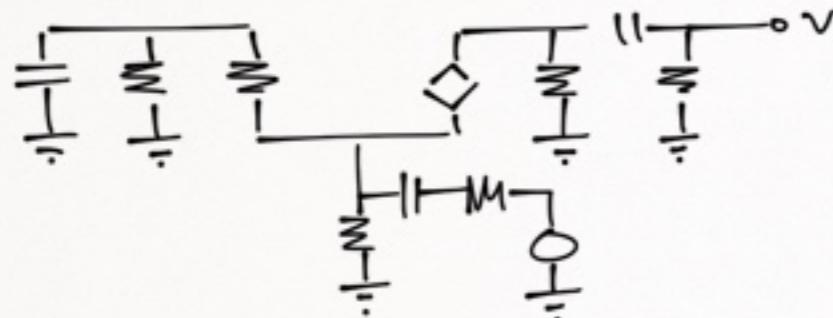

HIGH FREQUENCY SMALL SIGNAL MODEL

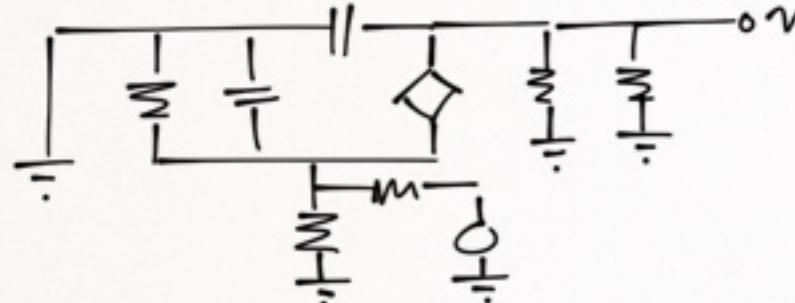

MIDBAND SMALL SIGNAL MODEL

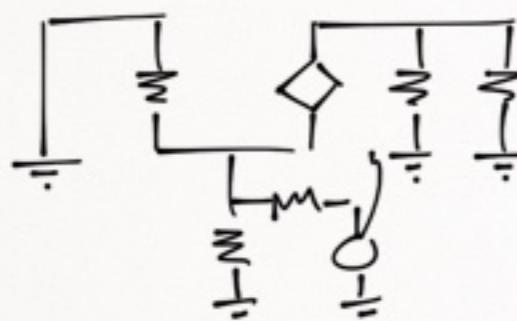

FORMULAS

$$A_m = \frac{-\beta}{r_{\pi}} (R_C // R_L) \frac{\frac{r_{\pi}}{1+\beta} // R_E}{R_S + \frac{r_{\pi}}{1+\beta} // R_E}$$

$$\omega_{Lz} = \frac{1}{(R_{B1} // R_{B2}) C_B}$$

$$\omega_{PH1} = \frac{1}{(R_E // R_S // \frac{r_{\pi}}{1+\beta}) C_{\pi}}$$

$$\omega_{PH2} = \frac{1}{(R_L // R_C) C_{\mu}}$$


$$\omega_{PL1} = \frac{1}{[R_{B1} // R_{B2} // (r_{\pi} + (1+\beta)(R_E // R_S))] C_B}$$

$$\omega_{PL2} = \frac{1}{[\frac{r_{\pi} + R_{B1} // R_{B2}}{1+\beta} // R_E + R_S] C_{\mu}}$$

$$\omega_{PL3} = \frac{1}{(R_C + R_L) C_{C2}}$$

CASCODE

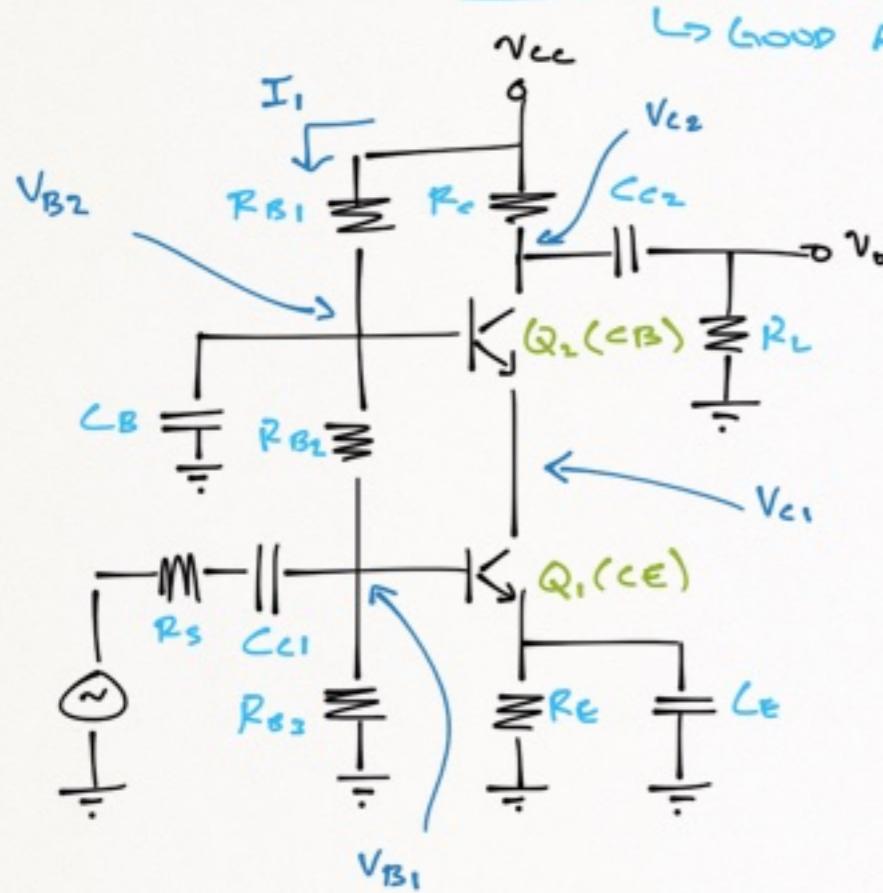COMBINES WIDE BANDWIDTH OF COMMON BASE
HIGH INPUT IMPEDANCE OF COMMON Emitter



Good amplification, doesn't require much I

BIAS USING $\frac{1}{4}, \frac{1}{2}$ RULE

$$V_{C_2} = \frac{3}{4} V_{cc}$$

$$V_{B_2} = \frac{1}{2} V_{cc} + 0.7$$

$$V_{L_1} = \frac{2}{4} V_{cc}$$

$$V_{B_1} = \frac{1}{4} V_{cc} + 0.7$$

$$V_E = \frac{1}{4} V_{cc}$$

$$I_I = \frac{I_e}{\sqrt{\beta}}$$



$$I_{E1,2} \approx I_{C1,2} = \frac{V_{cc} - V_{C_2}}{R_C}$$

$$I_{B1,2} \approx \frac{I_{e_1}}{\beta_1} \approx \frac{I_{e_2}}{\beta_2}$$

$$R_{B_1} = \frac{V_{cc} - V_{B_2}}{I_{B_1}}$$

$$R_{B_2} = \frac{V_{o_2} - V_{B_1}}{I_I - I_{B_1}}$$

MIDBAND SMALL SIGNAL MODEL

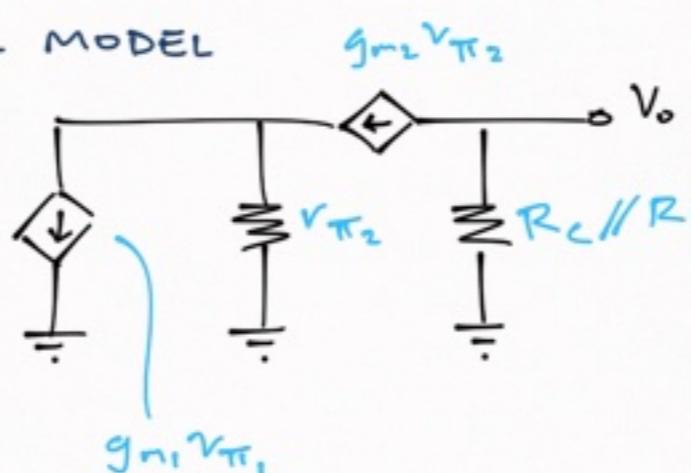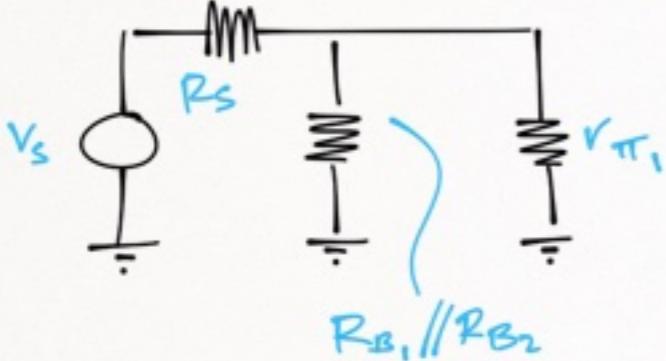


$$R_{B_2} = \frac{V_{B_1}}{I_I - 2I_{B_1}}$$

$$R_E = \frac{V_E}{I_{e_2} + 2I_{B_1}}$$

$$A_M = -g_m \frac{(R_C // R_L)(R_{B_2} // R_{B_3})}{(R_{23} + R_S)} \times \frac{r_\pi}{r_\pi + R_{S2} // R_{B_3} // R_S} (?)$$

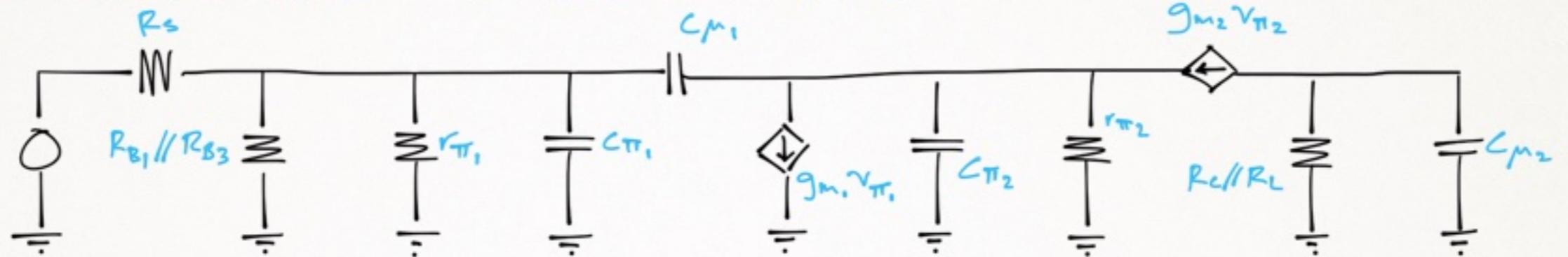HIGH FREQUENCY SMALL SIGNAL MODEL OF CASCODE



$$\omega_{HP1} = \frac{1}{C_{\mu_2}(R_c // R_L)}$$


$$\omega_{HP2} = \frac{1}{(C_{\pi_2} + 2C_{\mu_1}) \frac{r_{\pi_2}}{1+\beta}}$$

$$\omega_{HP3} = \frac{1}{(R_s // R_{B1} // R_{B2} // r_{\pi_2})(C_{\pi_1} + 2C_{\mu_1})}$$

$$r_{\pi_1} = r_{\pi_2}?$$


r_{π_1} Am cascode?

LOW FREQUENCY MODEL OF CASCODE

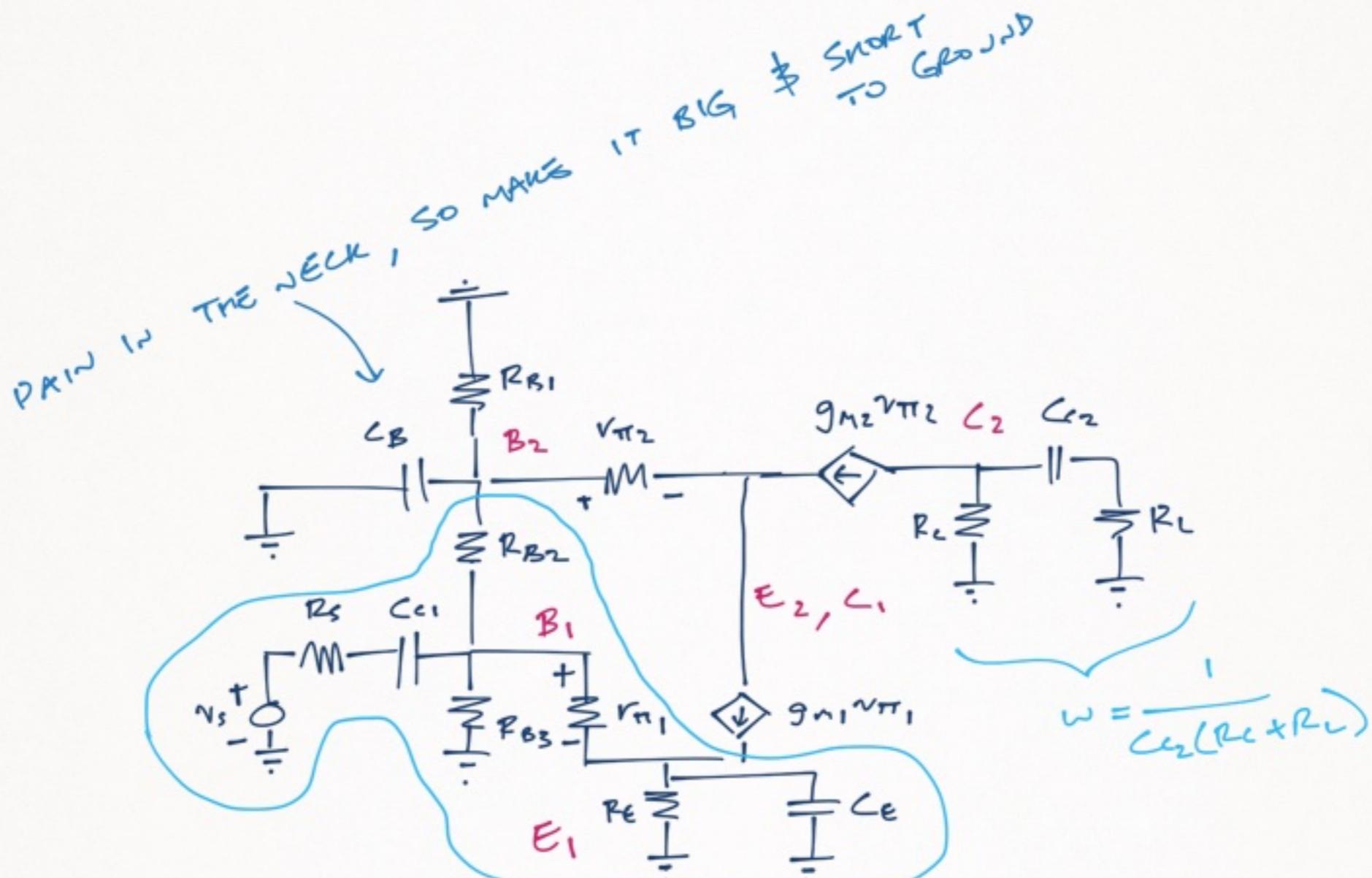

FOR $C_e \neq C_{ei}$, IF C_B IS SHORTED TO GND
LEFT w/ SAME CIRCUIT AS FOR C.E.

Q1

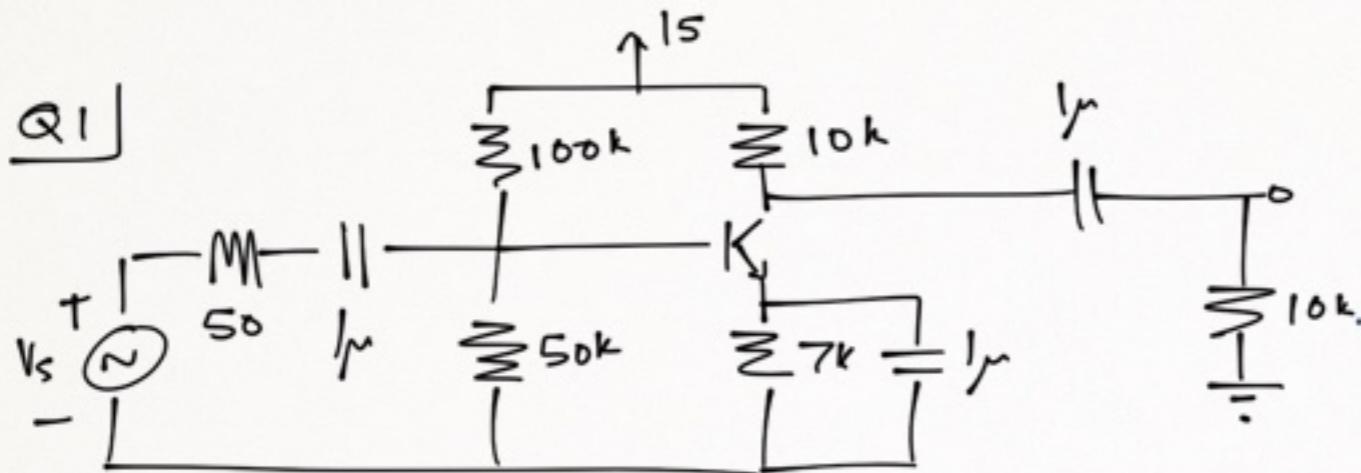

COMMON Emitter

$$r_{\pi} = V_t \frac{R_{B1}/R_{B2} + (\beta + 1)R_E}{V_{CE} \frac{R_{B2}}{R_{B1} + R_{B2}} - 0.7}$$

$$= 25 \text{ mV} \frac{100k/50k + (101)7k}{15 \frac{50k}{150k} - 0.7}$$

$$= 4.3043k \Omega$$

$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{4.3043k} = 23.233 \text{ mS}$$

$$\omega_{LZ1} = \phi$$

$$\omega_{LZ2} = \phi$$

$$\omega_{LZ3} = \frac{1}{R_E C_E} = \frac{1}{7k \cdot 1 \mu F} = 142.86 \frac{\text{rad}}{\text{s}}$$

$$\omega_{LP1} = \frac{1}{(R_C + R_L) C_{CE}} = \frac{1}{(10k + 10k) 1 \mu} = 50 \frac{\text{rad}}{\text{s}}$$

ASSUMING CE OPEN

$$r_{\pi} + (101)R_E$$

$$= 31.357 \frac{\text{rad}}{\text{s}}$$

ASSUMING CE CLOSED

$$\omega_{LP2} = \frac{1}{(R_S + R_{B1}/R_{B2}/r_{\pi}) C_{CE}}$$

$$= \frac{1}{(50 + 100k/50k/4.3k) 1 \mu} = 259.16 \frac{\text{rad}}{\text{s}}$$

ASSUMING C_E OPEN

$$\omega_{LP3} = \frac{1}{(R_E / (r_{\pi} + R_{B1}/R_{B2})) C_F}$$

$$= \frac{1}{(7k / (4.3k + 100k/50k)) 1 \mu} = 2826 \frac{\text{rad}}{\text{s}}$$

ASSUMING C_E CLOSED

$$= 23.362 \times 10^3 \frac{\text{rad}}{\text{s}}$$

WHICH TO CHOOSE?

$$V_B = \frac{1}{3} V_{CC}$$

1/3 rule VERSION 1

$$V_C = \frac{2}{3} V_{CC}$$

$$I_I = \frac{I_E}{\sqrt{\beta}} = \frac{V_{CC} - V_B}{R_{B1}} = \frac{V_{CC} - \frac{1}{3} V_{CC}}{R_{B1}} = \frac{2}{3} \frac{V_{CC}}{R_{B1}}$$

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{1}{3} \frac{V_{CC}}{R_C}$$

$$I_B = I_I - \frac{V_B}{R_{B2}} = I_I - \frac{1}{3} \frac{V_{CC}}{R_{B2}} = \frac{I_E}{\sqrt{\beta}} - \frac{1}{3} \frac{V_{CC}}{R_{B2}}$$

$$I_E = \frac{V_E}{R_E} = \frac{\frac{1}{3} V_{CC} - 0.7}{R_E}$$

$$R_C = \frac{1}{3} \frac{V_{CC}}{I_C}$$

$$R_{B1} = \frac{\frac{2}{3} V_{CC}}{I_I} = \frac{\frac{2}{3} V_{CC}}{\frac{I_E}{\sqrt{\beta}}}$$

$$R_E = \frac{\frac{1}{3} V_{CC} - 0.7}{I_E}$$

$$R_{B2} = \frac{\frac{1}{3} V_{CC}}{I_I - I_B} = \frac{\frac{1}{3} V_{CC}}{\frac{I_E}{\sqrt{\beta}} - \frac{I_E}{\beta}} = \frac{R_{B1}}{2} \left(\frac{1}{1 - \frac{1}{\sqrt{\beta}}} \right)$$

MIDTERM

2 QUESTIONS
75 MINUTES

IF BETA NOT SPECIFIED, $\beta = 100$

IF $c_\pi \neq c_n$ NOT SPECIFIED, COMPLAIN

DEMAG r_π IF GOING FROM E TO B

DON'T MAG r_π IF GOING FROM B TO E

[Q2]

$$V_B = \frac{1}{3} V_{CC} = 4 \text{ V}$$

$$V_C = \frac{2}{3} V_{CC} = 8 \text{ V}$$

$$I_E = \frac{\frac{1}{3} V_{CC} - 0.7}{R_E} = 1.65 \text{ mA}$$

$$R_{B1} = \frac{\frac{2}{3} V_{CC}}{\frac{I_E}{\sqrt{\beta}}} = \frac{8}{0.1 \cdot 1.65 \text{ mA}} = 496.485 \text{ k}$$

$$R_{B2} = \frac{\frac{1}{3} V_{CC}}{\frac{I_E}{\sqrt{\beta}} - \frac{I_E}{\mu}} = 26.936 \text{ k}$$

~~$$R_C = \frac{1}{3} \frac{V_{CC}}{I_C} =$$~~

$$12 \text{ k} \approx R_C = 2 \text{ k}$$

$$\omega_{PH1} = \frac{1}{R_L \parallel R_C \parallel C_M} = \frac{1}{2 \text{ k} / 14 \text{ k} \parallel 1 \text{ pF}} = 750 \text{ M rad/s}$$

Now we have
to

$$r_{\pi} = \frac{V_T}{I_B} = \frac{25 \text{ mV}}{16.5 \mu \text{A}} = 1.5152 \text{ k}$$

$$\frac{I_E}{\sqrt{\beta}} - \frac{1}{3} \frac{V_{CC}}{R_{B2}}$$

$$A_M = -\frac{160}{1.5152 \text{ k}} \cdot 2 \text{ k} \parallel 4 \text{ k} \cdot \frac{2 \text{ k} \parallel \frac{1.5152 \text{ k}}{101}}{2 + \frac{1.5152 \text{ k}}{101} + 50} = -20.19 \frac{\text{V}}{\text{V}}$$

$\frac{1}{3}$ rule ($\ln^2 N$)

A_M CASCADE

UPDATE

CB

‡

CE

FOR OPEN VS. CLOSED TESTS

A) E c
B
 $1k + 0.1k$

$1.1k$ OK?

B) c) ASSUMING INF S.C.
 $10\mu F \rightarrow 910 + \frac{rad}{s}$

INF O.C.
 $\times 90 \frac{rad}{s}$

e, f, b,


$$20 \frac{rad}{s} = \underline{\quad}$$


From where?

ASSUMING $10\mu F$ SHORTS
 $1M \frac{rad}{s}$


ASSUMING $10\mu F$ OPEN

$$90 k \frac{rad}{s}$$

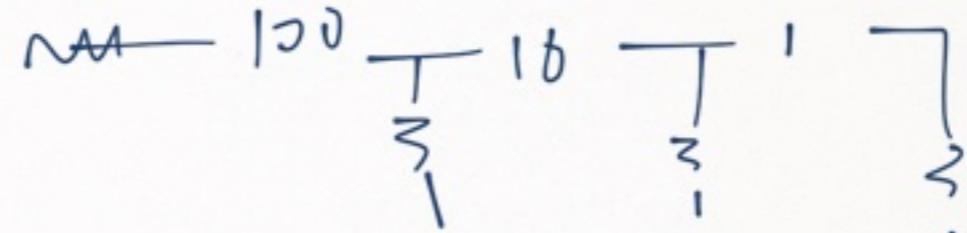

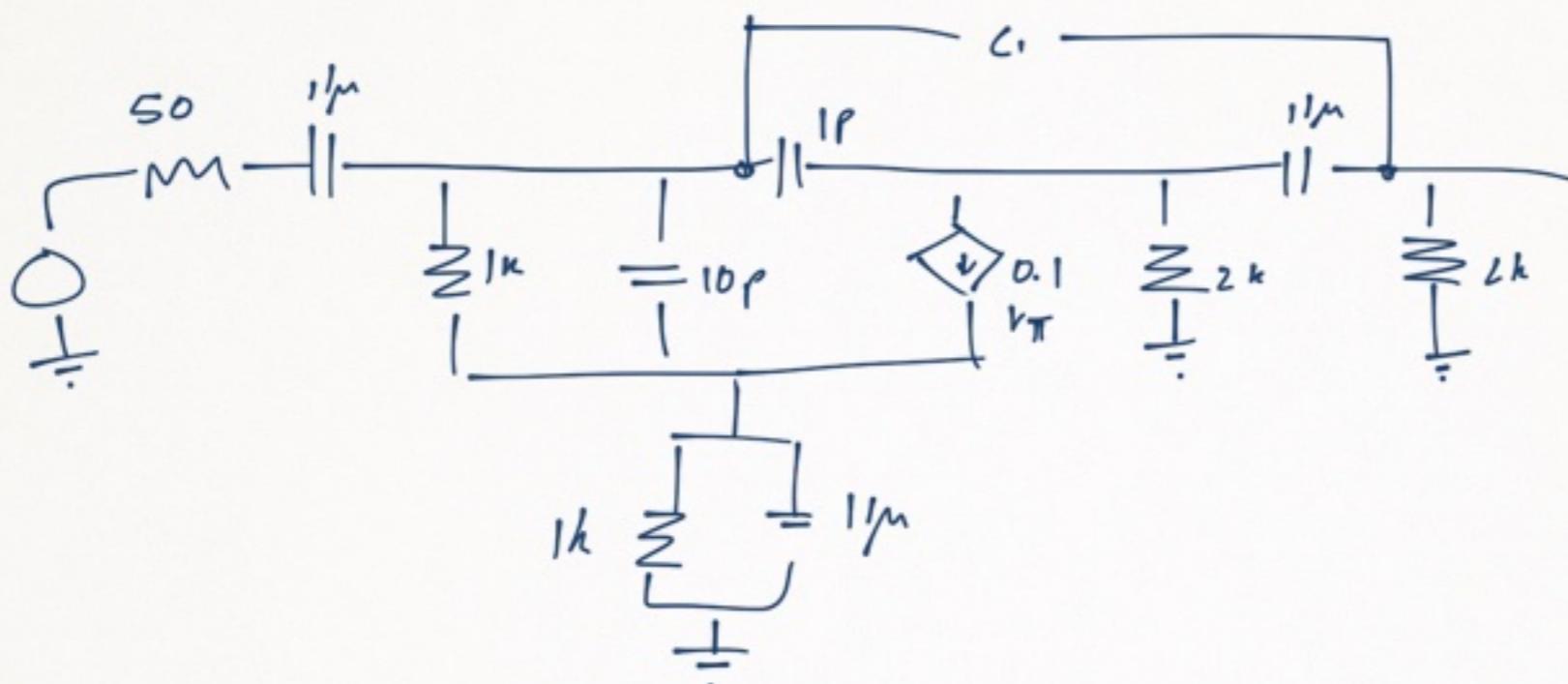

② HIGH FREQ. LARGE CAPACITORS ARE SHORTS

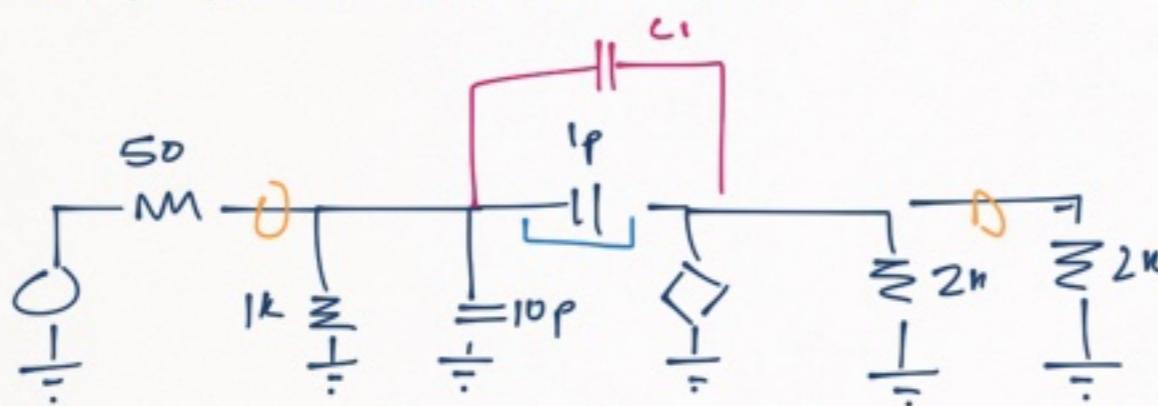

$10p$
ASSUMING
 I_p S.C.

$$\omega_{HP_1} = \frac{1}{10p(50//1k//2k//2k)} = 2.2 \cdot 10^4 \frac{\text{rad}}{\text{s}}$$

$10p$
ASSUMING
 I_p O.C.

$$\omega_{HP_1} = \frac{1}{10p(50//1k)} = 2.1 \cdot 10^4 \frac{\text{rad}}{\text{s}}$$

I_p ASSUMING
 I_p SC

$$\omega_{HP_2} = \frac{1}{I_p(2k//2k)} = 1 \cdot 10^4 \frac{\text{rad}}{\text{s}}$$

$10p$ OP


$$\omega_{HP_2} = \frac{1}{I_p(50//1k//2k//2k)} = 22 \cdot 10^4$$

PROJECT TUTORIAL

INERTIA IS FELT AT A ROTATING SHAFT

- ↳ "HOW MASSY DOES THIS FEEL?"
- ↳ FUNCTION OF RADIUS \neq MASS

$$Mr^2 \quad J \neq M$$

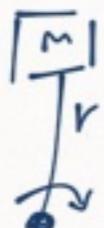

Ex)?

IF NEGATIVE

F.B. THE
C.E. IS $\rightarrow L + \frac{Ks(s+4)}{s^2 + 2s + 2} = \phi$

FIND POLES \neq ZEROS
FIND ROOT LOCUS

VERIFY CLOSED LOOP SYSTEM.

$$\frac{Y}{U} = \frac{KG}{1+KGH}$$


This is C.E. OF CLOSED LOOP Sys.

Ex)?

$$H(s) = 1 \quad w/ \quad \text{NEG. FB} \neq L(s) = G_c G = \frac{1}{s(s+2)(s^2 + 4s + 5)}$$

OPEN-LOOP GAIN
IS SHORTENED TO
"Loop Gain", i.e. L

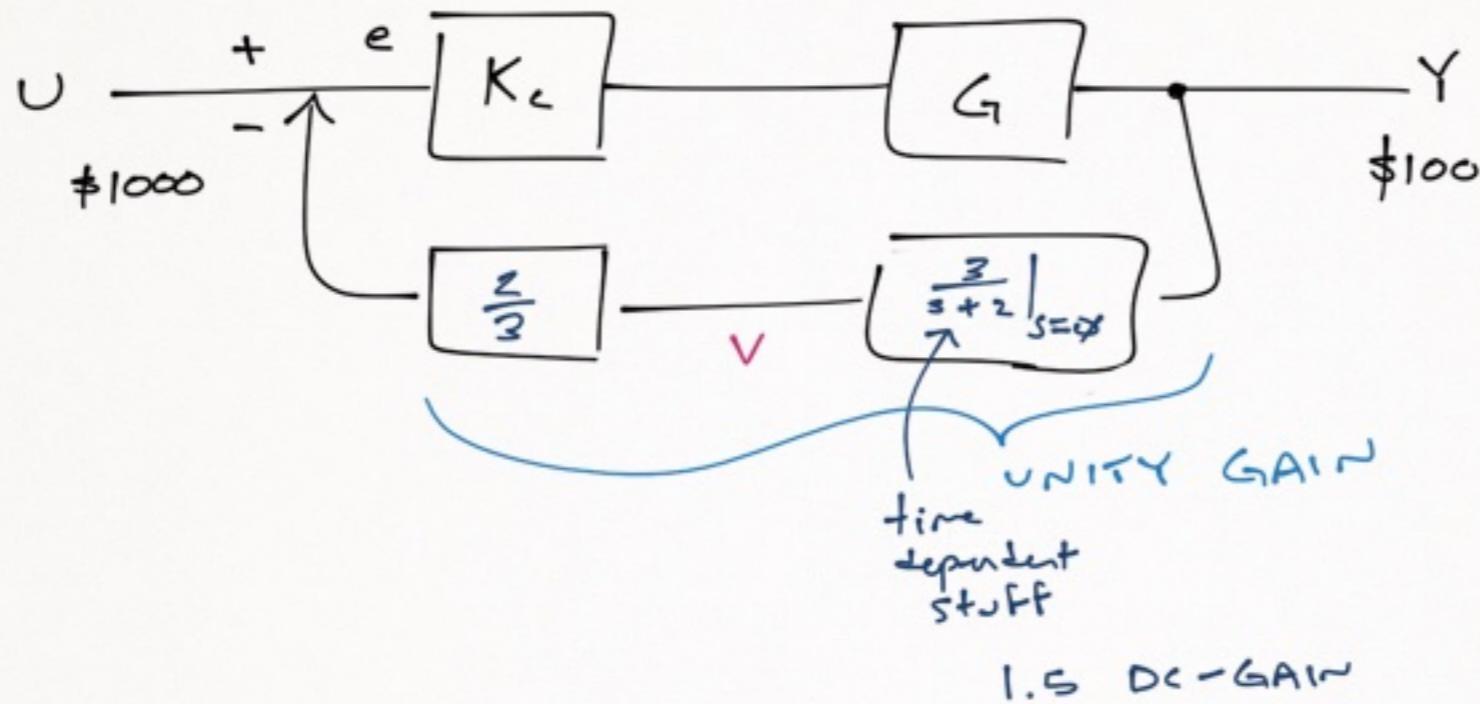G IS USED FOR FORWARD PATH STUFF
G_c IS FOR CONTROLLER



$$PID = k_D \frac{s^2 + \frac{k_p}{k_D}s + \frac{k_i}{k_D}}{s}$$

PLACE THE ZEROS
RIGHT ON TOP OF
THE POLES

$(s+1)(s+2) = s^2 + 3s + 2$

WANT TO PUT OUR
ZEROS OVER OUR
POLES @ $1 \neq 2$

$k_p = 25$
 $k_I = 17$
 $k_D = 12$

$$k_p = 3 \times k_D$$

$$k_I = 2 \times k_D$$

$$1. Si - E_g = 1.12 \text{ eV}, \quad n_i = 1 \cdot 10^{10} \frac{1}{\text{cm}^3}, \quad @ T = 300K$$

$$Ge - E_g = 0.67 \text{ eV}, \quad n_i = 2.3 \cdot 10^{13} \frac{1}{\text{cm}^3}, \quad @ T = 300K$$

a) CALC. n, p @ $T = 348.15K$ ($75^\circ C$)

$$n_i(300) = 10^{10} \frac{1}{\text{cm}^3} = Be^{\frac{-E_g}{2kT}} = Be^{\frac{-1.12 \text{ eV}}{2k \cdot 300}} \rightarrow B = 2.56 \cdot 10^{19}$$

$$n_i(348.15) = Be^{\frac{-1.12 \text{ eV}}{2k \cdot 348.15}} = 2.56 \cdot 10^{19} e^{\frac{-1.12 \text{ eV}}{2k \cdot 348.15 K}}$$

$$= \boxed{2.003 \cdot 10^{19} \frac{1}{\text{cm}^3}} = n_i = p_i \quad Si$$

$$n_i(300) = 2.3 \cdot 10^{13} \frac{1}{\text{cm}^3} = Be^{\frac{-0.67 \text{ eV}}{2k \cdot 300}} \rightarrow B = 9.761 \cdot 10^{18}$$

$$n_i(348.15) = 9.761 \cdot 10^{18} e^{\frac{-0.67 \text{ eV}}{2k \cdot 348.15 K}}$$

$$= \boxed{1.38 \cdot 10^{14} \frac{1}{\text{cm}^3}} = n_i = p_i \quad Ge$$

b) CALC CONDUCTIVITÉS @ $T = 348.15K$

$$Si - \mu_n = 1350 \frac{\text{cm}^2}{\text{Vs}}$$

$$\mu_p = 450 \frac{\text{cm}^2}{\text{Vs}}$$

$$Ge - \mu_n = 3900 \frac{\text{cm}^2}{\text{Vs}}$$

$$\mu_p = 1900 \frac{\text{cm}^2}{\text{Vs}}$$

$$\sigma_{Si} = q \mu_n n_i + q \mu_p p_i$$

$$= 4.332 \frac{\text{mS}}{\text{m}} + 1.444 \frac{\text{mS}}{\text{m}}$$

$$= 5.776 \frac{\text{mS}}{\text{m}} = \boxed{57.8 \frac{\text{mS}}{\text{cm}}}$$

$$\sigma_{Ge} = q \mu_n n_i + q \mu_p p_i = 12.82 \frac{\text{mS}}{\text{mm}} = \boxed{0.128 \frac{\text{S}}{\text{cm}}}$$

c) Si \neq Ge wafer doped with $N_D = 10^{16} \frac{1}{\text{cm}^3}$

FIND DENSITIES OF MAJORITY/MINORITY CARRIERS

$$n_0 p_0 = n_i^2$$

$$n_0 = N_D = 10^{16} \frac{1}{\text{cm}^3} \quad \text{MAJORITY}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{10^{20}}{10^{16}} = 10^4 \frac{1}{\text{cm}^3} \quad \text{MINORITY}$$

$$n_0 = N_D = 10^{16} \frac{1}{\text{cm}^3}$$

$$p_0 = \frac{(2.3 \cdot 10^{13})^2}{10^{16}} = 5.29 \cdot 10^{10} \frac{1}{\text{cm}^3}$$

} Silicon

$$\sigma_{Si} = q \mu_n p_i + q \mu_p n_i$$

$$= q (1350 \frac{\text{cm}^2}{\text{Vs}} 10^4 \frac{1}{\text{cm}^3} + 450 \frac{\text{cm}^2}{\text{Vs}} 10^{16} \frac{1}{\text{cm}^3})$$

$$= 0.72 \frac{S}{\text{cm}}$$

} Germanium

$$\sigma_{Ge} = q \mu_n p_i + q \mu_p n_i$$

$$= q [3900 (5.29 \cdot 10^{10}) + 1900 (10^{16})]$$

$$= 3.044 \frac{S}{\text{cm}}$$

d) $N_A = 9.9 \cdot 10^{15} \frac{1}{\text{cm}^3}$

$$n_0 = N_D - N_A = 10^{16} - 9.9 \cdot 10^{15} = 10^{14} \frac{1}{\text{cm}^3}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{10^{20}}{10^{14}} = 10^6 \frac{1}{\text{cm}^3}$$

$$n_0 = 10^{14} \frac{1}{\text{cm}^3}$$

$$p_0 = \frac{(2.3 \cdot 10^{13})^2}{10^{14}} = 5.29 \cdot 10^{12} \frac{1}{\text{cm}^3}$$

} Silicon

} Germanium

SAME AS ABOVE PROCEDURE

$$\sigma_{Si} = 2.163 \frac{S}{\text{cm}}$$

$$\sigma_{Ge} = 3.375 \frac{S}{\text{cm}}$$


2. Si PN JUNCTION $A = 1 \text{ mm}^2$, $N_D = 10^{16} \frac{1}{\text{cm}^2}$, $N_A = 4 \cdot 10^{15} \frac{1}{\text{cm}^2}$
 thickness of n & p-type regions is $10 \mu\text{m}$, $\tau_n = 1 \text{ ns}$, $\tau_p = 0.2 \text{ ns}$ ($n_i = 10^{10} \frac{1}{\text{cm}^2}$, $\mu_n = 1350$, $\mu_p = 450 \frac{\text{cm}^2}{\text{Vs}}$)
 ← middle of the band gap

a) $E_{fp} \neq E_{fn} = ?$ w.r.t. E_i @ $T = 300 \text{ K}$

$$E_{fp} = E_i - kT \ln\left(\frac{N_A}{n_i}\right) = E_i - k300 \ln\left(\frac{4 \cdot 10^{15}}{10^{10}}\right) = \boxed{E_i - 333.47 \text{ meV}}$$

$$E_{fn} = E_i + kT \ln\left(\frac{N_D}{n_i}\right) = E_i + k300 \ln\left(\frac{10^{16}}{10^{10}}\right) = \boxed{E_i + 357.159 \text{ meV}}$$

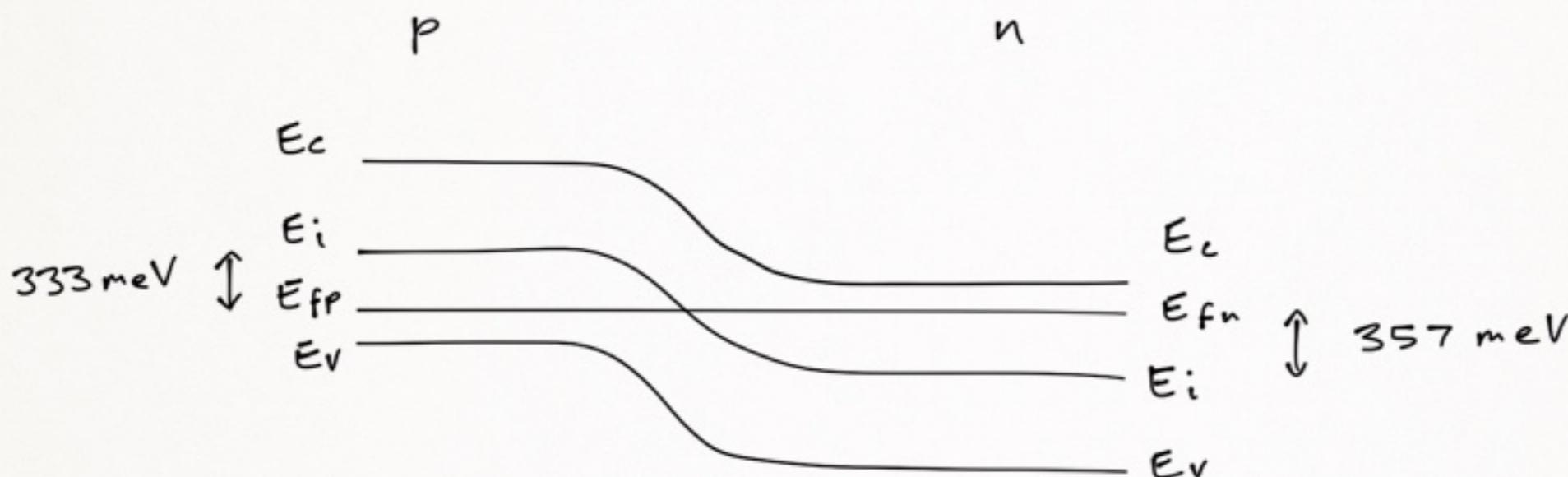b) DRAW JUNCTION BAND DIAGRAM FOR PN AT EQUILIBRIUM



c)

$$V_0 = \frac{kT}{q} \ln\left(\frac{N_A N_D}{n_i^2}\right) = \frac{k \cdot 300 \text{ K}}{q} \ln\left(\frac{4 \cdot 10^{15} \cdot 10^{16}}{10^{10} \cdot 10^{10}}\right) = \boxed{690.63 \text{ mV}}$$

$$E_0 = \frac{-q}{\epsilon} \times n N_D = \frac{-q}{\epsilon} \left(5.59 \cdot 10^{-7} \frac{4 \cdot 10^{15} \text{ cm}^{-2}}{4 \cdot 10^{15} \text{ cm}^{-2} + 10^{16} \text{ cm}^{-2}} \right) 10^{16} \frac{1}{\text{cm}^2} = \boxed{2.471 \cdot 10^6 \frac{\text{V}}{\text{m}}}$$

$$W_0 = \left(\frac{V_0 Z \epsilon}{q} \frac{N_A + N_D}{N_A N_D} \right)^{\frac{1}{2}} = \left(\frac{2 \cdot 11.7 \cdot 8.85 \cdot 10^{-14} \frac{\text{F}}{\text{cm}}}{q} \frac{4 \cdot 10^{15} + 10^{16}}{4 \cdot 10^{15} \cdot 10^{16}} 690.63 \text{ mV} \right)^{\frac{1}{2}} = \boxed{5.59 \cdot 10^{-7} \text{ m}}$$

d) FIND FORWARD CURRENT \neq DEPLETION WIDTH @ $V_A = 0.6 \text{ V}$ DRAW BAND DIAGRAM
 FIND TOTAL STORAGE CAPACITANCE FOR NEUTRAL N \neq P REGIONS AT THIS BIAS VOLTAGE

$$I_{\text{diode}} = A q n_i^2 \left(\frac{D_p}{L_p N_p} + \frac{D_n}{L_n N_A} \right) \left(e^{\frac{V_A}{V_{th}}} - 1 \right)$$

$\sqrt{D_p \tau_p}$ $\sqrt{D_n \tau_n}$

$$D_n = \mu_n \cdot V_{th}, \quad D_p = \mu_p \cdot V_{th}$$

$$C_s = I \frac{\tau_p}{V_{th}}$$

$$\frac{\mu_p \cdot V_{th}}{\sqrt{\mu_p V_{th} \tau_p} N_p} + \frac{\mu_n \cdot V_{th}}{\sqrt{\mu_n V_{th} \tau_n} N_A} = 6.76 \cdot 10^{-11} \frac{\text{Cm}^4}{\text{s}}$$

$$1 \text{ mm}^2 \cdot q \cdot \left(10^{10} \frac{1}{\text{cm}^3} \right)^2 = 1.602 \cdot 10^{-7} \frac{\text{sA}}{\text{m}^4}$$

$$\frac{\frac{m^2}{s} \cdot \cancel{s}}{\cancel{m^2} \cdot \cancel{N} \cdot \cancel{\sqrt{s}} \cdot \frac{1}{m^3}} = \frac{\frac{m^2}{s}}{\cancel{m} \cdot \frac{1}{m^2} \cancel{s^2}} = \frac{m^4}{s}$$

$$m^2 \cdot C \cdot \frac{1}{m^6} = \frac{C}{m^4} = \frac{As}{m^4}$$

$$I_{\text{diode}} = 4.608 \cdot 10^{-13} \text{ A}$$

$$C_s = 4.608 \cdot 10^{-13} \left(\frac{0.2 \text{ ns}}{25 \text{ mV}} \right) = 3.686 \cdot 10^{-21} \text{ F}$$


$$w = \left(\frac{2\epsilon}{q} \frac{N_A + N_D}{N_A N_D} (V_0 - V_A) \right)^{\frac{1}{2}} = 2.025 \cdot 10^{-7} \text{ m}$$

\nwarrow SAME AS
 PREVIOUS PAGE
 EXCEPT $-V_A$

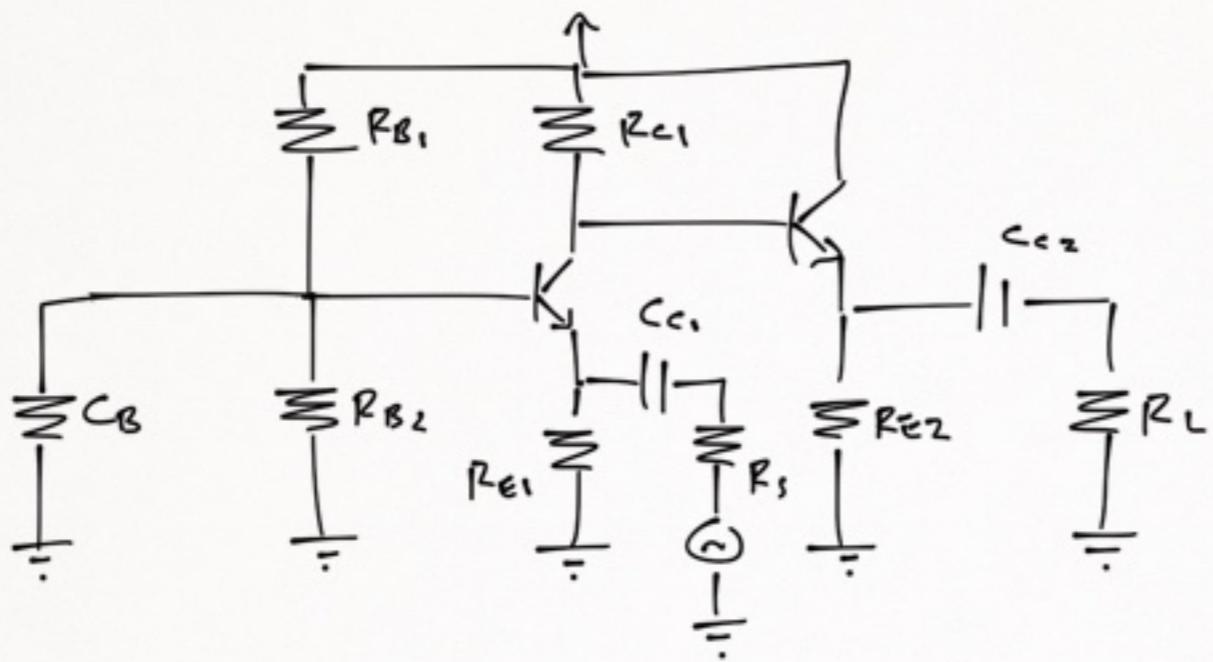e) $V_A = -0.6V$

$$W = \boxed{7.641 \cdot 10^{-7} \text{ m}}$$
$$I = \boxed{-4.42 \cdot 10^{-13} \text{ A}}$$
$$C_s = -4.42 \cdot 10^{-13} \frac{0.2 \text{ ns}}{25 \text{ mV}} = \boxed{-3.536 \cdot 10^{-21} \text{ F}}$$

} USING SAME FORMULAS AS ON PREV. PAGE BUT $V_A = -0.6V$





LOW FREQUENCY

NOT TESTING ON
SLEW RATE/FULL POWER BANDWIDTH

NOT TESTING OSCILLATORS & FILTERS

TESTING FEEDBACK

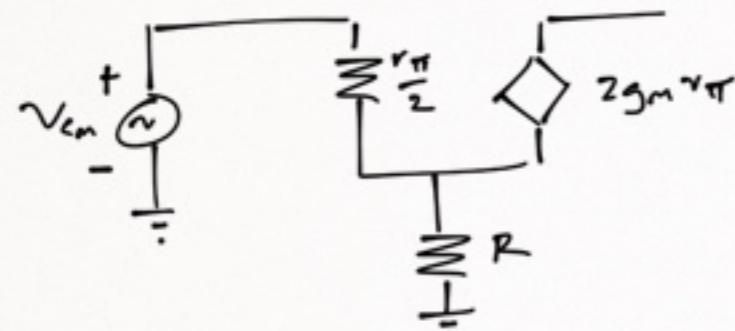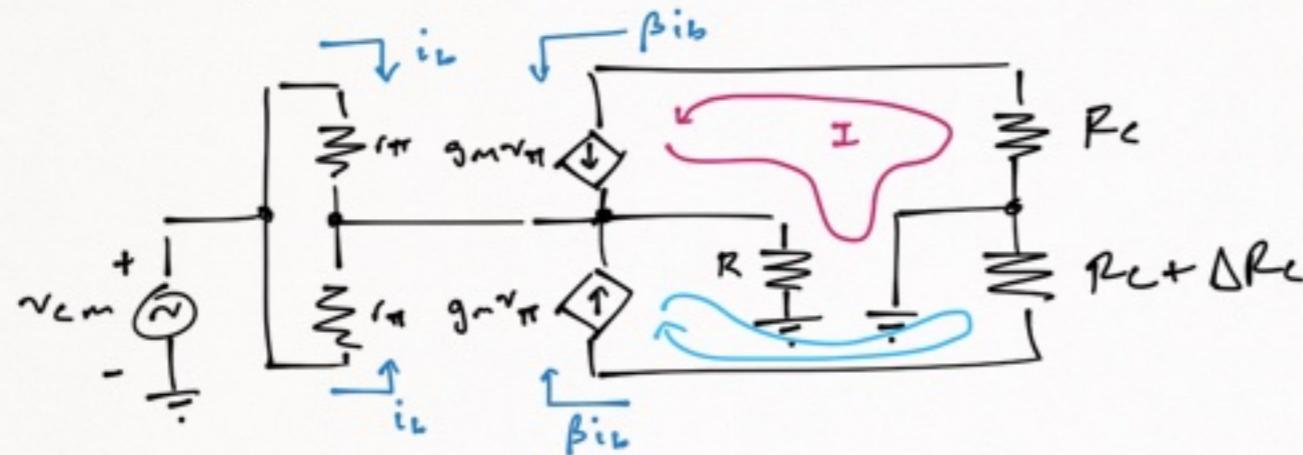SMALL SIGNAL MODEL FOR DIFFERENTIAL INPUT



$$v_\pi = \frac{v_{cm} \cdot \frac{r_\pi}{2}}{\frac{r_\pi}{2} + R(1+\beta)} = \frac{v_{cm} v_{icm}}{r_\pi + 2R(1+\beta)}$$

$$v_o = \frac{v_{cm} \Delta R_c}{\frac{1}{g_m} + 2R \frac{(1+\beta)}{\beta}} \approx v_{cm} \frac{\Delta R_c}{2R}$$

$$A_{cm} = \frac{\Delta R_c}{2R}$$


COMMON-MODE
REJECTION RATIO

$$CMR_{dB} = \left| \frac{A_J}{A_{cm}} \right| = g_m 2R \frac{R_c}{\Delta R_c} \approx 100,000$$

? in example
op-amp

PROBLEM SET 5


4]

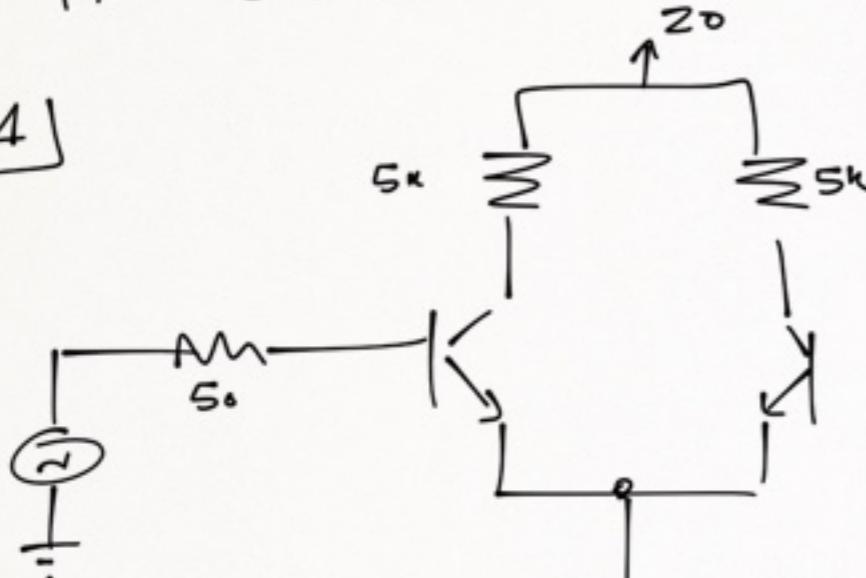

$$I_{E1} = I_{E2} = 2 \text{ mA} \approx I_{C1}, I_{C2}$$

$$g_m1 = g_m2 = 80 \text{ mV}$$
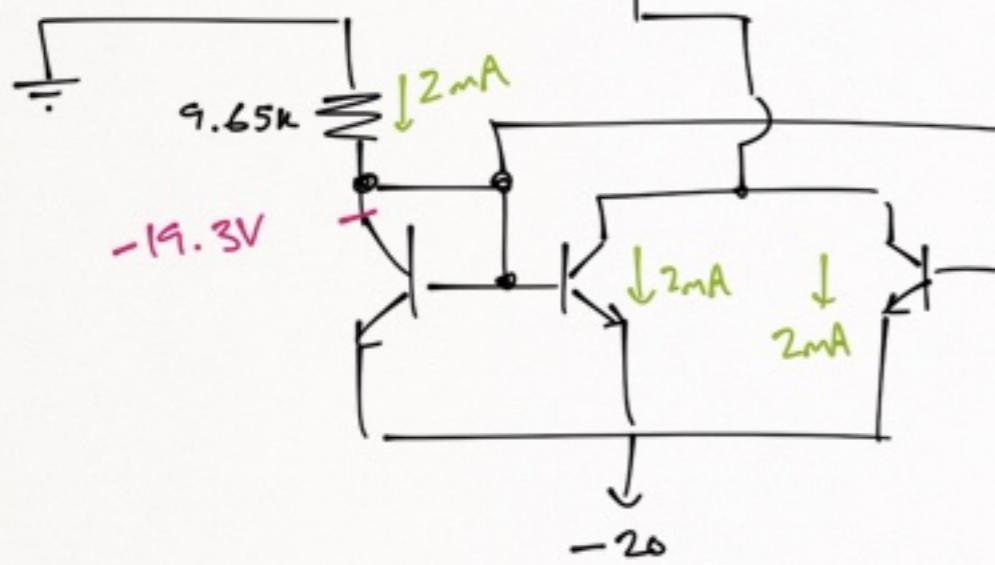
$$r_{\pi 1} = r_{\pi 2} = 1.25 \text{ k}\Omega$$




$$\omega_{n3dB} = \frac{1}{101\text{pF} \cdot 5\text{k}\Omega} = 2 \text{ M}\frac{\text{rad}}{\text{s}}$$

"BIG RESISTANCE, SMALL FREQ."


$\therefore V_o$ IS THE ONE WE CALC.

(?)

SMALL SIGNAL CIRCUIT

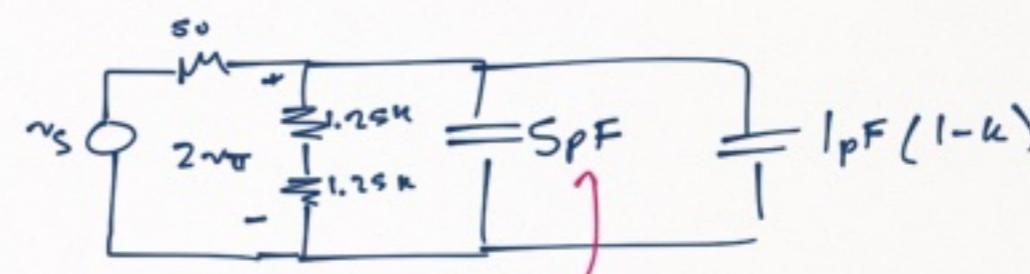

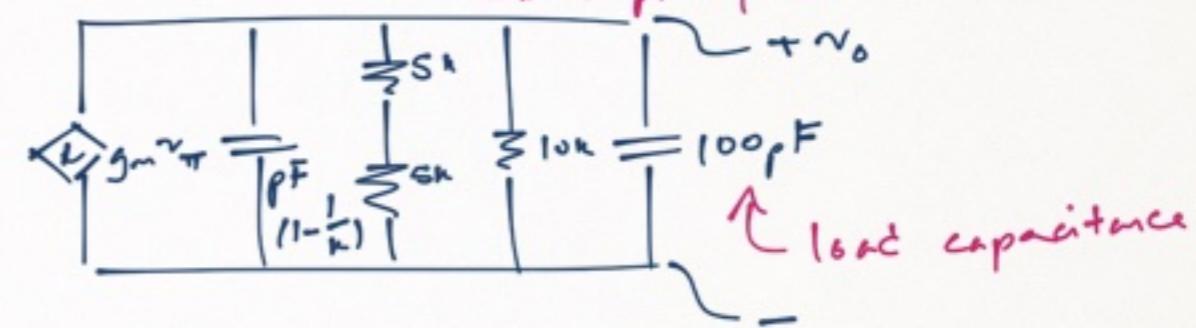$C_{\pi} = 10 \text{ pF} \not\parallel 2 \text{ in series}$



MIGLER'S

$$k = \frac{V_o}{2\pi f} = \frac{-g_m 10k // 10k}{2\pi f} = \frac{-400 \pi^2}{2\pi f} = -200$$

sees
 $\sim 49.8 \Omega$

$$\therefore C_1 = 206 \text{ pF} \quad \not\parallel C_2 = 101 \text{ pF} \quad \text{sees } \sim 5\text{k}\Omega$$

1. A feedback amplifier is designed using a gain of 10^4 for the basic amplifier and $\beta = 10^{-2}$. However, the basic amplifier actually has a gain of 7×10^3 .

a) What percentage of the intended gain does the actual gain represent?

b) Derive an expression for $\partial A_f / \partial A$ in terms of A and β .

c) By deriving the transfer function with feedback, explain why, for an amplifier having a low pass, single time-constant, frequency response, for every 20 dB of gain sacrificed by the application of negative feedback the 3dB bandwidth is extended by a decade. (Assume the feedback is purely real, i.e., frequency independent).

2. Use feedback techniques to show that the circuit shown in figure 1 has a gain of $-R_2/R_1$.



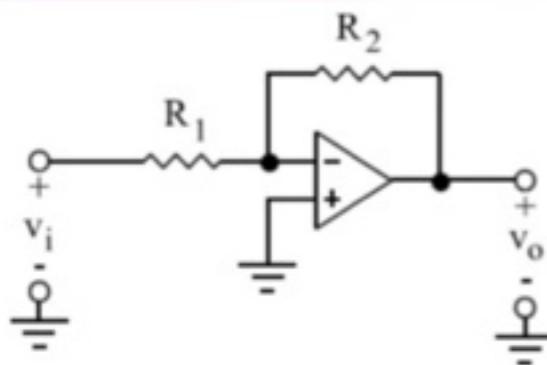


Figure 1.

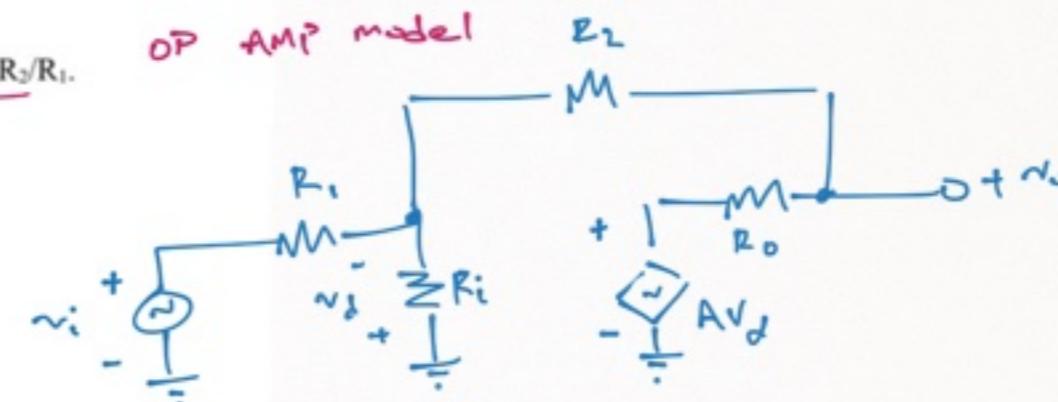

USE SHUNT-SHUNT $\rightarrow \gamma$ PARAMETER (will be told
about topology)

FEEDBACK
NETWORK

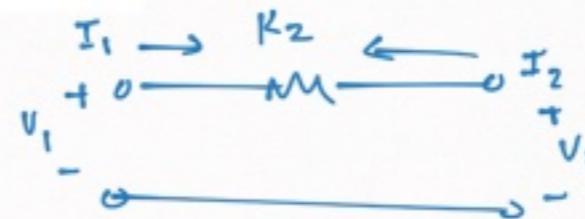


Voltage are indep.
currents are dep.

$$\gamma_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{R_2} \quad \text{means if } V_2 \text{ is shorted}$$


$$\gamma_{12} = \gamma_{21} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{R_2}$$

TRANSFORM SOURCE

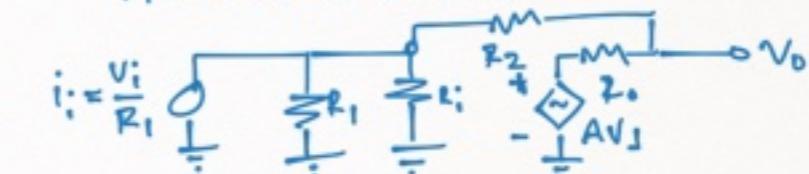


$$\gamma_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R_2}$$

IDEALIZED A CIRCUIT


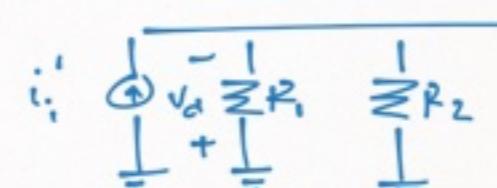


$$\text{let } V_{d'} = -V_d$$

$$A' = \frac{AR_2}{R_o + R_2}$$

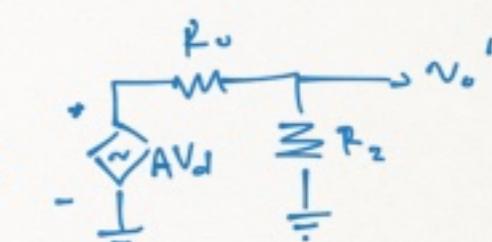



P7-2 CONT'D

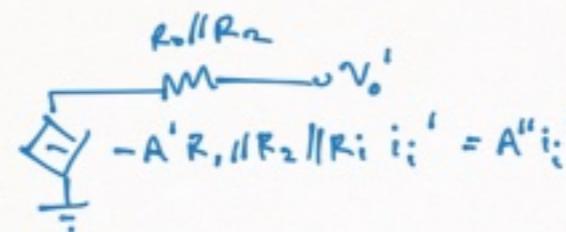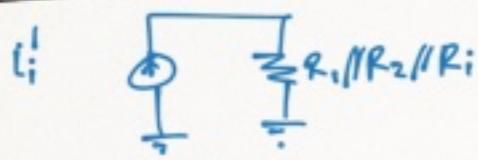

$$A_t = \frac{v_o}{i_i} = \frac{-A''}{1-A''B} \approx \frac{1}{\beta} = -R_2 \quad \text{accurate for very large } A$$

$$A_{fv} = \frac{v_o}{v_i} = \frac{v_o}{i_i R_1} = \frac{-R_2}{R_1}$$

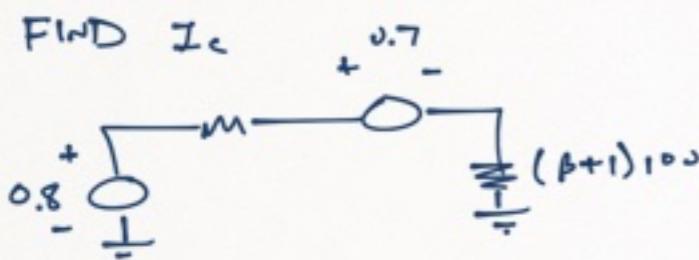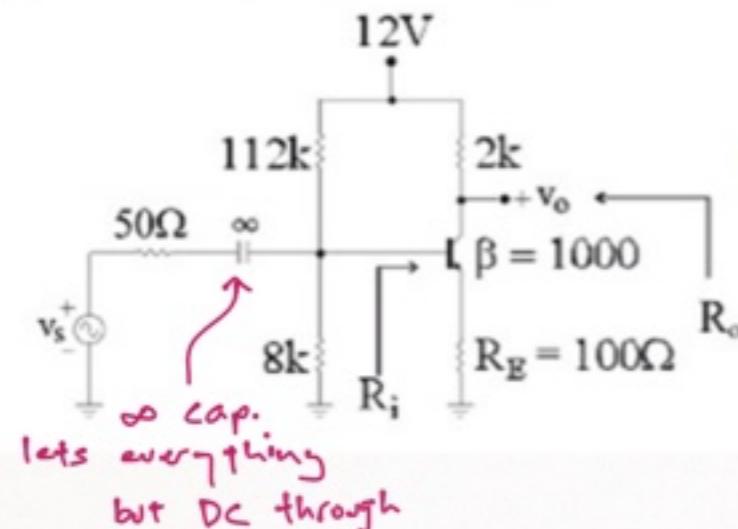
5. Analyze the circuit shown in figure 4 using feedback techniques (the best topology is the series-series topology) with RE forming the feedback network and for the transistor having an $r_o = 50 \text{ k}\Omega$ to find the small-signal voltage gain of the amplifier, $A_v = v_o/v_s$, R_i and R_o all at mid band.




$$I_B = \frac{0.8 - 0.7}{100\text{k} + 7.47\text{k}} = 0.93\text{nA}$$

$$I_C = 0.93\text{mA} \quad r_{\pi} = 26.7\text{k} \quad g_m = 37.2 \text{ mV}$$

small signal

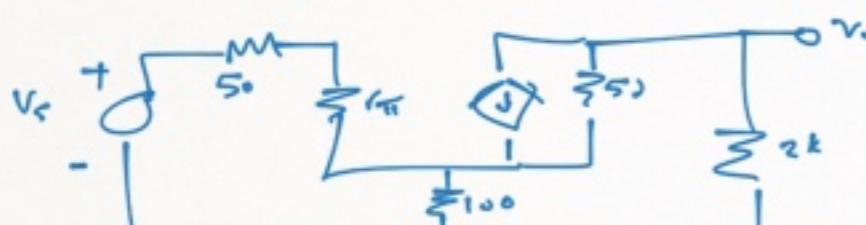

FEED BACK NETWORK

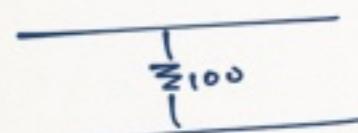

series-series

$$V_1 = z_{11} I_1 + z_{12} I_2$$



$$V_2 = z_{21} I_1 + z_{22} I_2$$

for fun we include r_o in this problem
 ↳ error for doing so is about 1% b/c of magnification due to feedback.

$$z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 100$$

$$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = 100$$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = 100$$

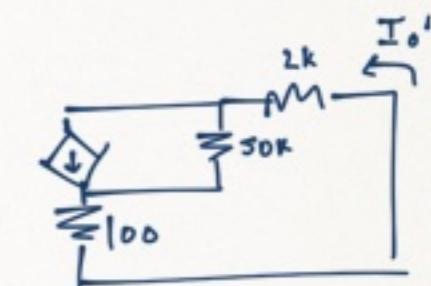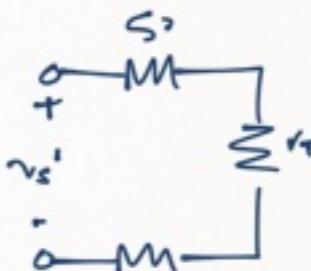

$$A' = \frac{I_o'}{V_s} = \frac{37.2 \text{ mV}}{\frac{50\text{k}}{100\text{k} + 2\text{k} + 0.1\text{k}} + 100} = 35.4 \text{ mV}$$

$$A'_f = \frac{I_o}{V_s} = \frac{35.4 \text{ mV}}{1 + 100 (35.4 \text{ mV})}$$

$$\text{since } V_o = -I_o \cdot 2\text{k}$$

$$A_V = \frac{V_o}{V_s} = -\frac{I_o \cdot 2\text{k}}{V_s} = -A'_f \cdot 2\text{k} = -15.6$$

$$R_{int} = (1 + A' f) (50 + r_{\pi} + 100) = 123\text{k}$$


$$R_i = 123\text{k} - 50 = 123\text{k}$$

$$R_{out} = (1 + A' f) \cdot R_{out} = 1.54 (50 + 2\text{k} + 100) = 236.5\text{k}$$

$$R_o' = 236.5\text{k} - 2\text{k} = 234.5\text{k} \quad R_o = 2\text{k} // 234.5\text{k} = 1.98\text{k}$$

in notes he put
Vs here. it shouldn't be

MIDTERM Q2

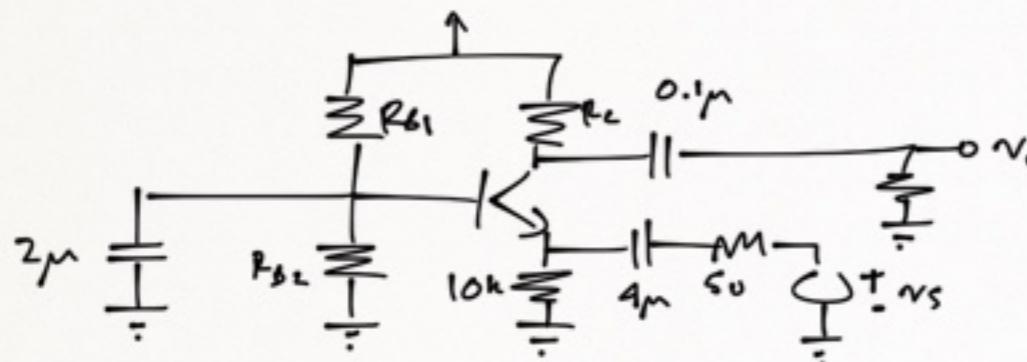

$$V_E = 10k(0.5mA) = \frac{1}{3}V_{cc} - V_B = 5.7$$

$$I_C \approx I_E \rightarrow R_C = 10k$$


$$I_I = 0.1 I_E$$

$$g_m = 20mV
r_\pi = 5k$$

$$R_{B1} = \frac{15 - 5.7}{0.05mA} = 186k$$

$$R_{B2} = \frac{5.7}{I_I - I_B} = \frac{5.7}{0.045mA} = 127k$$

$A_M = 55M$ @ midband

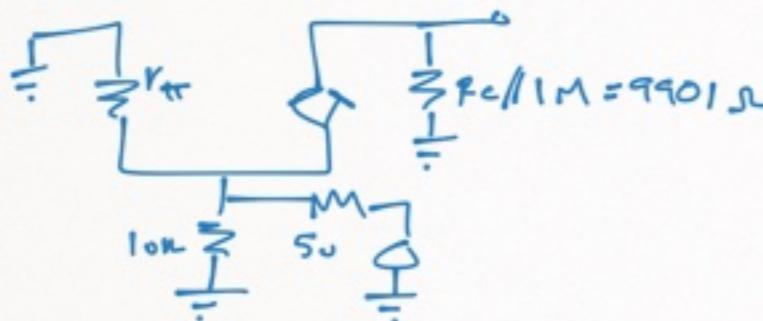

$$A_M = \frac{N_s}{N_\pi} \cdot \frac{V_T}{V_S}$$

$$\frac{N_s}{N_\pi} = -g_m \frac{N_\pi}{V_T} \cdot 9901 = -175 \frac{V}{V}$$

$$N_\pi = \left(-N_s \frac{V_T}{1+r_\beta} \parallel 10k \right) \left(\frac{r_\pi}{1+r_\beta} / (10k + 50) \right) = -\frac{N_s 49.2}{99.2} = -0.495 \text{ Vs}$$

$$\omega_{NP2} = \frac{1}{L_P F \cdot 9.7k} = 1.01 \cdot 10^4 \frac{\text{rad}}{\text{s}}$$

$$\omega_{NP1} = \frac{1}{10pF \cdot 4\pi \cdot 2 / 50} = 4.03(10^9) \frac{\text{rad}}{\text{s}}$$


$\omega_{NSdB} = 1.01(10^8) \frac{\text{rad}}{\text{s}}$ \curvearrowleft B/C ω_{NP1} & ω_{NP2} are more than a decade apart

$$\omega_{LP2} = \frac{1}{C_B R_{B2}} = \frac{1}{2\mu F \cdot 75.5k} = 6.6 \frac{\text{rad}}{\text{s}}$$

$$\omega_{LP3} = \frac{1}{0.1nF \cdot 1.01M} = 9.9 \frac{\text{rad}}{\text{s}}$$

$$A_M = 98 \frac{V}{V}$$

Ex cont'd

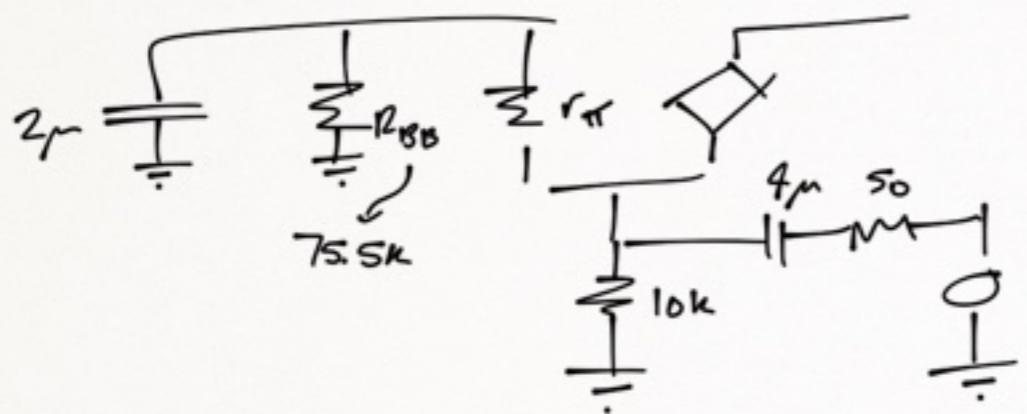

$$T_{C_{C_1}}^{sc} \Big|_{C_{C_1} \text{ short}} = f_n F(f_{q.s} + s_0)$$

$$T_{C_B}^{sc} \Big|_{C_{C_1} \rightarrow \infty} = Z_m \underbrace{\left(R_{BB} // \left(r_{pi} + (10k//s_0) | + \beta \right) \right)}_{\sim 75.5k//10k} =$$

$$\therefore \omega_{L3dB} = \frac{1}{C_{C_1}(77.5)} = 2.5(10^3) \frac{\text{rad}}{\text{s}}$$

Missing conclusion

OPEN-LOOP

$$G = \frac{1}{P_{OL}}$$

$$\frac{Y}{U} = k \frac{1}{P_{OL} + k}$$

$$k = k_d \left(\frac{s^2 + s \frac{k_p}{k_d} + \frac{k_i}{k_d}}{s} \right)$$

$$P + \frac{I}{s} + \frac{Ds}{\frac{1}{100s} + 1}$$

$$s^2 + s \frac{k_p}{k_d} + \frac{k_i}{k_d} = \emptyset$$

$$s = \pm \sqrt{\frac{k_p - 4k_p k_i + k_i}{2k_d}} \quad k_d \neq 0$$

$$\frac{k_d \left(s^2 + \frac{k_p}{k_d} s + \frac{k_i}{k_d} \right)}{(s + \frac{120}{18})(s + \frac{7}{570})(6700s^2) + k_d \frac{(s^2 + \frac{k_p}{k_d} s + \frac{k_i}{k_d})}{s}}$$

pick k_p, k_i, k_d such that zeros = poles

z_n

$$R-H \rightarrow k_v$$

$$T_v = \frac{2\pi}{\omega} @ k = k_v$$

$$\frac{1}{C_1 H + 1}$$

$$CE: \left(x + \frac{120}{13}\right) \left(x + \frac{7}{310}\right) (6700x^2)$$

$$\therefore 6700x^4 + 61997.4x^3 + 1396.53x^2 + 0_x + k_c$$

4 QUESTIONS

100 min designed for
150 to do it



PROBLEM # 2

MIDTERM

common collector

nothing or set 21/22
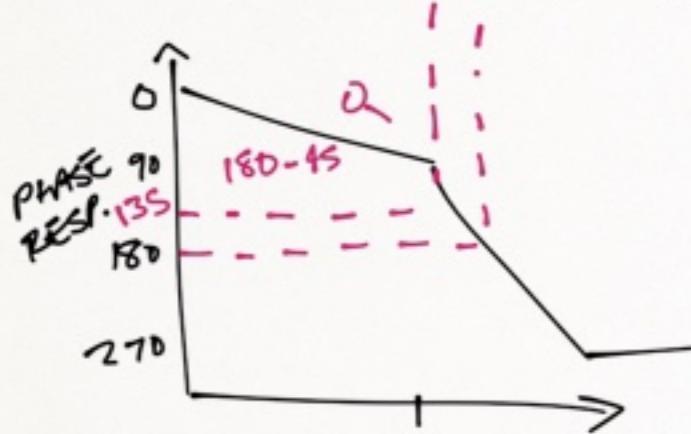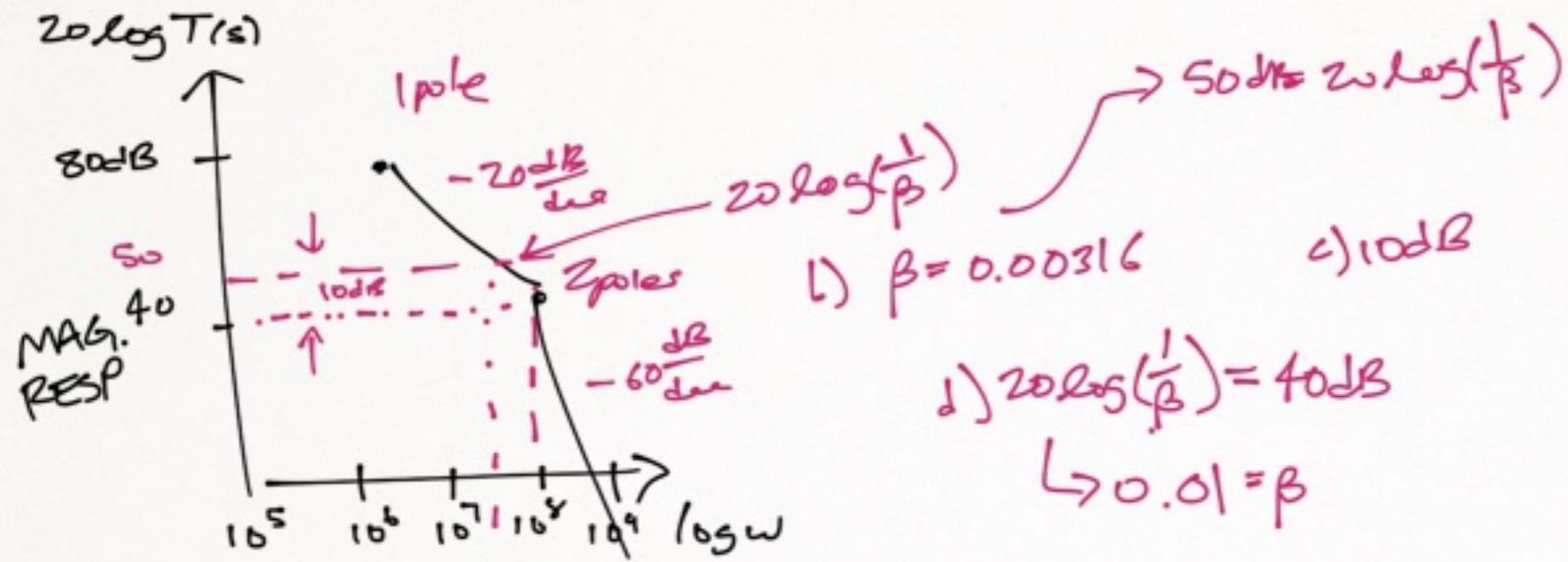
$$\begin{array}{c} z + z; - \\ \hline z - z; + \\ (\zeta + (3,2))(\zeta + (3,2)) \end{array}$$



#7 his solution annotated

STABILITY USING BODE PLOTS

