

# Phasors and Physics

Friday, January 8, 2016 10:56 AM

## 342 TOOA PHYSICS REVIEW

### LINEAR

$$v = \frac{d}{t}, a = \frac{v_f - v_0}{t}, d = v_0 t + \frac{1}{2} a t^2, v_f^2 = v_0^2 + 2 a d, \bar{F} = m \bar{a}$$

### ANGULAR

$$\begin{array}{l} r \text{ rpm} \rightarrow n \\ \text{rad/s} \rightarrow \omega \end{array} \quad \begin{array}{l} 360^\circ = 2\pi \text{ radians} \\ 1 \text{ radian angle} \approx 60^\circ \end{array}$$

$$\omega = \frac{\theta}{t}, \alpha = \frac{\omega_f - \omega_0}{t}, \theta = \omega_0 t + \frac{1}{2} \alpha t^2, \omega_f^2 = \omega_0^2 + 2 \alpha \theta, \bar{\Sigma} = \bar{R} \times \bar{F}$$
$$\bar{\Sigma} = I \bar{\alpha}$$

↑  
angular  
mass  
(kg/m²)

### ENERGY

$$\bar{W} = \bar{F} \cdot \bar{d}$$

must find component of force in direction.

$$W = T \theta$$

Types:

- 1. Kinetic energy  $\rightarrow W_k = \frac{1}{2} m v^2 / W_k = \frac{1}{2} I \omega^2$
- 2. Potential energy
- 3. Electric energy
- 4. Magnetic energy
- 5. Heat

### POWER

Do work in an interval, the rate at which we use energy

$$\text{Watt} = \frac{\text{Joules}}{\text{sec.}} \quad 1 \text{ HP} \equiv 745.7 \text{ W}$$

$$\text{LINEAR} \quad P = \frac{W}{t} = F v \quad \text{ANGULAR} \quad P = \frac{W}{t} = \frac{T \theta}{t} = T \omega$$

Ex) A car has a 300HP engine. It is 1705kg and can accelerate from 0 to 100kPH in 5.6 seconds. Its tires have a diameter of 83.2 cm.

what is the efficiency of the gearbox?  
what is the transmission system?

$$a = \frac{100 \text{ bhp}}{5.6 \text{ s}} = 4.96 \text{ m/s}^2$$

$$F = ma = (1705 \text{ kg})(4.96 \frac{\text{m}}{\text{s}^2}) = 8460 \text{ N}$$

$$W = F \cdot d = 8460 \text{ N} \cdot \frac{83.2 \text{ cm}}{2} = 35195$$

$$W = F \cdot d = 8460 N \cdot \frac{83.2 \text{ cm}}{2} = 35195$$

$$P = \frac{35195}{5.6 \text{ s}} = 628 \text{ W} \rightarrow 0.8422 \text{ hp}$$

$$\text{efficiency, } \eta_m = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{0.8422 \text{ hp}}{300 \text{ hp}} = 0.28\%$$

## 342 TOOB PHASORS REVIEW

### PHASOR 01

$$3+j4$$

~ this is only a representation of a complex number

### PHASOR 02

original ammeters measured average current through them

so when measuring AC signals, they measured  $\phi A$

because the average of a sinusoidal wave is zero.

So, to measure them we square it then take the average, but then we need to convert  $A^2$  back to  $A$ , so we square-root it:

$$\sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \quad (\text{root of the mean of the square of the current - RMS})$$

### EFFECTIVE VALUE, $I_{\text{eff}}$

A DC current that transmits same amount of energy in the same amount of time as the original AC  $i(t)$ .

TO RELATE  $i(t) \nparallel I_{\text{eff}}$

$$RI_{\text{DC}}^2 = \frac{1}{T} \int_0^T R i^2(t) dt$$

↑ power for DC current      ↗ average power for AC current

$$I_{\text{DC}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

↑ effective value of

a current  
is its RMS  
value

## EFFECTIVE VALUE OF A SINEOIDAL CURRENT (aka RMS value)

$$i(t) = I_{\text{peak}} \sin(\omega t + \Theta)$$


---


$$I_{\text{DC}} = \sqrt{\frac{1}{T} \int_0^T I_{\text{peak}}^2 \sin^2(\omega t + \Theta) dt} = \frac{I_{\text{peak}}}{\sqrt{2}}$$

$$AC: \quad i(t) = A \sin(\omega t + \phi)$$

This has the same power as  
a DC current of  $\frac{A}{\sqrt{2}}$

M is the effective value of current  $i(t)$

$$M = \frac{A}{\sqrt{2}} \quad \leftarrow \text{RMS value}$$

$$i(t) = \sqrt{2} M \sin(\omega t + \theta)$$

AC Ammeters/ AC voltmeters measure the RMS value.

↳ in power systems, we are by default talking about RMS voltages & currents

## PHASOR 03

elements in a circuit apply operations on a current or voltage:

$v(t) = R \cdot i(t)$  ← resistor multiplies by  $R$

$$v(t) = L \cdot \frac{di(t)}{dt} \leftarrow \text{inductor differentiates}$$

$$v(t) = \frac{1}{C} \int i(t) dt \leftarrow \text{capacitor integrates}$$

$$v(t) = V_{\max} \sin(\omega t + \theta)$$

amplitude  
 frequency  
 in  $\frac{rad}{s}$   
 $(2\pi f)$   
 in Hz

phase shift  
 in rad

## PHASOR NOTATION (Steinmetz Notation)

$$v(t) = \sqrt{2} V_{rms} \sin(\omega t + \theta)$$

$$\bar{V} = V_{RMS} \times \theta$$

$$v_1(t) = 100\sqrt{2} \sin\left(377t + \frac{30\pi}{180}\right)$$

$$v_2(t) = 70\sqrt{2} \sin(377t - \frac{15\pi}{180})$$

$$v_3(t) = 90\sqrt{2} \sin(377t + \frac{45\pi}{180})$$


30°

$$\bar{V}_1 = (100 \times 30)$$

$$\bar{V}_2 = (704 - 15)$$

$$\bar{v}_3 = (90 \times 45)$$

$$= (237.98 \times 23.68)$$

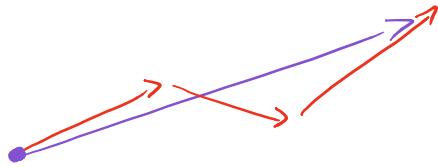

$$v_{\text{sum}}(t) = 237.9 \sqrt{2} \sin(377t + \frac{23.7\pi}{180})$$

multiplying by  $j\omega$  is the equivalent to differentiating in the time domain

$$v = L \frac{di(t)}{dt} \rightarrow \bar{V} = j\omega L \bar{I}$$

dividing by  $j\omega$  is equivalent to integrating in the time domain

$$v = \frac{1}{C} \int i(t) dt \rightarrow \bar{V} = \frac{\bar{I}}{j\omega C}$$

PHASOR DOMAIN

$$\bar{V} = R\bar{I}, \bar{V} = j\omega L \bar{I}, V = \frac{\bar{I}}{j\omega C} = -j \frac{\bar{I}}{\omega C}$$


IMPEDANCES (in Ohms)

$$\bar{Z}_R = R, \bar{Z}_L = j\omega L, \bar{Z}_C = -j \frac{1}{\omega C}$$

using this generalized Ohms law  $\bar{V} = \bar{I}\bar{Z}$ , we can use traditional tools KVL, KCL, & MNA just like we used to.

↳ just represent elements by their impedances & voltages/currents by phasors

#### PHASOR Q4

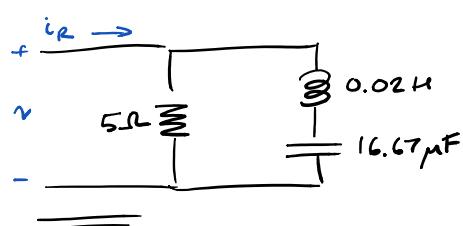

$$v(t) = 50\sqrt{2} \sin(2000t - \frac{90\pi}{180}) V$$

↑ RMS value      ↑ frequency      what's  $i_R(t)$ ?      phase shift

① write everything as a phasor

$$\bar{V} = (50\sqrt{2} \angle -90^\circ)$$

② represent all elements by their impedances

$$\bar{Z}_R = 5\Omega$$

$$\bar{Z}_L = j\omega L = j2000 \cdot 0.02 = j40\Omega$$

$$\bar{Z}_C = -j \frac{1}{\omega C} = -j \frac{1}{2000 \cdot 16.67} = -j30\Omega$$

$$\bar{Z}_L + \bar{Z}_C = j40 - j30 = j10\Omega$$

$$\bar{Z}_{\text{total}} = \bar{Z}_R // (\bar{Z}_L + \bar{Z}_C) = 5 // j10 = 4 + j2$$

③ Find  $\bar{I}_T$  phasor


$$\bar{I}_T = \frac{\bar{V}_T}{\bar{Z}_{TOTAL}} = \frac{(50 \angle -90^\circ)}{(4, 2)} = (-5, -10) = 11.18 \angle -116.6^\circ$$

④ convert from phasor domain to time domain

$$i(t) = \sqrt{2} (11.18) \sin(2000t - 116.6^\circ)$$

↑  $\sqrt{2}$  is to convert RMS to peak V      ↗ mind your sign, - means subtract, + means add

### PHASOR OS

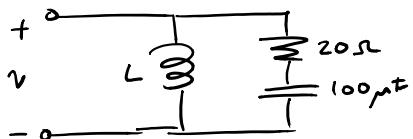

$$v(t) = 100\sqrt{2} \sin(500t) \quad \text{what's } L?$$

$$i(t) = 2.5\sqrt{2} \sin(500t)$$

① phasorify  $V \neq I$

$$\bar{V} = (100 \angle 0^\circ) = 100V$$

$$\bar{I} = (2.5 \angle 0^\circ) = 2.5A$$

② impedancey  $R, L, C$

$$\bar{Z}_R = 20, \bar{Z}_C = -j \frac{1}{\omega C} = -j \frac{10^6}{500 \cdot 100} = -20j \Omega, \bar{Z}_L = j\omega L = j500 \cdot L$$

$$\bar{Z}_{TOTAL} = j500L // (20 - 20j) \quad \text{don't need}$$

③ Ohm's law

~~$$\bar{V} = \bar{I}\bar{R} \rightarrow \frac{100 \angle 0^\circ}{2.5 \angle 0^\circ} = j500L // (20 - 20j)$$~~

~~$$\frac{100}{2.5} = 40 = \frac{1}{\frac{1}{j500L} + \frac{1}{20-20j}}$$~~

wrong strategy

$$\bar{I}_{RC} = \frac{\bar{V}}{\bar{Z}_R + \bar{Z}_C} = \frac{100}{20-20j} = (2.5, 2.5) = (3.536 \angle 45^\circ)$$


$$\bar{I}_L = \bar{I} - \bar{I}_{RC} = 2.5A - (3.536 \angle 45^\circ) = 2.5 \angle -90^\circ$$

$$\bar{Z}_L = \frac{\bar{V}}{\bar{I}_L} = \frac{100}{2.5 \angle -90^\circ} = 40 \angle 90^\circ \Omega$$


$$\bar{Z}_L = j\omega L \rightarrow L = \frac{\bar{Z}_L}{j\omega} = \frac{40 \angle 90^\circ}{j500} = 0.08 \angle 0^\circ = \boxed{0.08H}$$

### PHASOR OS




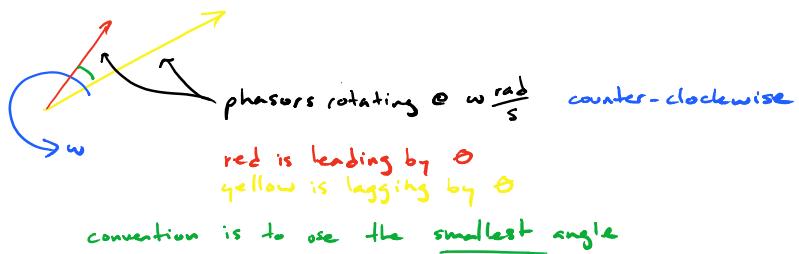


### IN AN INDUCTOR

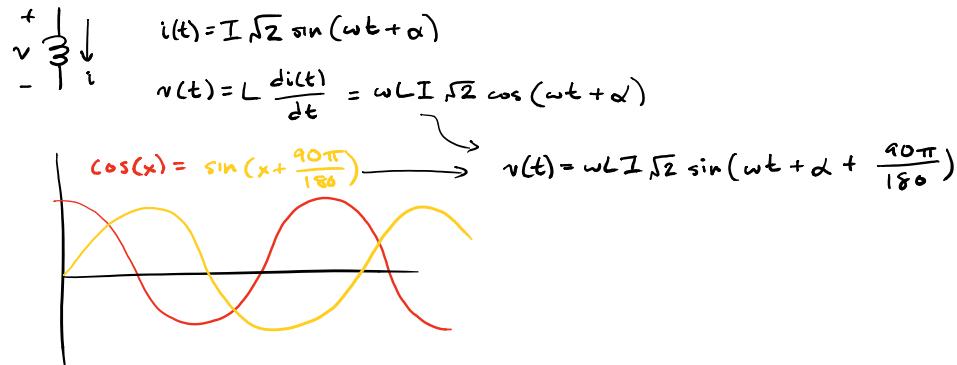

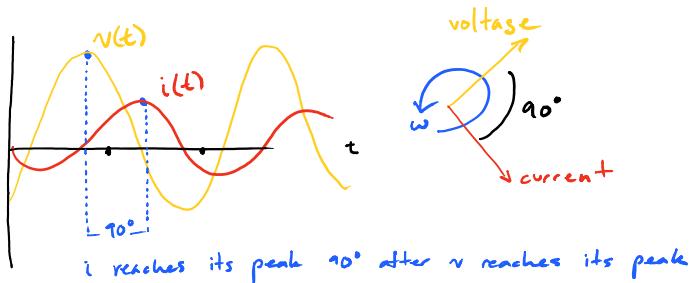
In an inductor, the current lags behind the voltage by  $90^\circ$   
 ↳ this makes sense b/c inductors slow change in current



### IN A CAPACITOR

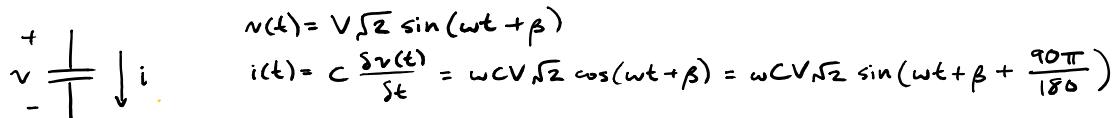


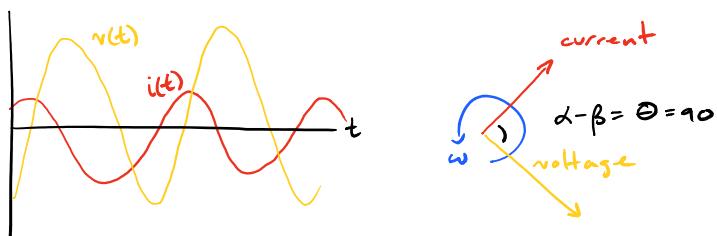In a capacitor, the current leads the voltage by  $90^\circ$   
 ↳ this makes sense b/c capacitors slow change in voltage.


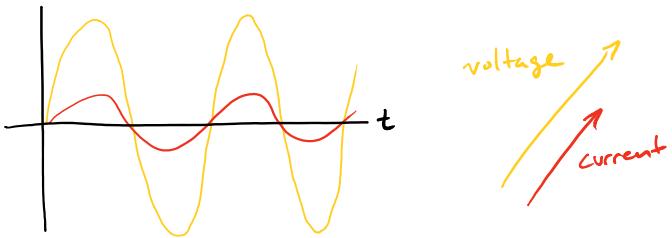
### IN A RESISTOR

In a resistor, the voltage and current phase are the same



### PHASOR 07

In a circuit AC steady state, all the voltages and currents have the same sinusoidal frequency,  $\omega$

The power also varies sinusoidally, but with frequency  $2\omega$

↳ positive part of the time/negative part of the time  
ie. absorbs power/delivers power in variation

$$\begin{array}{c}
 + \quad | \quad I \\
 V \quad \square \quad \\
 - 
 \end{array}
 \quad
 \begin{aligned}
 v(t) &= \sqrt{2} V \sin(\omega t + \alpha) \\
 i(t) &= \sqrt{2} I \sin(\omega t + \beta)
 \end{aligned}$$

$$\text{absorbed power: } p(t) = v(t) i(t)$$

$$= 2VI \sin(\omega t + \alpha) \sin(\omega t + \beta)$$

$$\text{using } \sin(x+y) = \sin x \cos y + \cos x \sin y$$

$$\text{then } \sin^2 x = \frac{1 - \cos 2x}{2}, \cos^2 x = \frac{1 + \cos 2x}{2}, \sin x \cos x = \frac{\sin 2x}{2}$$

$$\begin{aligned}
 p(t) &= VI \cos(\alpha - \beta) - VI \cos(2\omega t + \alpha + \beta) \\
 &\quad \underbrace{\text{constant}}_{\text{function of time}}
 \end{aligned}$$


current phase shift &  
voltage phase shift

average of a cosine w/ respect to time = 0

$$P = VI \cos(\alpha - \beta)$$

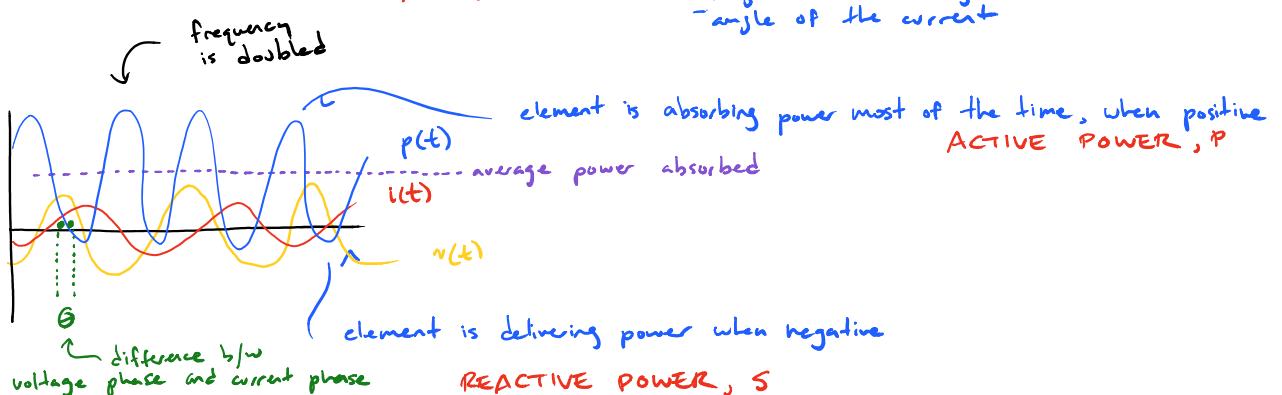**ACTIVE POWER**

angle of the voltage  
- angle of the current



**APPARENT POWER, S**

$$S = VI \quad (\text{a real number})$$

units Volt-Ampères

**ACTIVE POWER, P**

$$P = VI \cos \theta \quad (\text{a percentage of the apparent power})$$

This is the average power, units Watts

The percentage of apparent power that becomes active power is the power-factor

$$PF = \cos \theta$$

### REACTIVE POWER, Q

$$Q = VI \sin \theta \quad (\text{power not used})$$

units Volt-Ampere Reactive (VARs)


### PHASOR 07b

$$v(t) = \sqrt{2} V \sin(\omega t + \alpha), \quad i(t) = \sqrt{2} I \sin(\omega t + \beta)$$

$$p(t) = VI \cos(\alpha - \beta) - VI \cos(2\omega t + \alpha + \beta)$$

average

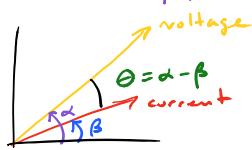
$$P = VI \cos(\alpha - \beta) \quad \begin{matrix} \uparrow \\ \text{RMS values} \end{matrix}$$




$$S = V_{\text{RMS}} \cdot I_{\text{RMS}} \equiv VA$$

$$P = V_{\text{RMS}} I_{\text{RMS}} \cos(\alpha - \beta) \equiv W$$
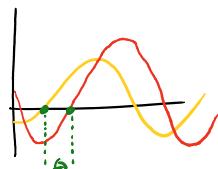
$$Q = V_{\text{RMS}} I_{\text{RMS}} \sin(\alpha - \beta) \equiv VAR$$



### POWER TRIANGLE

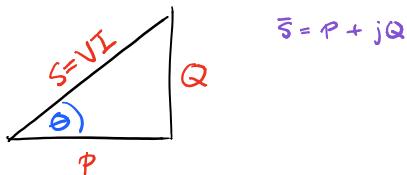

PHASORS:  $\bar{V} = V_{\text{RMS}} \angle \alpha$ ,  $\bar{I} = I_{\text{RMS}} \angle \beta$

COMPLEX POWER IS THE PRODUCT OF THE V PHASOR WITH THE CONJUGATE OF I.


$$\bar{S} = \bar{V} \bar{I} = V_{\text{RMS}} I_{\text{RMS}} \angle (\alpha - \beta)$$


FOR RESISTORS:  $P = R I_{\text{RMS}}^2 = \frac{V_{\text{RMS}}^2}{R}, \quad Q = \emptyset$

FOR INDUCTORS/CAPACITORS:  $X = \omega L \quad X = -\frac{1}{\omega C}$   
reactance  $P = \emptyset, \quad Q = X I_{\text{RMS}}^2 = \frac{V_{\text{RMS}}^2}{X}$
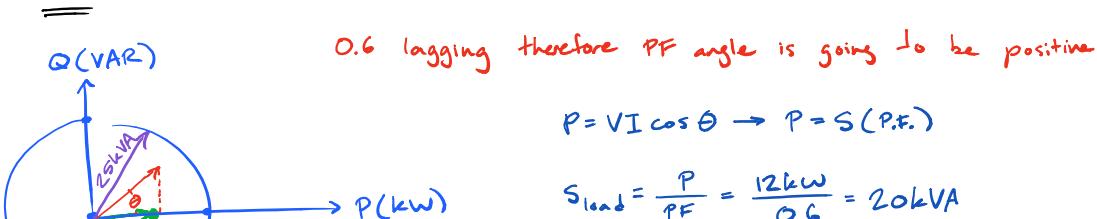
### PHASOR 09

- Ex) A 25 kVA transformer supplies a load of 12 kW at a PF of 0.6 lagging. Find the percentage of full load the transformer is carrying.




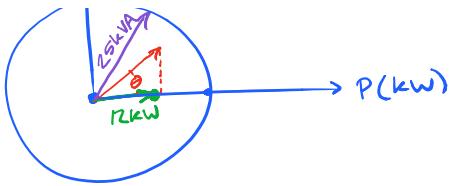

$$S_{load} = \frac{P}{PF} = \frac{12kW}{0.6} = 20kVA$$


$$\% \text{ load} = \frac{S_{load}}{S_{max}} = \frac{20kVA}{25kVA} = 80\%$$

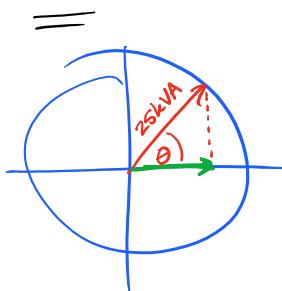Ex) cont'd How much more kW of resistive load can we add without overloading the transformer?



~~$0.6 = \cos \theta$~~

~~$\theta = \cos^{-1}(0.6) = 53.13^\circ$~~

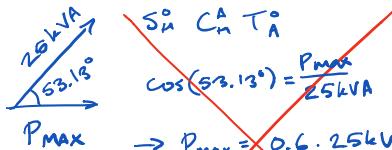
 ~~$S_{in} C_A T_A$~~ 


~~$\cos(53.13^\circ) = \frac{P_{max}}{25kVA}$~~

~~$\rightarrow P_{max} = 0.6 \cdot 25kVA = 15kW$~~

~~$\rightarrow 15kW - 12kW = 3kW$~~

~~could add 3kW more of power~~

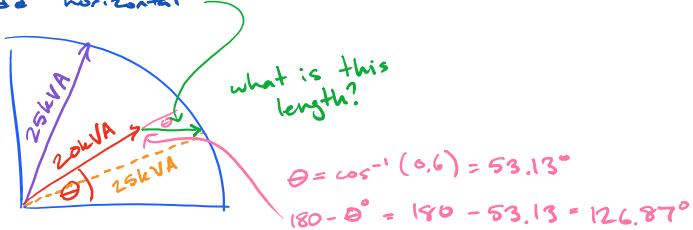Because it is resistive load, it is only active power we are adding so we only add horizontal



$$\theta = \cos^{-1}(0.6) = 53.13^\circ$$

$$(180 - \theta)^\circ = 180 - 53.13 = 126.87^\circ$$




Cosine law:  $a^2 = b^2 + c^2 - 2bc \cdot \cos A$

$$25^2 = x^2 + 20^2 - 2 \cdot x \cdot 20 \cos(126.87)$$

$$\downarrow \quad \begin{matrix} \text{not what} \\ \text{we're looking for} \end{matrix}$$

$$x = -15.2, x = 7.209$$

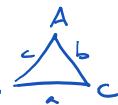

~~Could add 7.2kW more resistive load.~~

## PHASOR 10

Flow of Active Power (P) & Reactive Power (Q)

Slightly Inductive (absorbs active and reactive power)



$$\theta = \angle V_f - \angle I > 0^\circ$$

$$\cos \theta > 0 \rightarrow P > 0$$

$$\sin \theta > 0 \rightarrow Q > 0$$

Purely Inductive (absorbs only reactive power)



$$\theta = \angle V_f - \angle I = 90^\circ$$

$$\cos \theta = 0 \rightarrow P = 0$$

$\theta = \frac{1}{2}V_f - \frac{1}{2}I = 90^\circ$   
 $\cos \theta = 0 \rightarrow P = 0$   
 $\sin \theta = 1 \rightarrow Q = VI > 0$

Resistive (absorbs only active power, no reactive power)

$\theta = \frac{1}{2}V - \frac{1}{2}I = 0$   
 $\cos \theta = 1 \rightarrow P = VI > 0$   
 $\sin \theta = 0 \rightarrow Q = 0$

Capacitive (absorbs active power and produces reactive power)



$\theta = \frac{1}{2}V - \frac{1}{2}I < 0$   
 $\cos \theta > 0 \rightarrow P = VI \cos \theta > 0$   
 $\cos \theta < 0 \rightarrow Q = VI \sin \theta < 0$



Purely Capacitive (absorbs no active power, produces reactive power)

$\theta = \frac{1}{2}V - \frac{1}{2}I = -90^\circ$   
 $\cos \theta = 0 \rightarrow P = 0$   
 $\sin \theta = -1 \rightarrow Q < 0$

Generator Load (produces active power, absorbs reactive power)

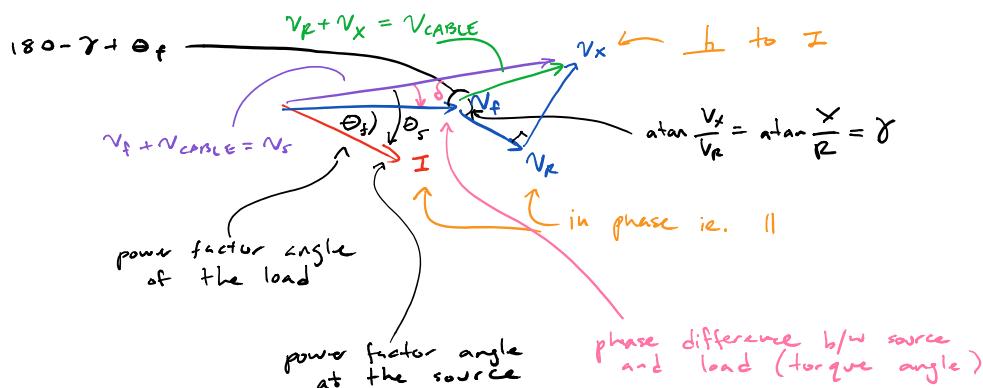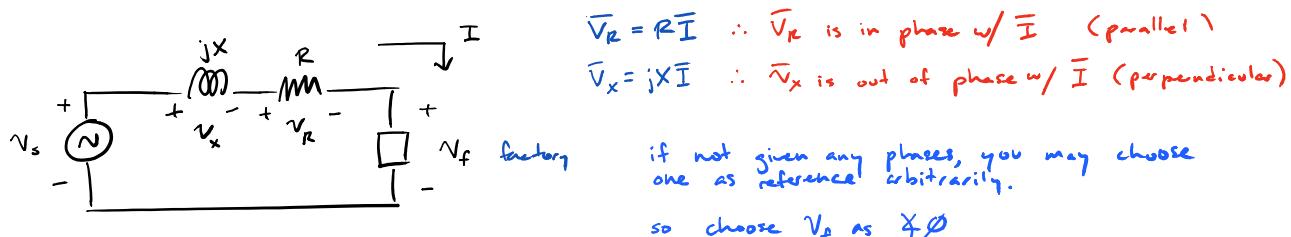$\theta = \frac{1}{2}V - \frac{1}{2}I, 180^\circ < \theta < 90^\circ$   
 $\cos \theta < 0 \rightarrow P < 0$   
 $\sin \theta > 0 \rightarrow Q > 0$



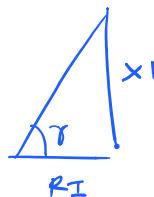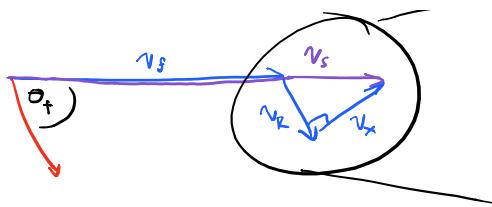

on load, only  $\times \rightarrow$


$$\gamma = \arctan \frac{X}{R} = \arctan \frac{X}{R}$$

## PHASOR 12

A real coil has a resistance  $R$  and an inductance  $L$ . The coil is represented by a model consisting of in series  $R$  in series with its inductance  $L$ . To determine  $R$  and  $L$ , the coil is connected in series with an external resistor  $R_X = 10$  ohms. Then we apply a sinusoidal voltage of 60Hz, 36V to the entire group "coil plus  $R_X$ ". We measure the voltage in the coil  $V_{coil} = 22.4$ V, and the voltage in the external resistor  $V_{Rx} = 20$ V. Calculate the values of  $R$  and  $L$ , the resistance and inductance of the coil.

if  $\Theta_f = \gamma$  greater difference b/w mag. voltage at factory and voltage at source



↳ more voltage drop

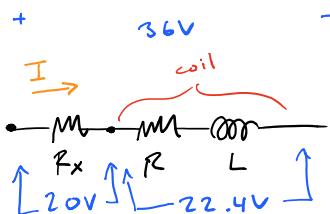

Choose phase reference  $I @ 0^\circ$

Both  $V_{Rx}$  &  $V_L$  are in phase

voltage of entire group

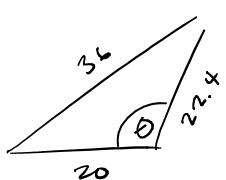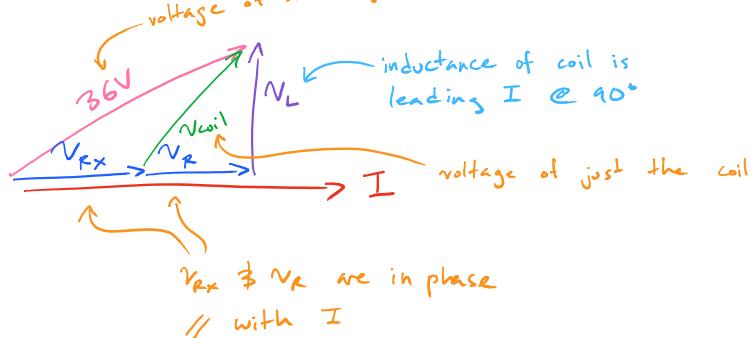

$$\Theta = \arccos \left[ (36^2 - 20^2 - 22.4^2) / (-2 \cdot 20 \cdot 22.4) \right] = 116.10^\circ$$



$$\alpha = 180^\circ - \Theta = 63.90^\circ$$

$$V_R = 22.4 \cos \alpha = 9.86V$$

$$V_L = 22.4 \sin \alpha = 20.1V$$

$$R = \frac{9.86}{2A} = 4.93 \Omega$$

$$V_L = 2X \rightarrow X = 10.0 \Omega$$

$$X = 20\pi f L \rightarrow L = \frac{10.0}{2\pi f} = 26.68 mH$$



