 


Address Decoding Techniques


Partial Address Decoding

- Here only a **sub-set** of the unused **address** lines are employed by the decoder circuit.
- Partial decoding can lead to a reduction in
 - **Complexity** of decoder (fewer gates)
 - **Propagation delay** of the decoder
 - **Power consumption** (fewer gates)
 - PCB/chip "**real-estate**" and **cost**
- Partial address decoders are particularly attractive when used with CPUs having a large address space i.e. **32/64 bit address**
- Going back to our very **1st** example of a memory system, (Lecture 3) we could design a simple **partial address** decoder for a system with **2K words** of Rom and Ram like this.
- With only two blocks to decode (**Rom** + **Ram**) we should only need to decode 1 address line e.g. **A23** could be used
- We could arrange for **M1** (Rom) to be enabled when **A23 = 0** and **M2** (Ram) to be enabled when **A23 = 1** thus both devices can never be selected at the same time. It also means there is still ROM located at address 0 (a requirement for the 68000).



Address Decoding Techniques

- However, there are drawbacks to partial decoding, for example take the circuit just considered.
- Because only **A23** was used by the address decoder, the other **11** address lines (**A22 - A12**) play no part in the decoding process and thus act as '**don't cares**' to the decoder.
- The effect of this is that both **2k word** memory blocks get '**mirrored**', in the memory map.
- That is, each block appears to the CPU to be **replicated 2048** times and appears as **4M words**. This is because **A22 - A12** plays no part (i.e. 11 address lines) and $2^{11} = 2048$
- This would certainly confuse a booting operating system searching for installed memory.
- Here the OS might conclude that the system has **8M bytes** of Ram instead of the **4K bytes** it really has which is *devastating* to say the least.

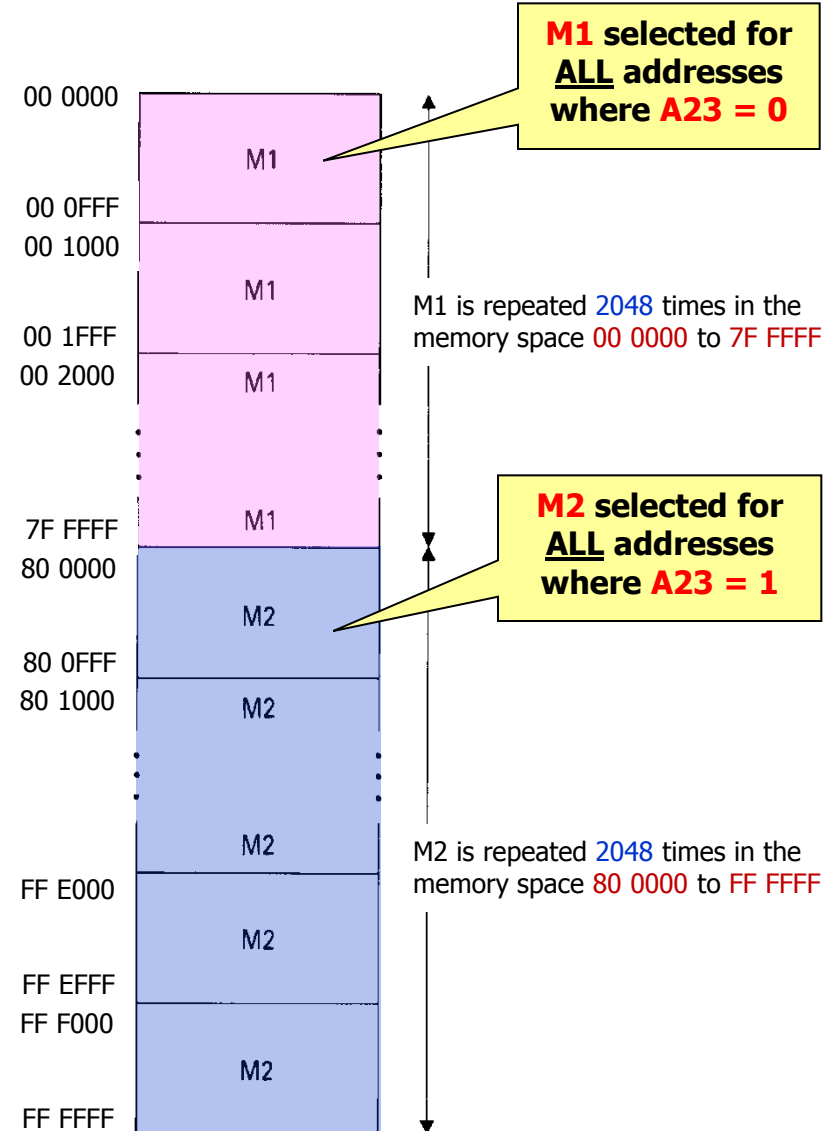

Partial Decoding: A more practical example

- Let's go back to the problem of the simple **Rom**, **Ram** and **Peripheral** mapping problem from lecture 3. That system comprised of the following

- **10K words** of Rom arranged as
 - A block of **2K (Rom1)** plus
 - A block of **8K (Rom2)**
- **2K words** of Ram (**Ram1**)
- **2 individual words** for Peripheral 1 (**Peri1**)
- **2 individual words** for Peripheral 2 (**Peri2**)

- The address table for a **FULL** address decoder scheme is **repeated** below for the sake of **comparison** and uses many gates to fully decode all unused address lines. Let's look at a **partial** decoding scheme.


Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	
000000-000FFF	0	0	0	0	0	0	0	0	0	0	0	0	x	x	x	x	x	x	x	x	x	x	x	Rom1
001000-001FFF	0	0	0	0	0	0	0	0	0	0	0	1	x	x	x	x	x	x	x	x	x	x	x	Ram1
004000-007FFF	0	0	0	0	0	0	0	0	0	1	x	x	x	x	x	x	x	x	x	x	x	x	x	Rom2
008000-008003	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	x	Peri1
008004-008007	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	x	Peri2

Solution using Partial Decoding

- With 5 chip select signals to produce, in *theory* only 3 address lines should be needed by our decoder ($2^3 > 5$).
- One possible address table for a simple memory map is illustrated below where only the 3 highest address lines are decoded (*it's common to use the highest address lines unless a specific base address is req'd*).

(**Note:** this address map is different to the original full address decoder from lecture 3 and has been chosen to maximise the advantages of *partial* address decoding, however *Rom1* is still at address 0).

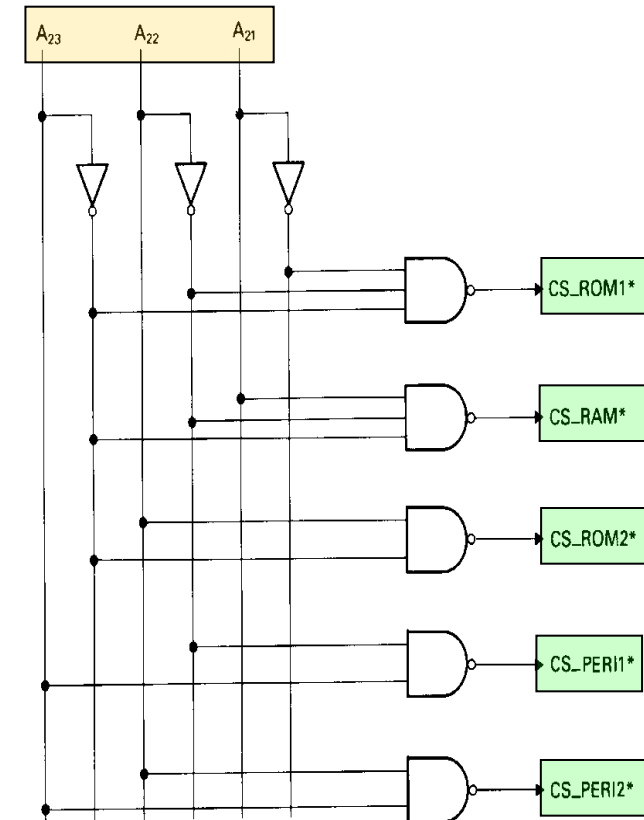- What is address range and size (including mirroring) of each block?



Logic Equations

$$\text{Rom1 CS}^* = \neg(\neg A_{23} \cdot \neg A_{22} \cdot \neg A_{21})$$

$$\text{Ram1 CS}^* = \neg(\neg A_{23} \cdot \neg A_{22} \cdot A_{21})$$

$$\text{Rom2 CS}^* = \neg(\neg A_{23} \cdot A_{22})$$

$$\text{Peri1 CS}^* = \neg(A_{23} \cdot \neg A_{22})$$

$$\text{Peri1 CS}^* = \neg(A_{23} \cdot A_{22})$$

Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1		
	0	0	0	ignored									x	x	x	x	x	x	x	x	x	x	x	x	Rom1
	0	0	1	ignored									x	x	x	x	x	x	x	x	x	x	x	x	Ram
	0	1	x	ignored									x	x	x	x	x	x	x	x	x	x	x	x	Rom2
	1	0	x										ignored									x	Peri1		
	1	1	x										ignored									x	Peri2		

Address Decoding Techniques

Exercise 11

- Design a **Partial** address decoder for a 68000 based system with **8K Words** of **EPROM** space, so that it responds to a **base address** of **\$00 8000**, using **8K byte** memory chips.


Solution 11

- Two chips are needed to give **8k x 16**. Each chip will use **13 address lines**, ($2^{13} = 8192$) **a0-a12** connected to **A1-A13** on the CPU leaving potentially **A14-A23** to feed the decoder.
- A Base address of **\$00 8000** = binary **[0000,0000,10xx,xxxx,xxxx,xxxx]**, i.e. when **A15 = logic 1**
- An address table is given below, along with a sample circuit.
- As a minimum solution to this problem, **A15** could be used as our **ROMSEL** signal as this would mean the device definitely responds to address **\$00 8000** but also to a lot of other addresses too.
- We could reduce the extent of mirroring and free up more space in the memory map for future expansion etc. if we just included **A23-A20 = 0** into the decoding logic. The ROM would still respond to the base address required but it might not "**start**" or be **limited** to that address.

Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	
	0	0	0	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Rom

Logic Equations
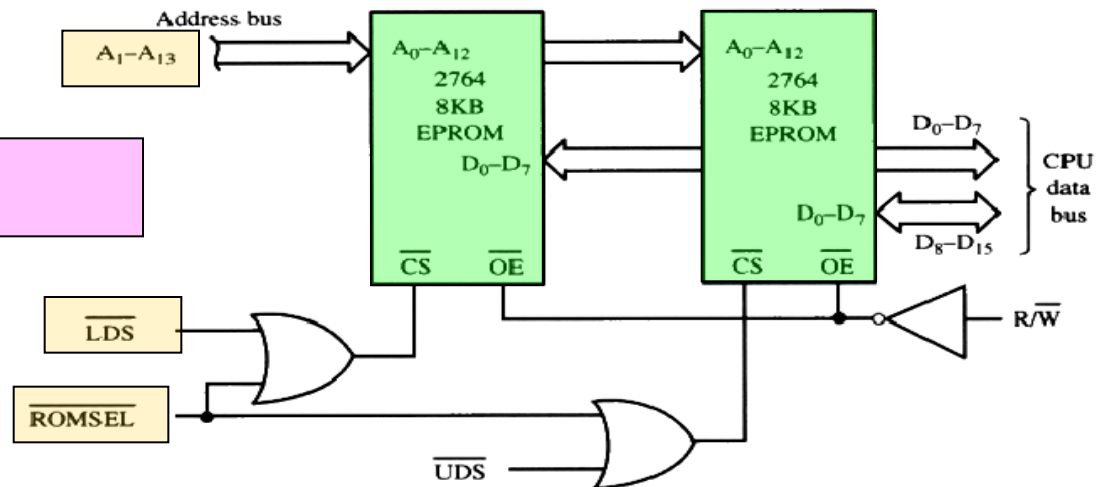
$$\overline{\text{ROMSEL}} = \overline{A_{23}} \cdot \overline{A_{22}} \cdot \overline{A_{21}} \cdot \overline{A_{20}}$$



Address Decoding Techniques

Exercise 12

- Design a partial address decoder for a 68000 based system that contains
 - 2M bytes of Eprom starting at \$00 0000 using 512k byte chips.
 - 2M bytes of Ram starting at \$20 0000 using 256k byte chips.
 - 64k bytes of I/O space starting at \$80 0000.

Solution 12

- For the EPROM we will need 4, 512k byte chips, organized as 2 banks of 512k words (512k = 19 address lines) or 1M byte.
- For the RAM we will need 8, 256k byte chips, organized as 4 banks of 256k words: RAM1 to RAM4 (256k = 18 address lines).
- The 64k IO Space = 32k words at \$80 0000 = 15 lines
- The address table is given below, while the logic equations for a simple partial decoder circuit is given alongside.
- The equations have been carefully chosen to fix the devices at the addresses specified and to ensure no overlap and to make banks contiguous within a block.

Logic Equations

$$\text{Eprom1} = \neg(\neg A_{23} \cdot \neg A_{21} \cdot \neg A_{20})$$

$$\text{Eprom2} = \neg(\neg A_{23} \cdot \neg A_{21} \cdot A_{20})$$

$$\text{Ram1} = \neg(\neg A_{23} \cdot A_{21} \cdot \neg A_{20} \cdot \neg A_{19})$$

$$\text{Ram2} = \neg(\neg A_{23} \cdot A_{21} \cdot \neg A_{20} \cdot A_{19})$$

$$\text{Ram3} = \neg(\neg A_{23} \cdot A_{21} \cdot A_{20} \cdot \neg A_{19})$$

$$\text{Ram4} = \neg(\neg A_{23} \cdot A_{21} \cdot A_{20} \cdot A_{19})$$

$$\text{IO} = \neg(A_{23})$$

Address	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	
	0	x	0	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Eprom (Bank1)
	0	x	0	1	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Eprom (Bank2)
	0	x	1	0	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Ram1 (Bank1)
	0	x	1	0	1	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Ram2 (Bank2)
	0	x	1	1	0	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Ram3 (Bank3)
	0	x	1	1	1	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	Ram4 (Bank4)
	1	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x	IO

Address Decoding Techniques

Block Address Decoding

- Block decoding partitions the CPU address space into equal sized blocks and can be used with both full and partial address decoding schemes.
- The resultant block size is dependent upon those address lines used by the block decoder.
- For example we could partition an address space of 64K into

- 4 blocks of 16k, or
- 8 blocks of 8k or
- 16 blocks of 4k etc.

- Once memory has been partitioned into blocks, full, partial or additional block decoders can subsequently be employed to refine and resolve the address map into smaller and smaller blocks.
- For example, in the case of a 64k system partitioned into 4 blocks of 16k, we could use additional block decoders to partition this into


- 4 blocks of 4k, or
- 8 blocks of 2k or
- 16 blocks of 1k etc.

Address Decoding Techniques

Block Decoders

- Fortunately for us, **devices** exist, often in the form of a single chip, to make block decoding solutions easy for us, or we can use **VHDL** for programmable logic.
- For example the **74138** is a simple **3 to 8 line decoder**, giving us the ability to partition memory into **8** equal sized blocks.
- A Pin Out and Truth Table for this device is illustrated below. It has 3 inputs (which could be fed to address lines), 8 outputs for 8 individual equal sized block select signals and 3 enable signal (*for further refinement of address range*).

INPUTS						OUTPUTS							
G ₁	$\overline{G_{2A}}$	$\overline{G_{2B}}$	C	B	A	Y ₀	Y ₁	Y ₂	Y ₃	Y ₄	Y ₅	Y ₆	Y ₇
0	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	1	X	X	X	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	0	1	1	0	1	1	1	1	1	1
1	0	0	0	1	0	1	1	0	1	1	1	1	1
1	0	0	0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	0	0	1	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1	1	1	1	0	1	1
1	0	0	1	1	0	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0

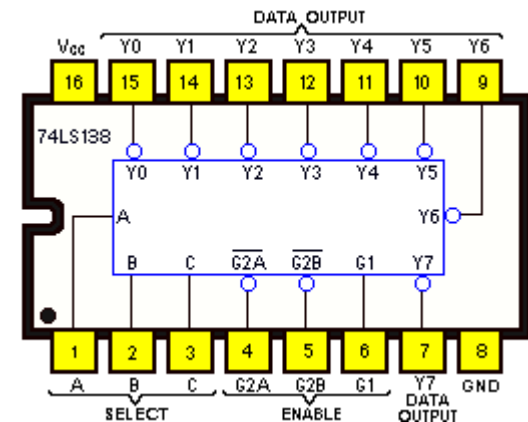

2 active low plus 1 active high enable

Example VHDL code for a simple 3-8 Decoder

```
LIBRARY      IEEE ;
USE          IEEE . STD_LOGIC_1164 . ALL ;

-----

-- 3 TO 8 Line Decoder

-----

ENTITY Decoder3to8Line IS
    PORT(  CBA      : IN  STD_LOGIC_VECTOR ( 2 downto 0 );           -- 3 bit input select bus
           G1, G2A, G2B : IN  STD_LOGIC ;                           -- 3 enable inputs
           Y7_Y0      : OUT STD_LOGIC_VECTOR ( 7 downto 0 )         -- 8 active low outputs as a bus
    );
END ;

-----


ARCHITECTURE Behavioural OF Decoder3to8Line IS
BEGIN
    PROCESS( CBA , G1 , G2A , G2B )
    BEGIN
        IF ( ( G1 = '1' ) AND ( G2A = '0' ) AND ( G2B = '0' ) ) THEN -- if device enabled
            IF ( CBA = "000" ) THEN Y7_Y0 <= "11111110" ;           -- if CBA = 000 set y0 to 0
            ELSIF ( CBA = "001" ) THEN Y7_Y0 <= "11111101" ;       -- else if CBA = 001 set y1 to 0
            ELSIF ( CBA = "010" ) THEN Y7_Y0 <= "11111011" ;       -- else if CBA = 010 set y2 to 0
            ELSIF ( CBA = "011" ) THEN Y7_Y0 <= "11110111" ;       -- else if CBA = 011 set y3 to 0
            ELSIF ( CBA = "100" ) THEN Y7_Y0 <= "11101111" ;       -- else if CBA = 100 set y4 to 0
            ELSIF ( CBA = "101" ) THEN Y7_Y0 <= "11011111" ;       -- else if CBA = 101 set y5 to 0
            ELSIF ( CBA = "110" ) THEN Y7_Y0 <= "10111111" ;       -- else if CBA = 110 set y6 to 0
            ELSE Y7_Y0 <= "01111111" ;                               -- else if CBA = 111 set y7 to 0
            END IF;
        ELSE -- if not enabled
            Y7_Y0 <= "11111111" ;
        END IF ;
    END PROCESS;
END ;
```

Note: Y7-Y0 assigned a value for each path in the process above. Result: combinatorial logic with no storage/latches

Address Decoding Techniques

Simple Block decoder schemes using a 74138

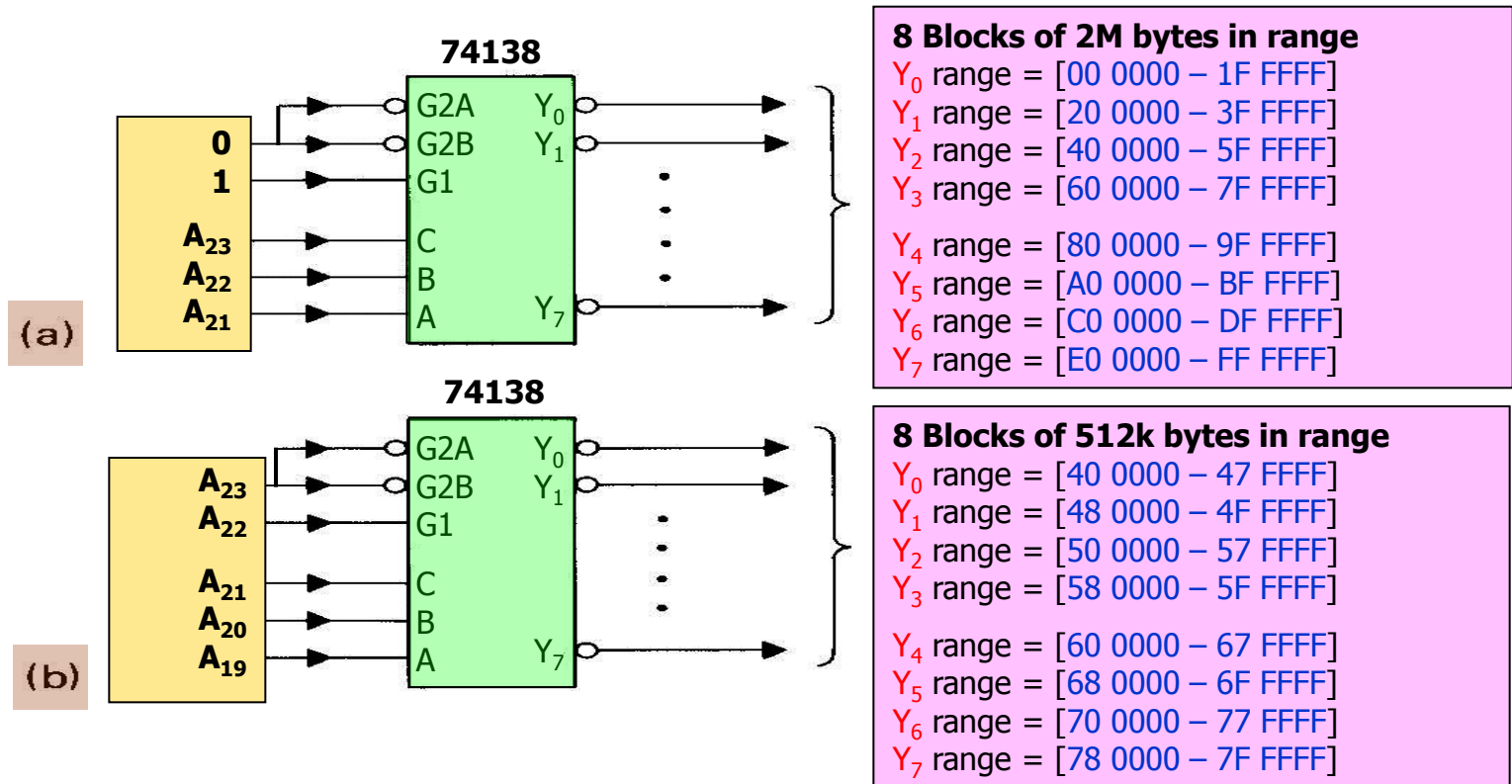- Circuit **a)** below is used to decode the upper 3 address lines of the 68000 address bus to provide 8 blocks of 2M bytes, i.e. address blocks in the range hex 00 0000 – 1F FFFF, 20 000 – 3F FFFF etc.
- Circuit **b)** makes use of the enable lines to assist in the decoding of 8 blocks in the lower quarter of the address space ($A_{23}, A_{22} = [0,1]$).




Address Decoding Techniques

More Block decoder schemes using 74138 (cont...)

- This uses two cascaded 74138 devices to provide more refined block decoding. **A23-A21** feed into the 1st device which provides block outputs of **2M bytes** (as before).

The **2nd output** from this device (**Y1**) which is enabled in the address range [**20 0000-3F FFFF**] is then used to enable a **2nd cascaded** device fed with address lines **A20-18**.

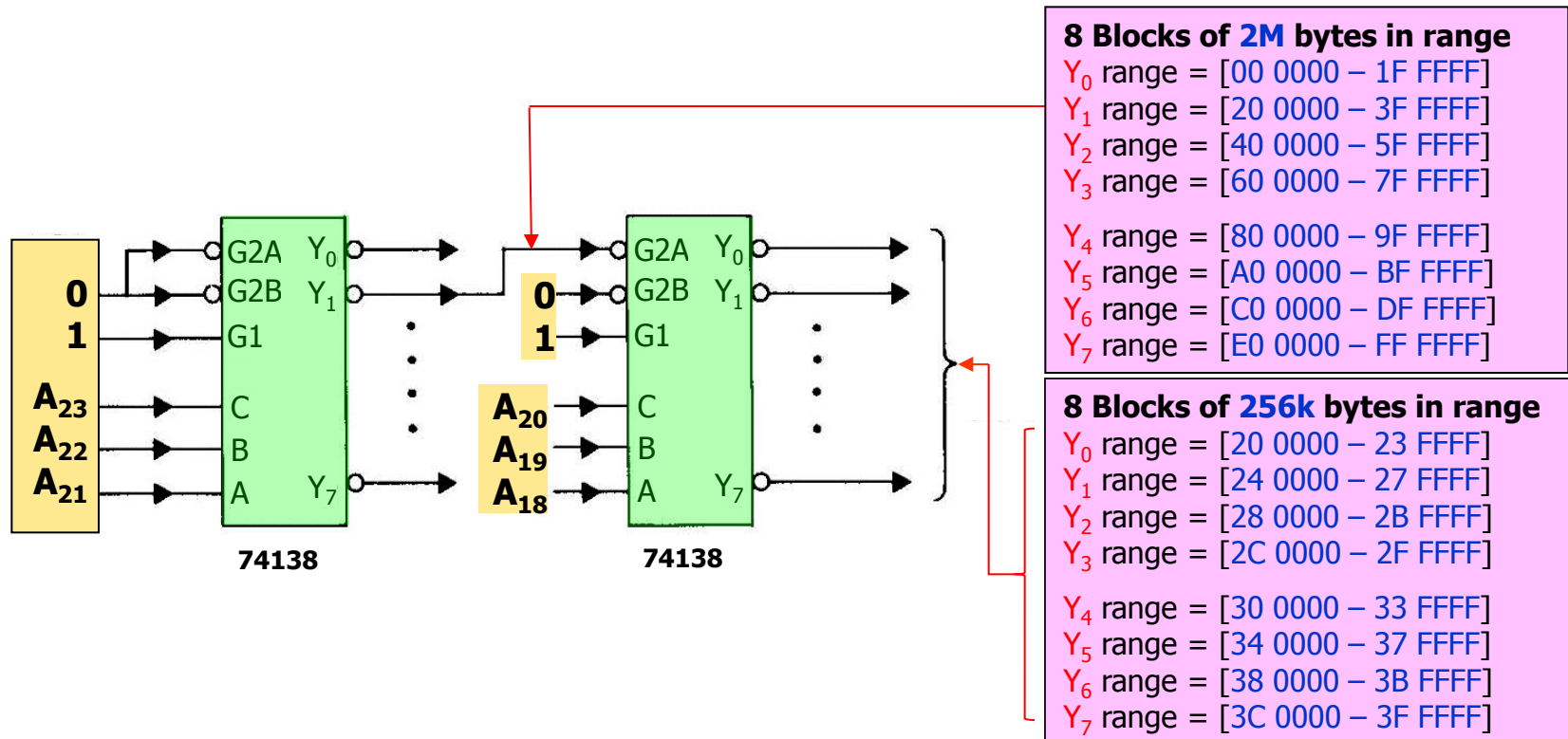
This **2nd** device decodes the address **20 0000-3F FFFF** into 8 smaller blocks of **256k** words in the range **20 0000-23 FFFF**, **24 0000-27 FFFF** etc.



Address Decoding Techniques

Sample Block decoder schemes using 74138 (cont...)

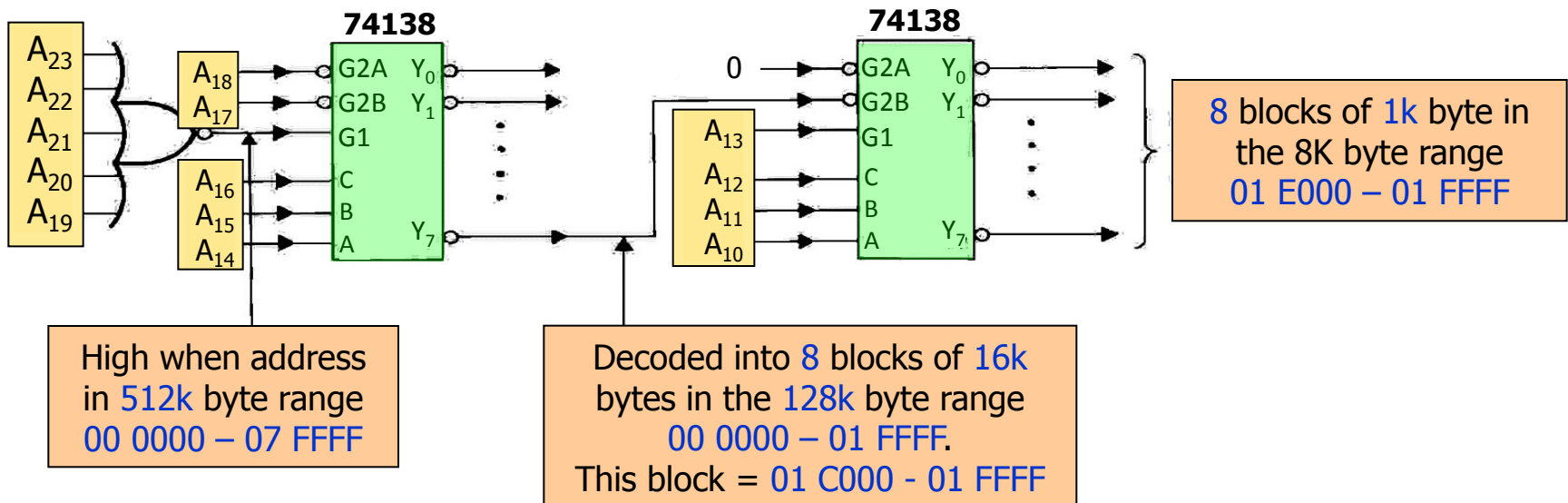
- Finally, the circuit below, provides very fine grained address decoder resolution to provide **8 blocks of 1K byte** in the address range **01 E000 – 01 FFFF**.
- Such a scheme might be employed to select 1 of 8 possible small I/O devices within the system and limit their address space to a very small part of the overall memory map of the system.



Address Decoding Techniques

Address Decoding Using Programmable logic


- Simple programmable logic has an architecture ideally suited to implementing a sum-of-products (SOP) expression.
- Given that any decoder can be expressed in SOP form it follows that we can program a GAL to do any address decoding function we like provided it has enough inputs and outputs.
- The illustration here demonstrates the principle with a simplified section of a device.
- This device has **3 input terms**, $[a_0, a_1, a_2]$ which are available in their **normal** and **inverted** forms.
- The diagram illustrates a device with **6 product terms**, i.e. **6 AND** gates connected via 'fuses' to any combination of the **3 input terms**, thus each AND gate has **6 inputs** and **6 fuses**.
- Designing address decoders with PALs involves **generating the Boolean logic equations** from the address table and 'generating a fuse map' (JEDEC file) which can be downloaded to a Prom programmer to 'blow' the device.

 

Address Decoding Techniques

GAL Example: GAL16V8

 
- The Pin out for the Lattice GAL16V8 is shown below:



The pins can be grouped as follows:

Pins	Signal Names
1	Clock input (not used for decoding)
2-9	Inputs: Address line from CPU
10	Ground (0V)
11	Output Enable
12-19	Outputs: Chips selects
20	Power (5V)

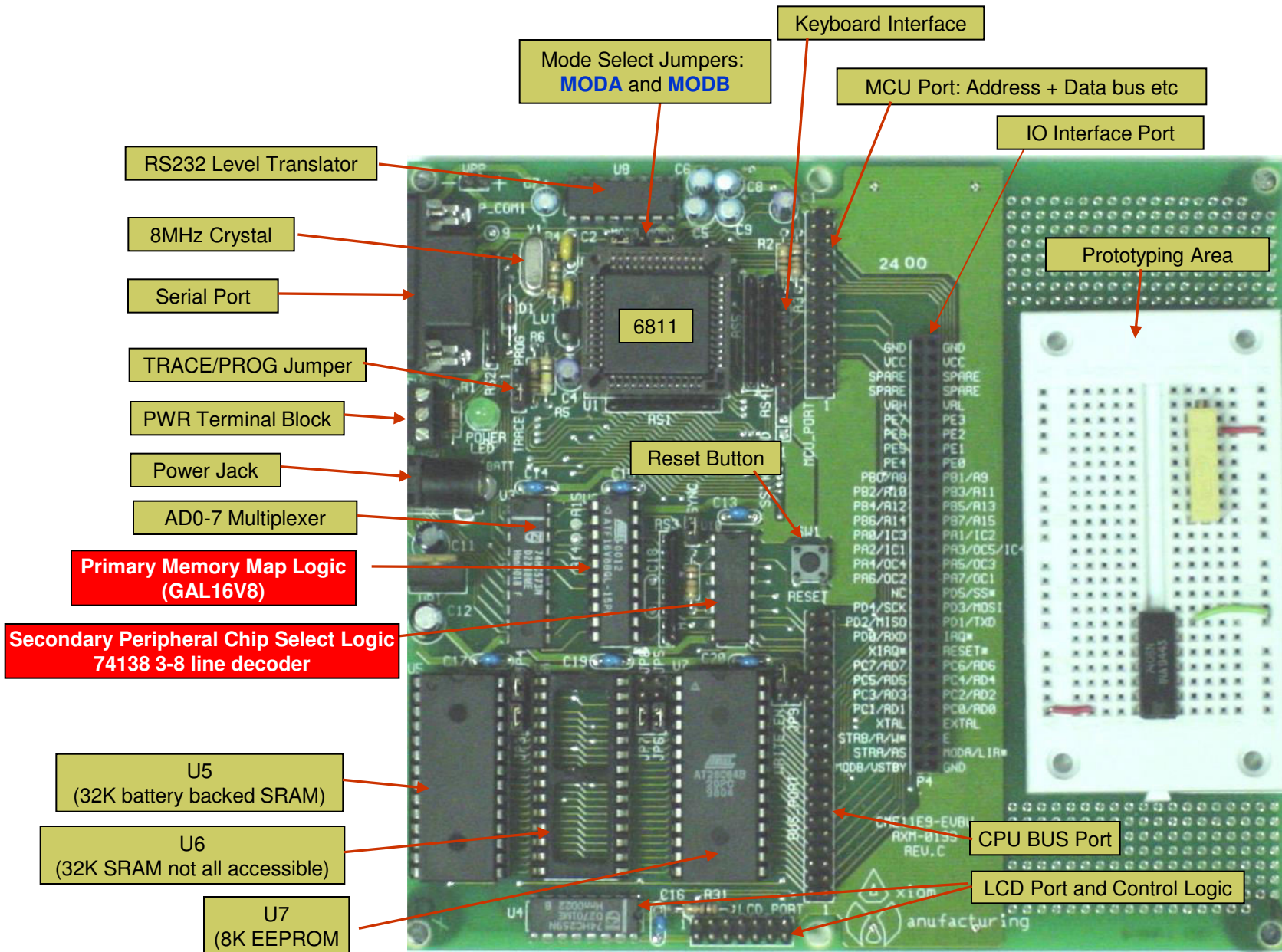- The **GAL16V8** is a fast PAL with a **3.5nsec** decode time.
- It uses an **erasable process technology**, with a **100msec** erase time.
- This device performed address decoding duties on the 6811 boards some that we used a few years ago in ECE 259.



Axiom 68HC11 - Microcomputer System Board