 



Static Memory Systems Design

- **Async Static (SRAM) Memory Technology**
 - Internal Architecture of the Async SRAM Chip.
 - Operation of a Single bit Sram Cell – read/write operation.
 - Important Asynchronous Sram Timing Parameters
- **Synchronous and Dual Port SRAM**



Asynchronous Static Memory on the DE2

 - The *vast majority* of stand-alone Sram chips are **asynchronous** by nature, i.e. they require **no clock** and operation is defined by the asynchronous timing of control signals, i.e. the **levels** of the signals rather than clocks/edges.
- The **DE2** board has an external **256k x 16** asynchronous SRAM chip made by **ISSI**, as well as some synchronous Sram on the FPGA.




A0	1	44	A17
A1	2	43	A16
A2	3	42	A15
A3	4	41	OE
A4	5	40	UB
CE	6	39	LB
I/O0	7	38	I/O15
I/O1	8	37	I/O14
I/O2	9	36	I/O13
I/O3	10	35	I/O12
Vcc	11	34	GND
GND	12	33	Vcc
I/O4	13	32	I/O11
I/O5	14	31	I/O10
I/O6	15	30	I/O9
I/O7	16	29	I/O8
WE	17	28	NC
A5	18	27	A14
A6	19	26	A13
A7	20	25	A12
A8	21	24	A11
A9	22	23	A10

IS61LV25616


General Architecture of an Asynchronous Sram Chip

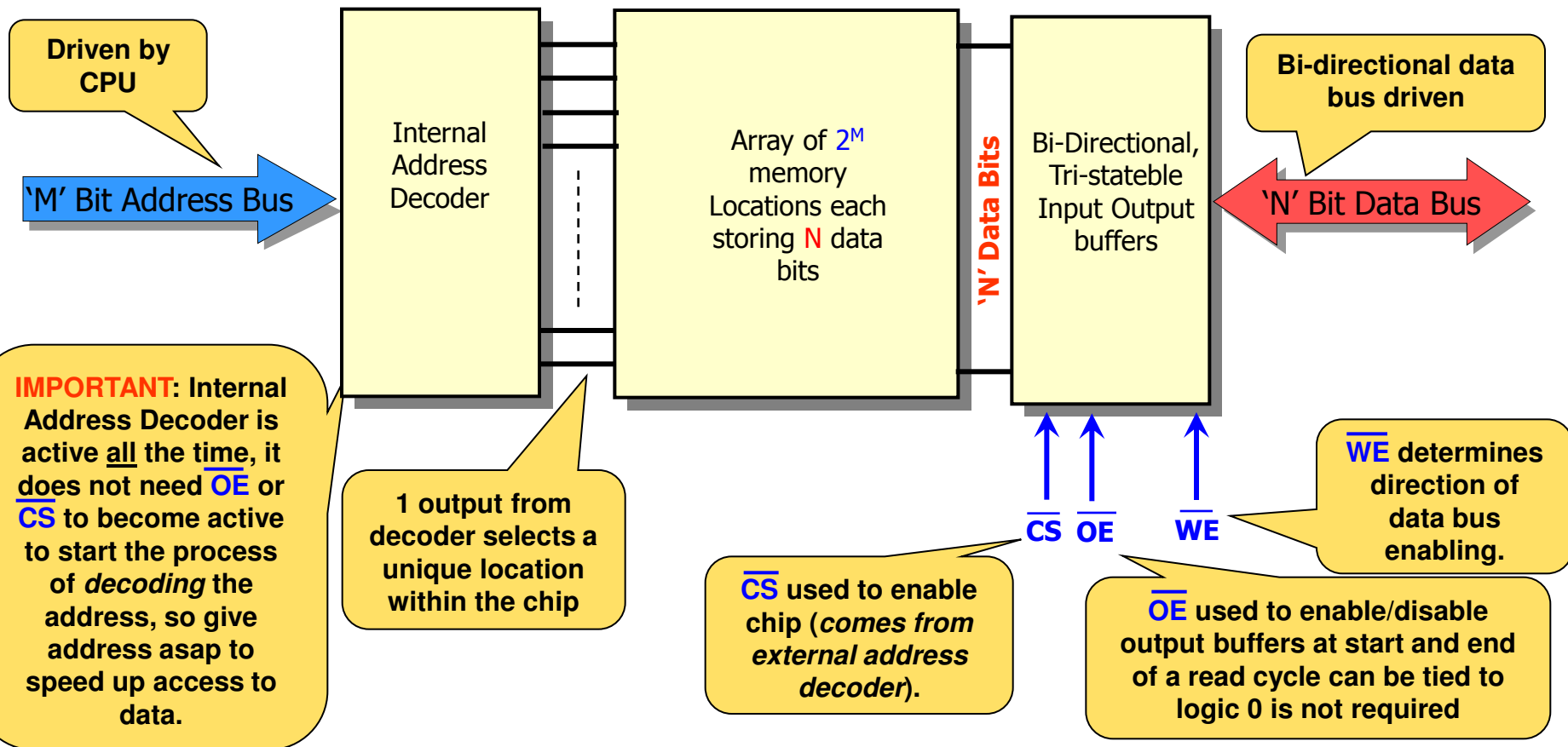- Internally an SRAM chip is organised as an **array** of memory locations.
- Each location is able to store **1** or **more** bits. Defined by the **width** of the chips Data Bus.
- 'M' address lines are **internally** decoded to select **1 unique location** from 2^M locations.



Architecture of a 32k x 8 Asynchronous Sram Chip



- To simplify the internal address decoder, a 32k device (with 15 address lines) is physically organised into two smaller row and column decoders.
- The Row decoder is fed with 8 (of the 15) address lines selecting 1 of 256 rows.
- The Column decoder is fed with the remaining 7 address lines selecting 1 out of a possible 128 columns. The intersection of a row and column output is used to select a location within a 2 dimensional array within the chip.

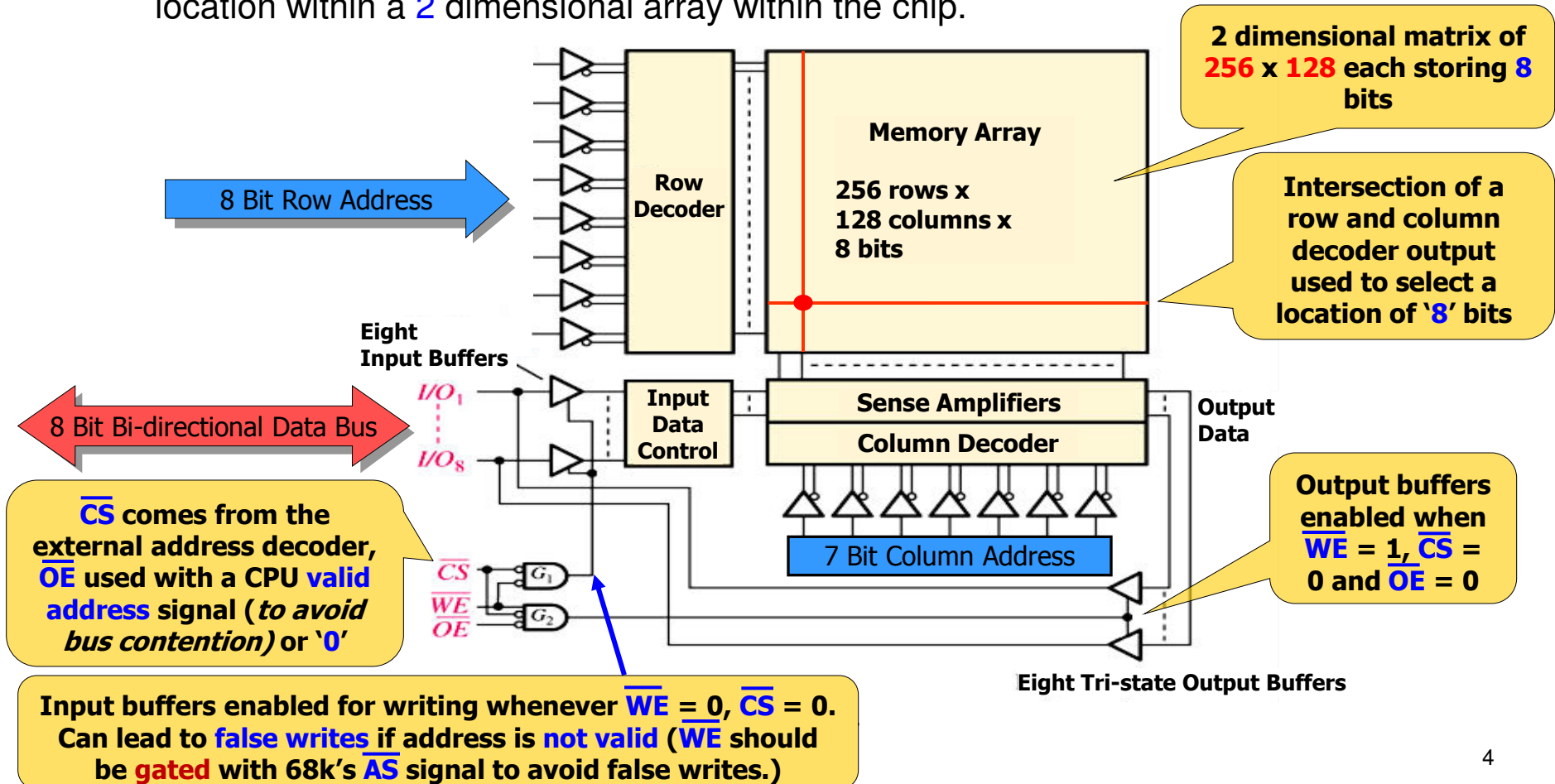

Static Memory Technology

Static (SRAM) Memory Cell


- The illustration opposite is that of an SRAM cell able to store a **single bit** of data, requiring **six** Mosfets (**6T** cell).
- Four low power Mosfets are used to make a pair of **inverters** – i.e. **NOT** gates.
- The two inverters are connected in a **back-to-back** loop, with the output of one connected as the input of the other, **reinforcing** each other, providing two **stable states** at the output of each inverter: '0' or '1'. It is these inverters that perform the data storage.
- The other two Mosfets control activation of the cell for reading and writing purposes and are activated by memory chip's **internal address decoder**, selecting a cell within the chip.

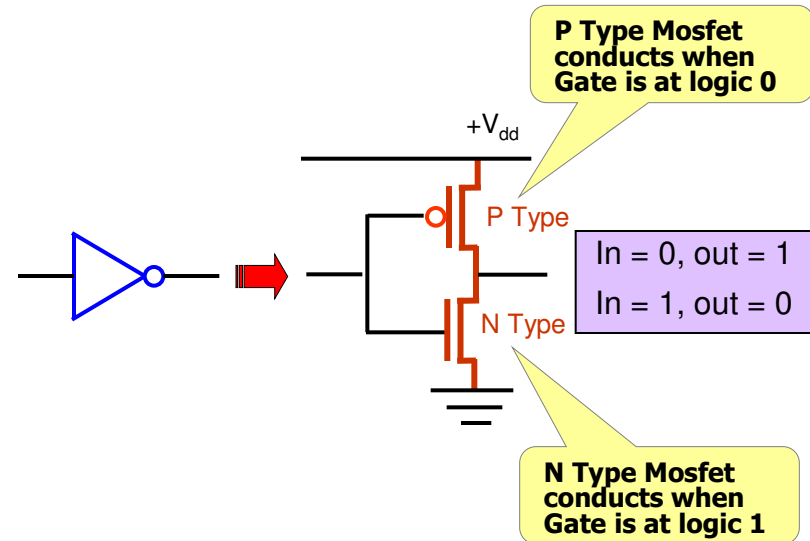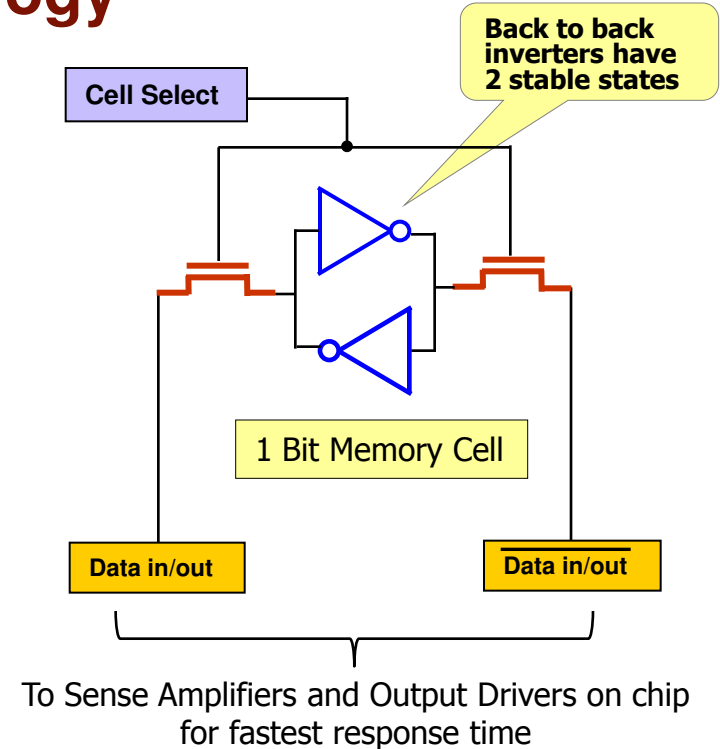

Static Memory Technology

Reading

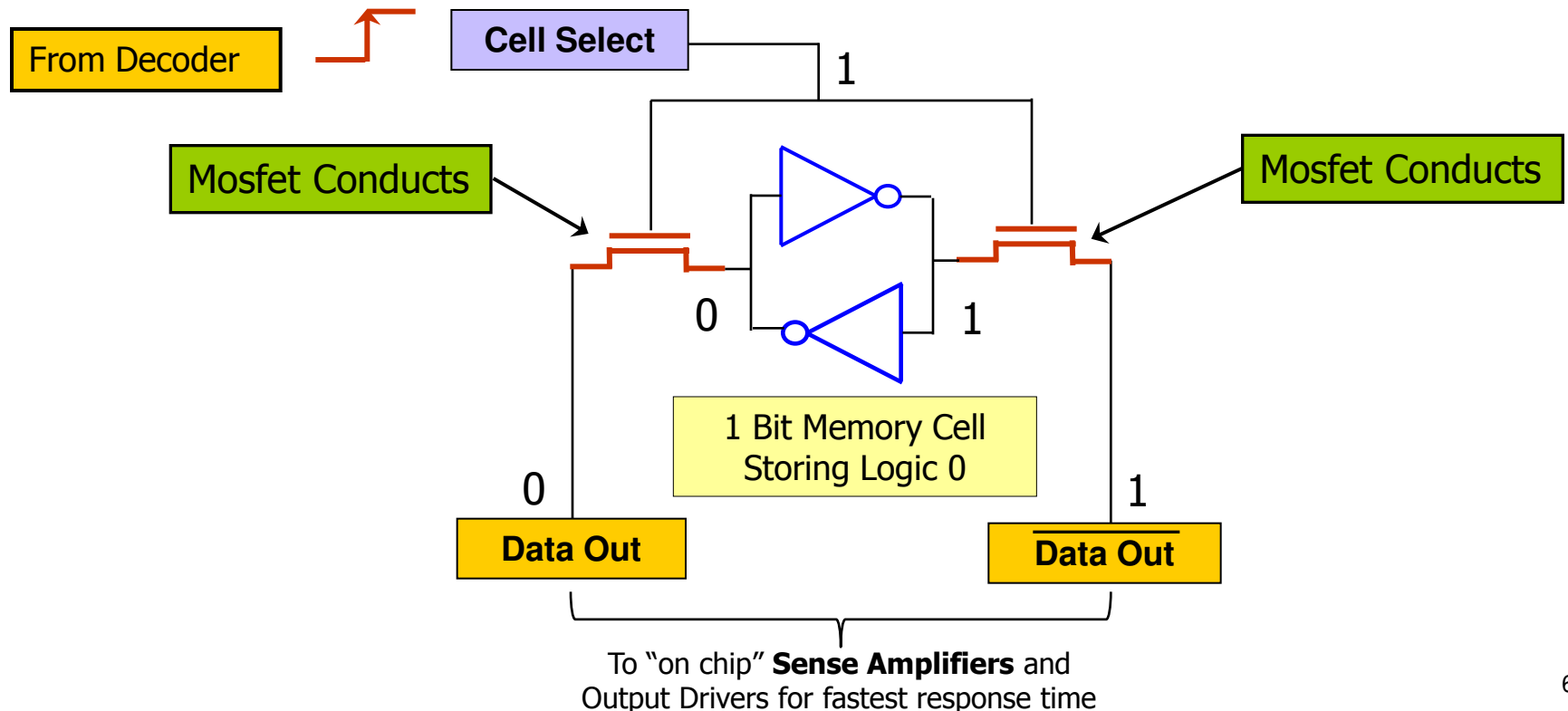
- The *cell select* line is activated (*logic 1*) by the internal address decoder in response to a CPU address. The signal is formed from the 'AND' of the internal row and column decoders. This turns on the two control Mosfets and the differential (*opposite*) value of the two inverter outputs is fed to a *sense amplifier* which drives the Logic 0 or 1 at the chip output buffers.



Static Memory Technology



Writing

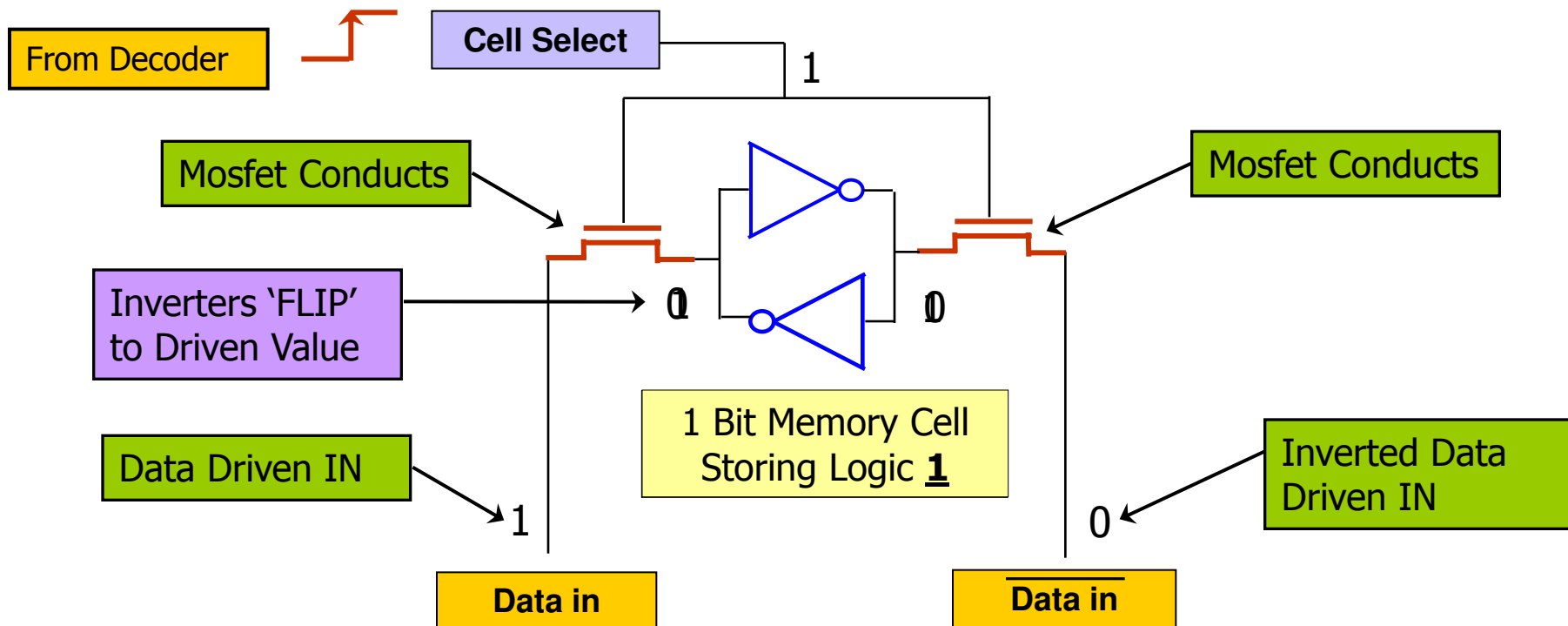- To **write** to the cell, the **cell select** line is again taken high in response to a particular address, but this time the CPU's data is **driven** into the **Data in/out** line (*and its inverse*). The higher power control mosfets literally **overpower** the inverters to adopt the appropriate stable state.



Static Memory Technology

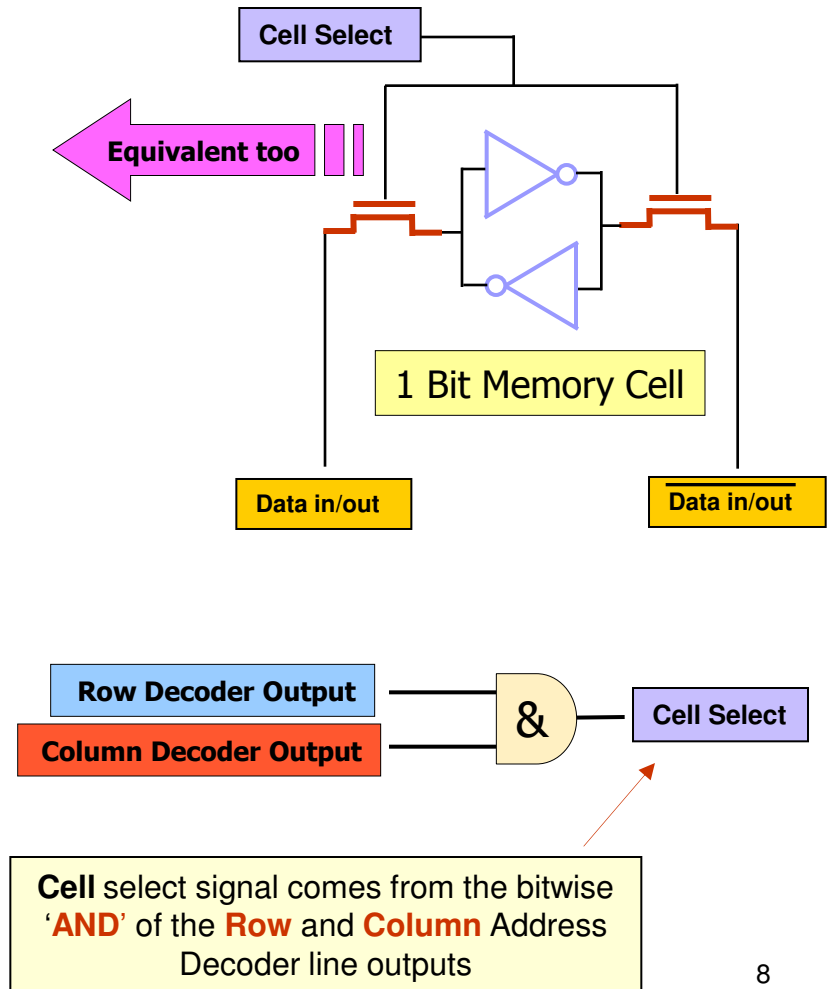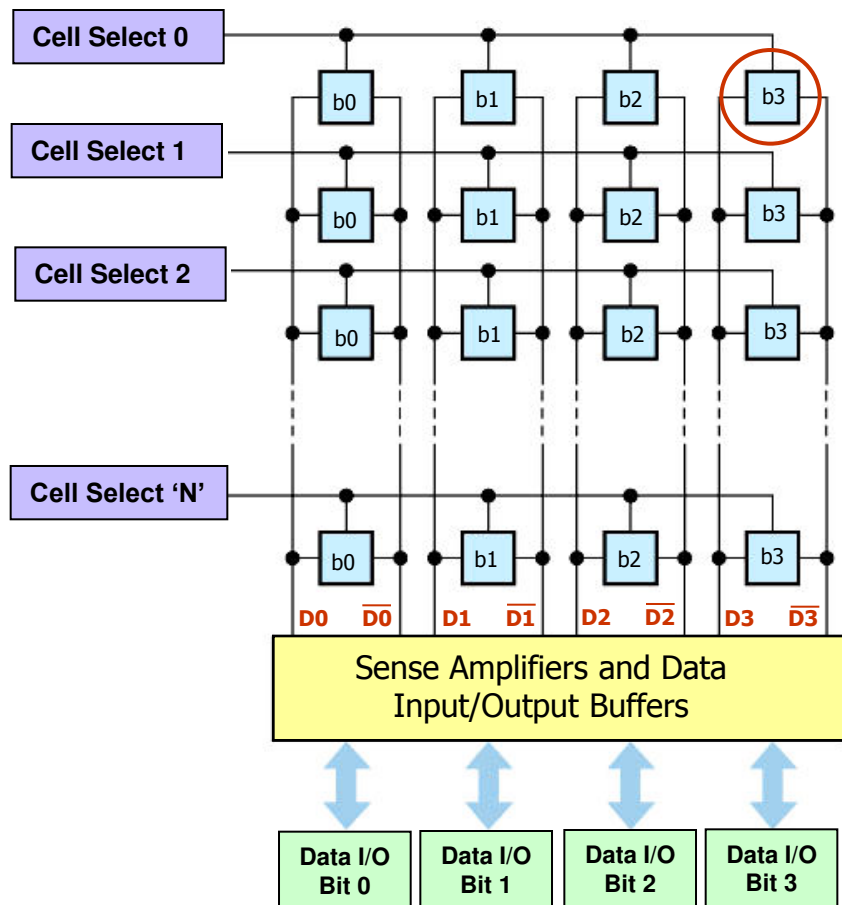- The illustration below shows how a **4 bit wide** memory chip might be organised internally.
- Each blue cell corresponds to the 6 transistor implementation seen previously, capable of storing a single bit of data. Thus in this case, 4 cells are activated by each cell select line.
- The **cell select** lines correspond to **Row** and **Column** decoder outputs **And'ed** together.




Asynchronous Static Memory Timing Diagrams – Read Cycle

- An appreciation of the timing characteristics of an **Async** Sram chip is essential for determining if a specific device will interface to the CPU correctly. For example, is it **fast enough** to supply the data, during a CPU **read** operation.

t_{AA} – The **worst case Read Access Time** of the chip after address becomes **stable**. A **key** parameter

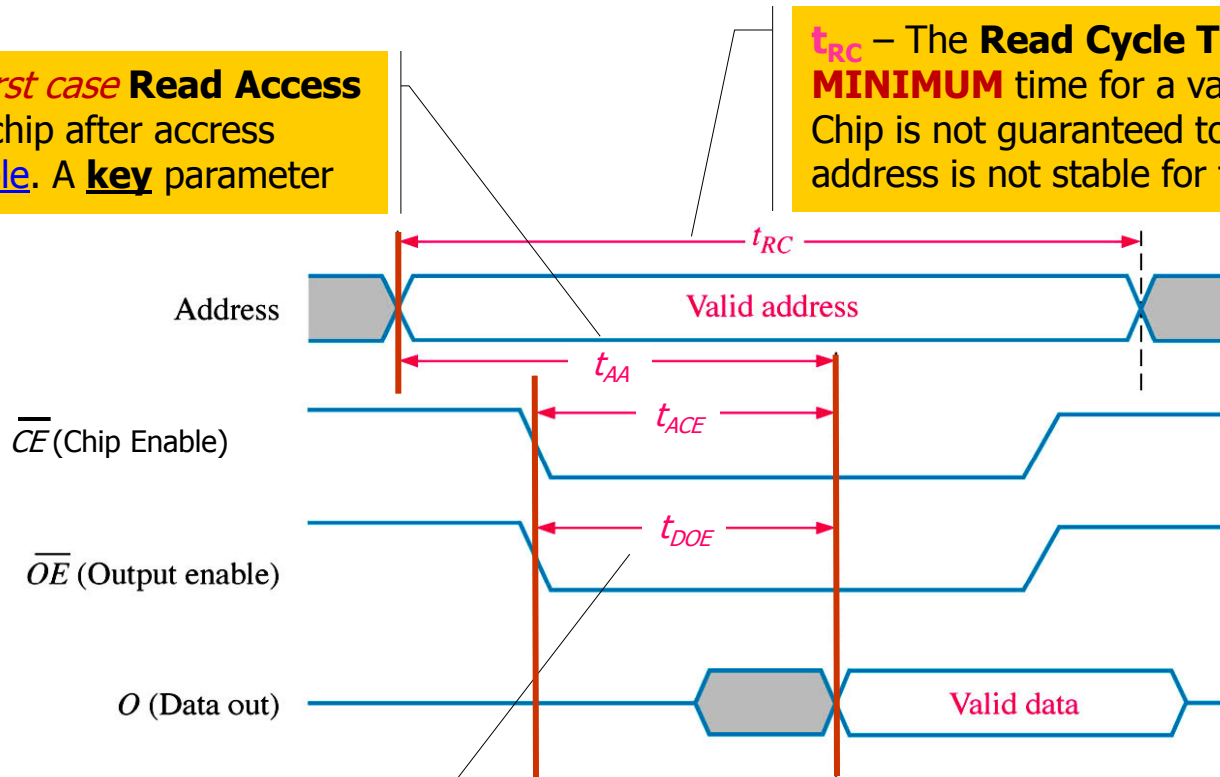t_{RC} – The **Read Cycle Time** of the chip, the **MINIMUM** time for a valid read operation. Chip is not guaranteed to read correctly if address is not stable for this length of time.




t_{ACE} and t_{DOE} – The **worst case** time taken to **turn on** the output buffers of the chip after presentation of \overline{CE} and/or \overline{OE} which **can** delay the data out if either is late or delayed.

Key design decisions for READ operation:

- 1) Make sure \overline{CE} and \overline{OE} arrive early so as **not** to delay turning on output buffers inside the memory chip (usually easy)
- 2) Get the CPU **address** to the chip **ASAP** don't wait for \overline{AS} . This means internal decoders can go to work on the address quickly.
- 3) Make sure CPU **waits** T_{AA} seconds before "**reading**" Data.

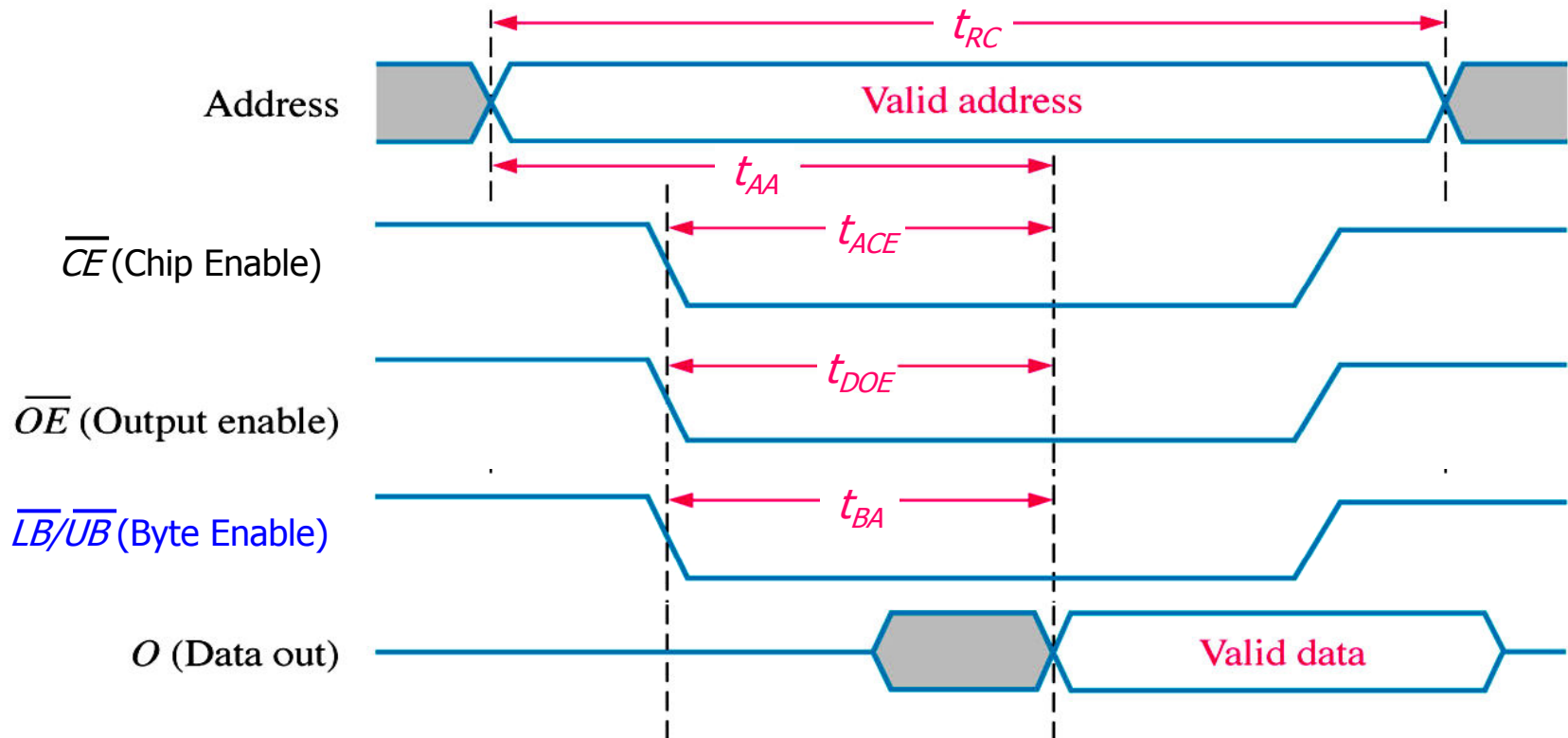Example Static Ram Memory Chip

The **ISSI IS61LV25616-10** **256K** x **16** Async Static Ram (**DE2**) – Read Cycle Parameters




Parameter	Symbol	Min	Max
Read Cycle Time	t_{RC}	10ns	
Address Access Time	t_{AA}		10ns
Chip Enable Access Time	t_{ACE}		10ns
Output Enable Access Time	t_{DOE}		4ns
Byte Enable Access Time	t_{BA}		4ns

Propagation Delays Inherent in Memory Systems


Other Timing Considerations

- The block diagram below shows a **simple** 68k CPU interfacing to a **256K** word memory chip. The Parameters, t_{PAB} , t_{PAD} , t_{PDB} and t_{AA} indicate the various signal propagation delays and access times that may be encountered (*depending on inclusion of buffers etc.*) along the way, during a CPU **read** cycle. Time t_{DSU} is the Data **setup** time back at data pins of the CPU. Why are these important?
- When the CPU outputs an address, it will expect to sample the data some time later. Our job is to do the **timing analysis** and make sure that our data is back at the CPU in time to be read.

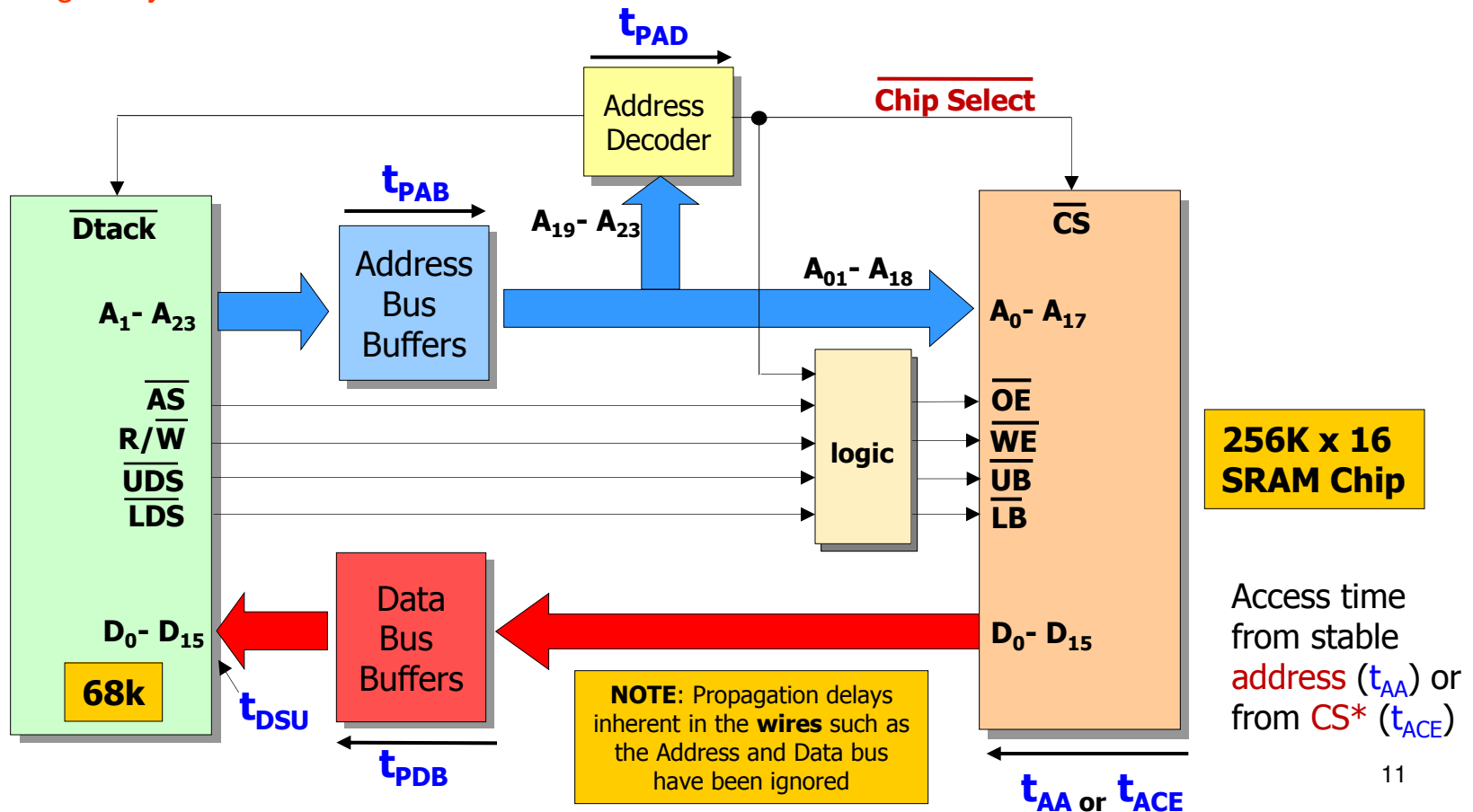

Typical CPU Read Cycle Timing

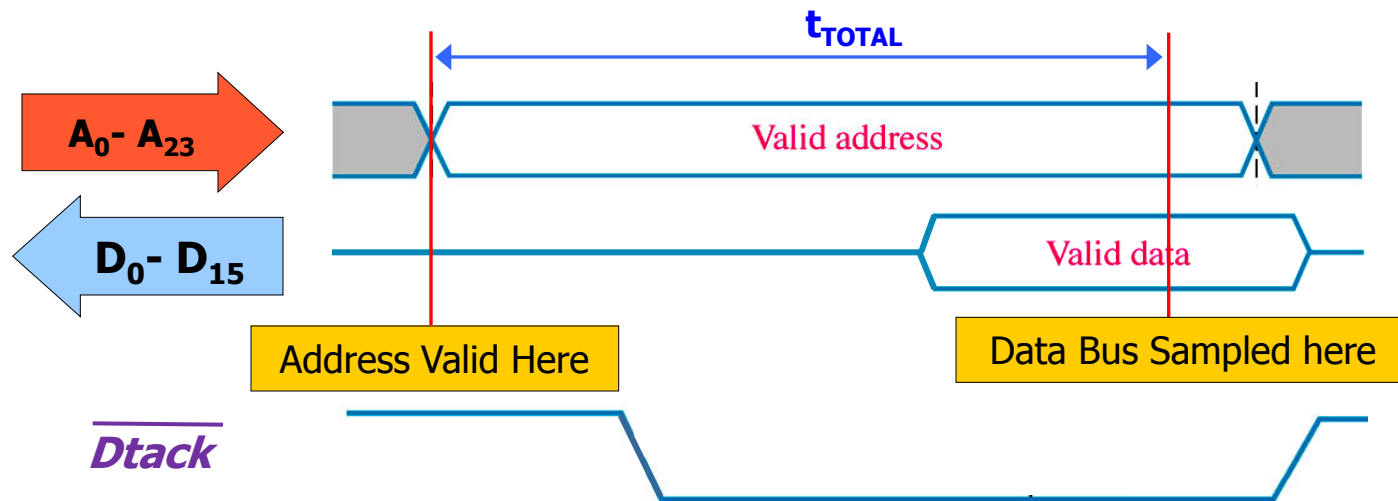- The timing diagram below shows a simple but typical 68k **read** cycle in action.
- An address is **issued**, and some time t_{TOTAL} later, after D_{tack} received, the CPU will expect the memory system to have decoded the address and supplied the data back at the CPU data inputs.



- We can see that in order for the memory system to work correctly for a CPU **read**

$$t_{TOTAL} > t_{PAB} + t_{AA} + t_{PDB} + t_{DSU}$$


$$t_{TOTAL} > t_{PAB} + t_{PAD} + t_{ACE} + t_{DSU}$$

Synchronous Sram

- Synchronous Sram (**SSRAM**) is a development of Asynchronous Sram for **very high speed** systems and uses a clock synchronised to the CPU. Often used as cache memory.
- Same internal Architecture and Sram Cell (**6 Mosfets** per bit) etc.
- Asynchronous control signals such as **CS***, **Address Bus**, **Data Bus**, **R/W*** etc. latched internally (*see below right for latches on input/output signals*) on a clock edge, meaning address and data-in etc. do not need to be held for duration of read/write, i.e. they can change while read/write is in progress making successive access's faster.
- Data out may also be latched as an option but this delay access to memory by 1 more clock cycle.
- Some SSRams may have internal **counters** to auto increment the last address, allowing **burst reading** or **writing** of data **from/to chip**, one data item per clock without need for a new address from CPU.

Synchronous Sram

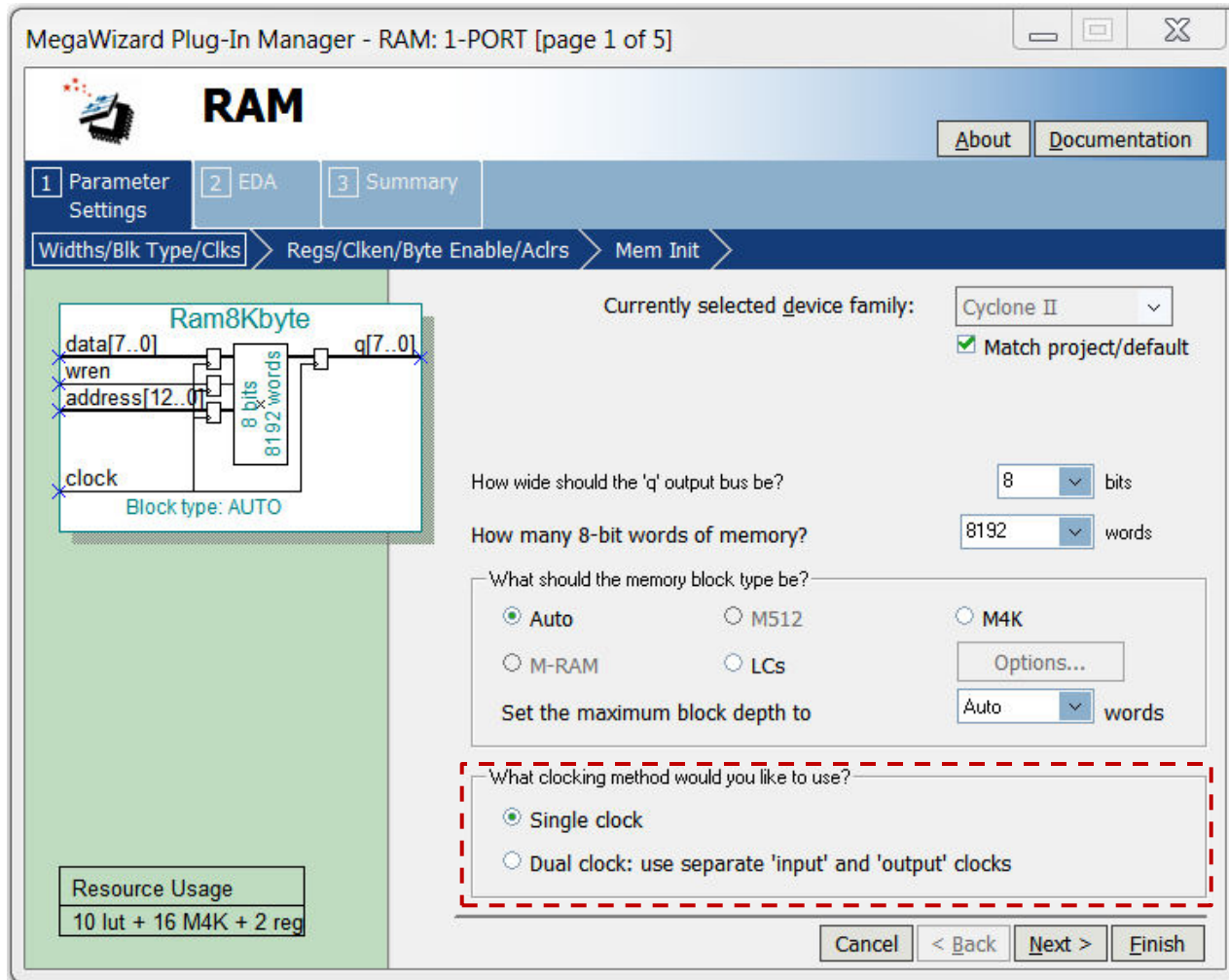
- Altera's FPGAs only support SSRam. An example illustration of the Megawizard in Quartus being used to construct 8k bytes of SSRam is shown below.



Synchronous Sram

Class Exercise 1:

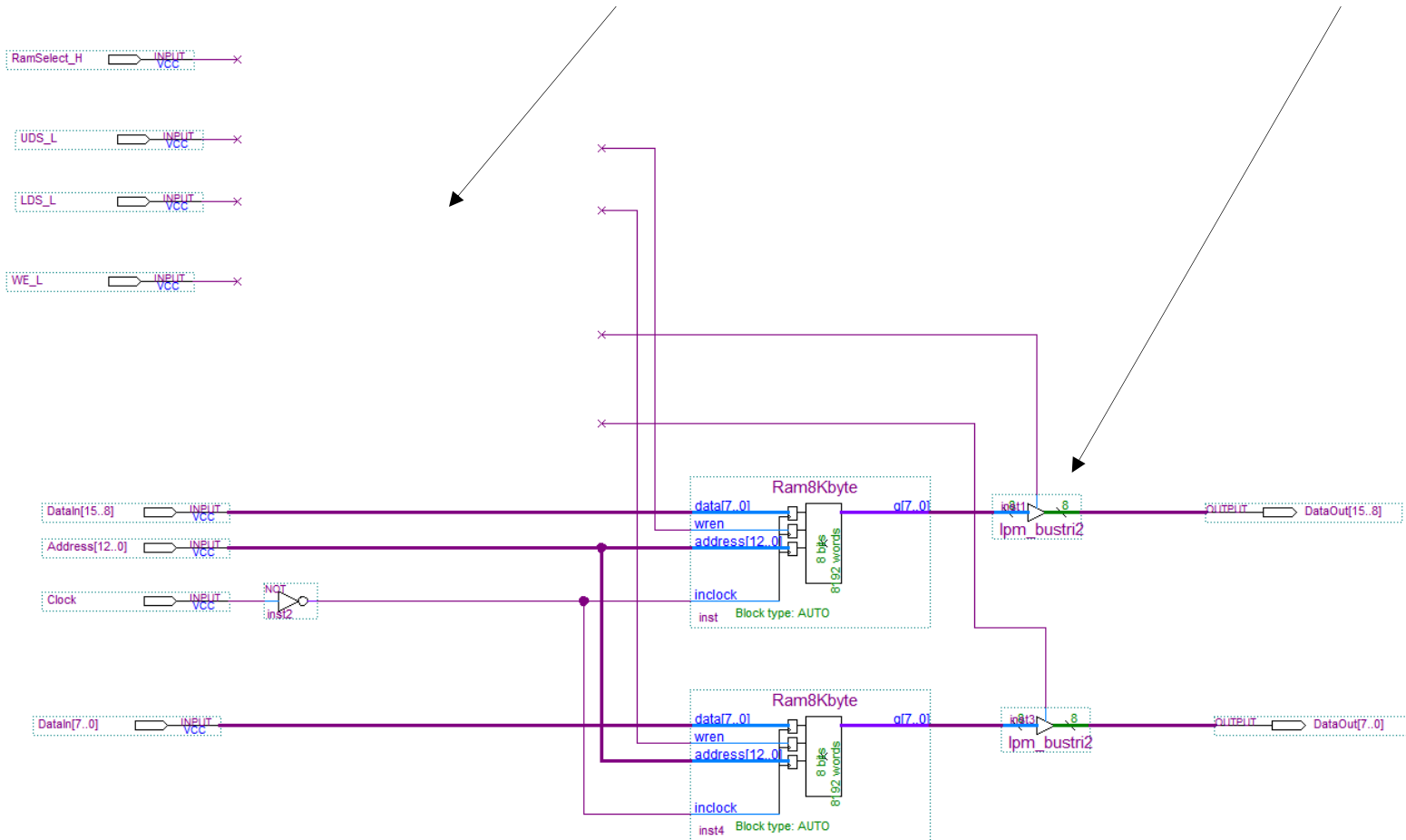- Think about the logic to drive the Sync SRam and the output buffers below.



- Don't worry about timing at the moment, just functionality


Tri-State Memory Outputs

Class Exercise 2:

- Why do memory chips typically need **tri-state outputs**?
- What is wrong with just connecting the **memory outputs** directly back to the CPU **data inputs**?

Synchronous Sram Read Operation Timing

 - An example of a ssram chip **read** cycle timing is shown below for the Microsemi WED2DL32512V **512k x 32 **pipelined, burst mode**** device.
- **CE, WE, Addr Latch** and **Address** signals latched on rising clock edge.
- In non burst mode, data out available on next clock edge, subject to no delay in asserting OE L




Dual Ported Sram

- Dual Port Sram has **two address**, **two data** and **two control buses** to allow two devices to simultaneously share the same memory without external synchronisation or *multiplexing* of those signals.
- **Rare** to see this for **external** chips due to the number of pins required, however it's common on ASICs and FPGAs.

Application 1: - Multi-processor applications:

 
- Two CPUs can share data through the use of dual port Ram - Some Sram chips have built in **hardware semaphores** for processor synchronisation so that read/modify/writes by two processors to the same locations do not interfere e.g. two processors trying to say increment the data in the same location at the same time.



Dual Ported Sram

Application 2: Video Memory frame buffer

- Dual port memory also enables a video display controller to display images at the **same time** as the CPU/GPU is updating the image (i.e. writing to video memory).
- This reduces **flicker** that might occur on the display monitor if **single port memory** had been used (*due to the GPU taking control of the memory chip's only/single port during drawing/writing.*) and **eliminates** the external multiplexer that would be required to switch the memory between Video controller and GPU.
- It also means the GPU can draw a new image at full speed without having to wait for the **horizontal** and **vertical “sync”** periods when the video controller is not displaying an image (*at the end of a line or frame*).

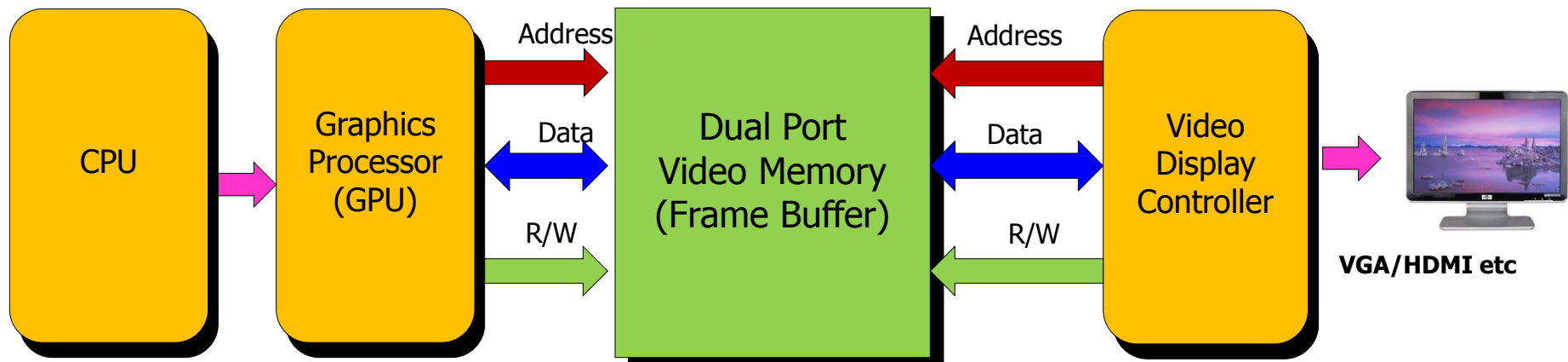

Dual Ported Synchronous Sram

- Quartus can synthesize **dual port** *synchronous* sram on an FPGA

RAM: 2-PORT

1 Parameter Settings | 2 EDA | 3 Summary

General | **Widths/Blk Type** | Clks/Rd, Byte En | Regs/Clks/Aclrs | Mem Init

testmem

data_a[15..0]
address_a[15..0]
wren_a
data_b[15..0]
address_b[15..0]
wren_b
clock_a
clock_b

65536 Word(s) RAM

q_a[15..0]
q_b[15..0]

Block Type: AUTO

How many 16-bit words of memory? 65536

☐ Use different data widths on different ports

Read/Write Ports

How wide should the 'q_a' output bus be? 16

How wide should the 'data_a' input bus be? 16

How wide should the 'q_b' output bus be? 16

Note: You could enter arbitrary values for width and depth

What should the memory block type be?

☒ Auto ☐ M512 ☐ M4K

☐ M-RAM ☐ LCs Options...

Set the maximum block depth to Auto words

Resource Usage
392 lut + 256 M4K + 8 reg

Cancel < Back Next > Finish

Registers to hold input signals. Can have separate clocks (as shown here) or have a common clock.